
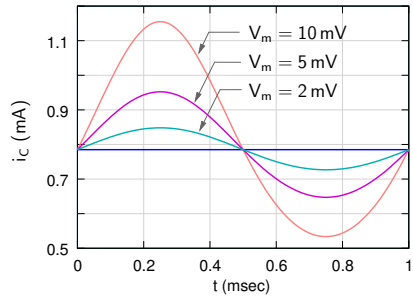


$$v_{BE}(t) = V_0 + V_m \sin \omega t$$

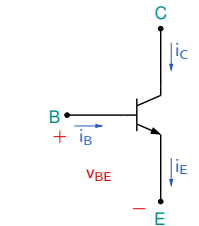
$$V_0 = 0.65 \text{ V}, \quad f = 1 \text{ kHz}$$






$$v_{BE}(t) = V_0 + V_m \sin \omega t$$
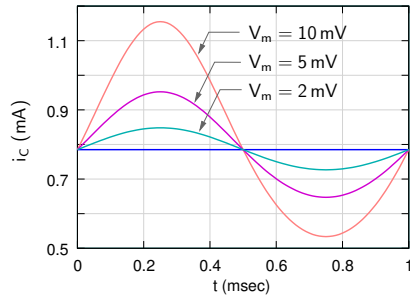
$$V_0 = 0.65 \text{ V}, \quad f = 1 \text{ kHz}$$




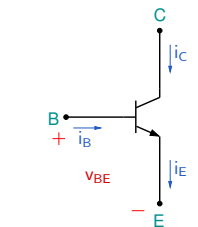- * As the v_{BE} amplitude increases, the shape of $i_C(t)$ deviates from a sinusoid → distortion.




$$v_{BE}(t) = V_0 + V_m \sin \omega t$$
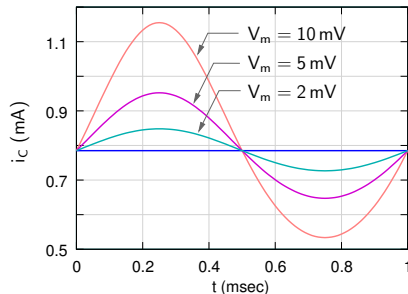
$$V_0 = 0.65 \text{ V}, \quad f = 1 \text{ kHz}$$




- * As the v_{BE} amplitude increases, the shape of $i_C(t)$ deviates from a sinusoid \rightarrow distortion.
- * If $v_{be}(t)$, i.e., the time-varying part of v_{BE} , is kept small, i_C varies linearly with v_{BE} . How small? Let us look at this in more detail.


BJT: small-signal model

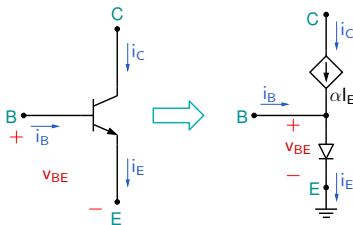

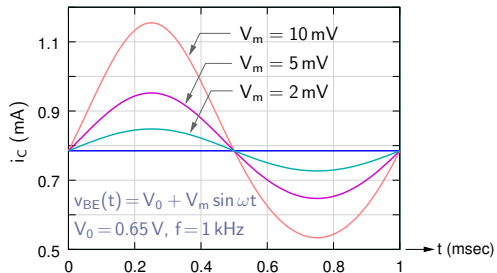Let $v_{BE}(t) = V_{BE} + v_{be}(t)$ (bias+signal), and $i_C(t) = I_C + i_c(t)$.




BJT: small-signal model


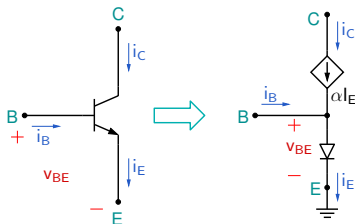


Let $v_{BE}(t) = V_{BE} + v_{be}(t)$ (bias+signal), and $i_C(t) = I_C + i_c(t)$.

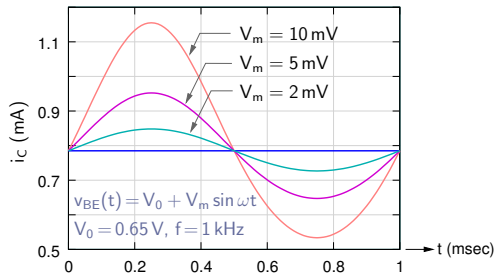Assuming active mode, $i_C(t) = \alpha i_E(t) = \alpha I_{ES} \left[\exp \left(\frac{v_{BE}(t)}{V_T} \right) - 1 \right]$.



BJT: small-signal model

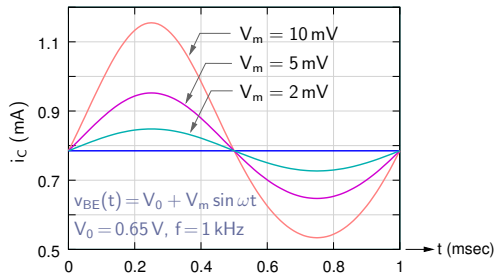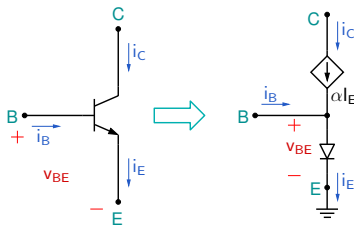



Let $v_{BE}(t) = V_{BE} + v_{be}(t)$ (bias+signal), and $i_C(t) = I_C + i_c(t)$.

Assuming active mode, $i_C(t) = \alpha i_E(t) = \alpha I_{ES} \left[\exp \left(\frac{v_{BE}(t)}{V_T} \right) - 1 \right]$.

Since the B-E junction is forward-biased, $\exp \left(\frac{v_{BE}(t)}{V_T} \right) \gg 1$, and we get

$$i_C(t) = \alpha I_{ES} \exp \left(\frac{v_{BE}(t)}{V_T} \right) = \alpha I_{ES} \exp \left(\frac{V_{BE} + v_{be}(t)}{V_T} \right) = \alpha I_{ES} \exp \left(\frac{V_{BE}}{V_T} \right) \times \exp \left(\frac{v_{be}(t)}{V_T} \right).$$

BJT: small-signal model

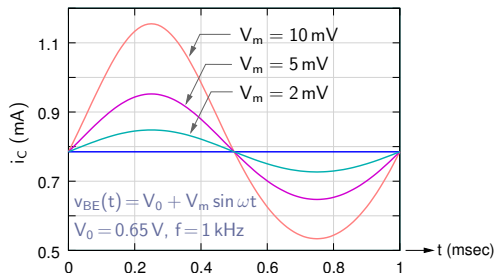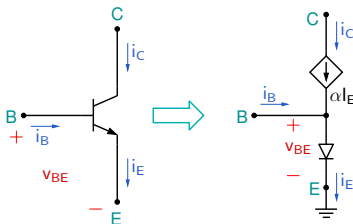

Let $v_{BE}(t) = V_{BE} + v_{be}(t)$ (bias+signal), and $i_C(t) = I_C + i_c(t)$.

Assuming active mode, $i_C(t) = \alpha i_E(t) = \alpha I_{ES} \left[\exp \left(\frac{v_{BE}(t)}{V_T} \right) - 1 \right]$.



Since the B-E junction is forward-biased, $\exp \left(\frac{v_{BE}(t)}{V_T} \right) \gg 1$, and we get

$$i_C(t) = \alpha I_{ES} \exp \left(\frac{v_{BE}(t)}{V_T} \right) = \alpha I_{ES} \exp \left(\frac{V_{BE} + v_{be}(t)}{V_T} \right) = \alpha I_{ES} \exp \left(\frac{V_{BE}}{V_T} \right) \times \exp \left(\frac{v_{be}(t)}{V_T} \right).$$

If $v_{be}(t) = 0$, $i_C(t) = I_C$ (the bias value of i_C), i.e., $I_C = \alpha I_{ES} \exp \left(\frac{V_{BE}}{V_T} \right)$



$$\Rightarrow i_c(t) = I_C \exp \left(\frac{v_{be}(t)}{V_T} \right).$$

BJT: small-signal model

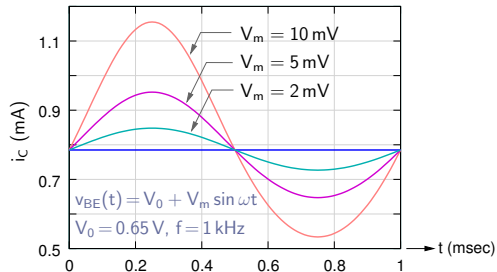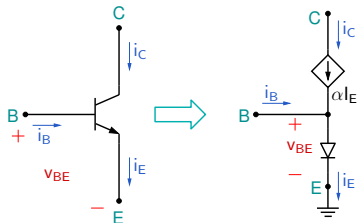

$$i_C(t) = I_C \exp\left(\frac{v_{be}(t)}{V_T}\right) = I_C \left[1 + x + \frac{x^2}{2} + \dots\right], \quad x = v_{be}(t)/V_T.$$

BJT: small-signal model

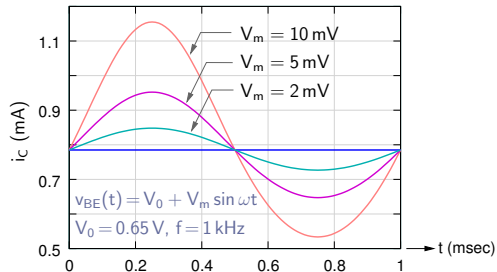
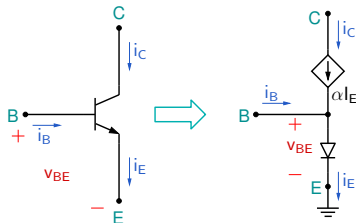


$$i_C(t) = I_C \exp\left(\frac{v_{be}(t)}{V_T}\right) = I_C \left[1 + x + \frac{x^2}{2} + \dots\right], \quad x = v_{be}(t)/V_T.$$

If x is small, i.e., if the amplitude of $v_{be}(t)$ is small compared to the thermal voltage V_T , we get

$$i_C(t) = I_C \left[1 + \frac{v_{be}(t)}{V_T}\right].$$

BJT: small-signal model

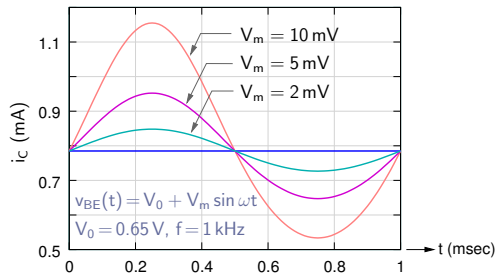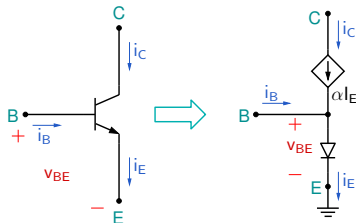



$$i_C(t) = I_C \exp\left(\frac{v_{be}(t)}{V_T}\right) = I_C \left[1 + x + \frac{x^2}{2} + \dots\right], \quad x = v_{be}(t)/V_T.$$

If x is small, i.e., if the amplitude of $v_{be}(t)$ is small compared to the thermal voltage V_T , we get

$$i_C(t) = I_C \left[1 + \frac{v_{be}(t)}{V_T}\right].$$

We can now see that, for $|v_{be}(t)| \ll V_T$, the relationship between $i_C(t)$ and $v_{be}(t)$ is linear, as we have observed previously.

BJT: small-signal model

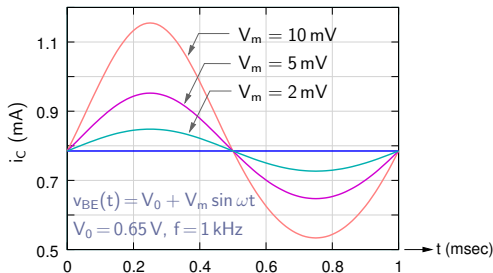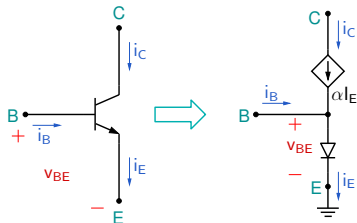

$$i_C(t) = I_C \exp\left(\frac{v_{be}(t)}{V_T}\right) = I_C \left[1 + x + \frac{x^2}{2} + \dots\right], \quad x = v_{be}(t)/V_T.$$


If x is small, i.e., if the amplitude of $v_{be}(t)$ is small compared to the thermal voltage V_T , we get

$$i_C(t) = I_C \left[1 + \frac{v_{be}(t)}{V_T}\right].$$

We can now see that, for $|v_{be}(t)| \ll V_T$, the relationship between $i_C(t)$ and $v_{be}(t)$ is linear, as we have observed previously.


$$i_C(t) = I_C + i_c(t) = I_C \left[1 + \frac{v_{be}(t)}{V_T}\right] \Rightarrow i_c(t) = \frac{I_C}{V_T} v_{be}(t)$$

BJT: small-signal model

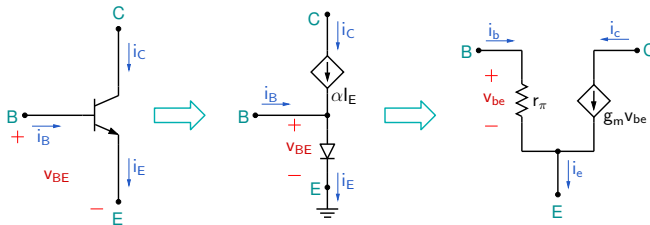

The relationship, $i_c(t) = \frac{I_C}{V_T} v_{be}(t)$ can be represented by a VCCS, $i_c(t) = g_m v_{be}(t)$, where $g_m = I_C/V_T$ is the “transconductance.”

BJT: small-signal model

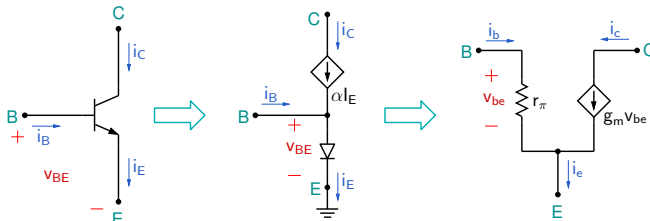


The relationship, $i_c(t) = \frac{I_C}{V_T} v_{be}(t)$ can be represented by a VCCS, $i_c(t) = g_m v_{be}(t)$, where $g_m = I_C/V_T$ is the “transconductance.”

For the base current, we have,

$$i_B(t) = I_B + i_b(t) = \frac{1}{\beta} [I_C + i_c(t)]$$

$$\rightarrow i_b(t) = \frac{1}{\beta} i_c(t) = \frac{1}{\beta} g_m v_{be}(t) \rightarrow v_{be}(t) = (\beta/g_m) i_b(t).$$

BJT: small-signal model

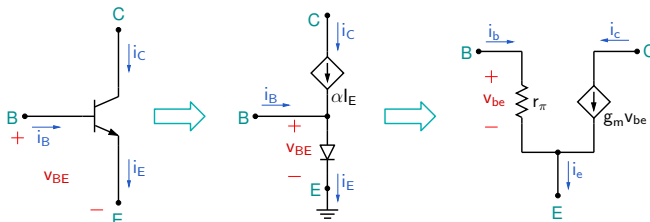

The relationship, $i_c(t) = \frac{I_C}{V_T} v_{be}(t)$ can be represented by a VCCS, $i_c(t) = g_m v_{be}(t)$, where $g_m = I_C/V_T$ is the “transconductance.”


For the base current, we have,

$$i_B(t) = I_B + i_b(t) = \frac{1}{\beta} [I_C + i_c(t)]$$

$$\rightarrow i_b(t) = \frac{1}{\beta} i_c(t) = \frac{1}{\beta} g_m v_{be}(t) \rightarrow v_{be}(t) = (\beta/g_m) i_b(t).$$

The above relationship is represented by a resistance, $r_\pi = \beta/g_m$, connected between B and E.

BJT: small-signal model

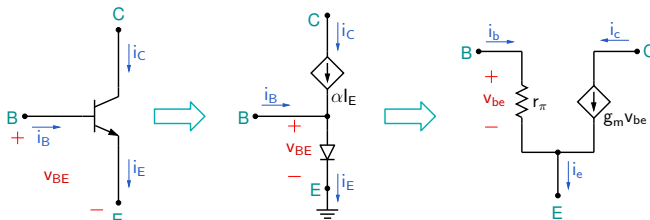

The relationship, $i_c(t) = \frac{I_C}{V_T} v_{be}(t)$ can be represented by a VCCS, $i_c(t) = g_m v_{be}(t)$, where $g_m = I_C/V_T$ is the “transconductance.”


For the base current, we have,

$$i_B(t) = I_B + i_b(t) = \frac{1}{\beta} [I_C + i_c(t)]$$


$$\rightarrow i_b(t) = \frac{1}{\beta} i_c(t) = \frac{1}{\beta} g_m v_{be}(t) \rightarrow v_{be}(t) = (\beta/g_m) i_b(t).$$

The above relationship is represented by a resistance, $r_\pi = \beta/g_m$, connected between B and E.

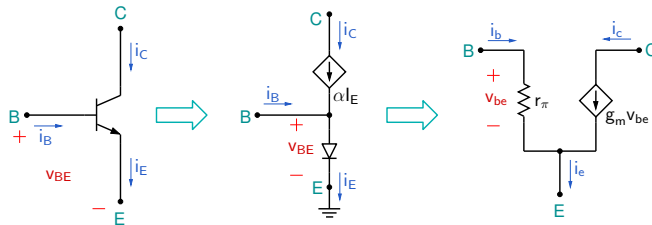
The resulting model is called the π -model for small-signal description of a BJT.



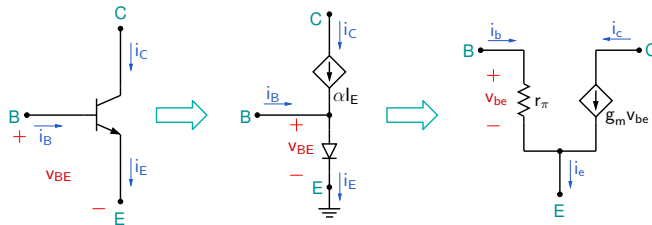- * The transconductance g_m depends on the biasing of the BJT, since $g_m = I_C/V_T$. For $I_C = 1\text{ mA}$, $V_T \approx 25\text{ mV}$ (room temperature), $g_m = 1\text{ mA}/25\text{ mV} = 40\text{ m}\Omega$ (milli-mho or milli-siemens).




- * The transconductance g_m depends on the biasing of the BJT, since $g_m = I_C/V_T$. For $I_C = 1 \text{ mA}$, $V_T \approx 25 \text{ mV}$ (room temperature), $g_m = 1 \text{ mA}/25 \text{ mV} = 40 \text{ mS}$ (milli-mho or milli-siemens).
- * r_π also depends on I_C , since $r_\pi = \beta/g_m = \beta V_T/I_C$. For $I_C = 1 \text{ mA}$, $V_T \approx 25 \text{ mV}$, $\beta = 100$, $r_\pi = 2.5 \text{ k}\Omega$.

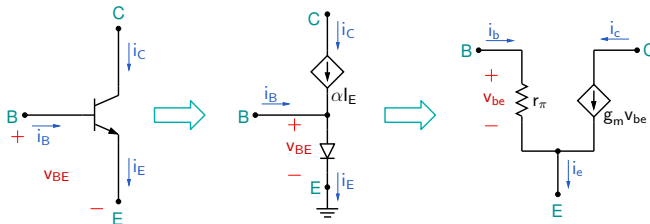


- * The transconductance g_m depends on the biasing of the BJT, since $g_m = I_C/V_T$. For $I_C = 1\text{ mA}$, $V_T \approx 25\text{ mV}$ (room temperature), $g_m = 1\text{ mA}/25\text{ mV} = 40\text{ m}\Omega$ (milli-mho or milli-siemens).
- * r_π also depends on I_C , since $r_\pi = \beta/g_m = \beta V_T/I_C$. For $I_C = 1\text{ mA}$, $V_T \approx 25\text{ mV}$, $\beta = 100$, $r_\pi = 2.5\text{ k}\Omega$.
- * Note that the small-signal model is valid only for small v_{be} (small compared to V_T).

BJT: small-signal model

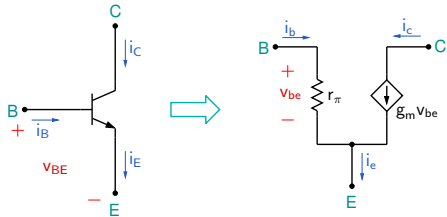


* In the above model, note that i_c is independent of v_{ce} .

BJT: small-signal model



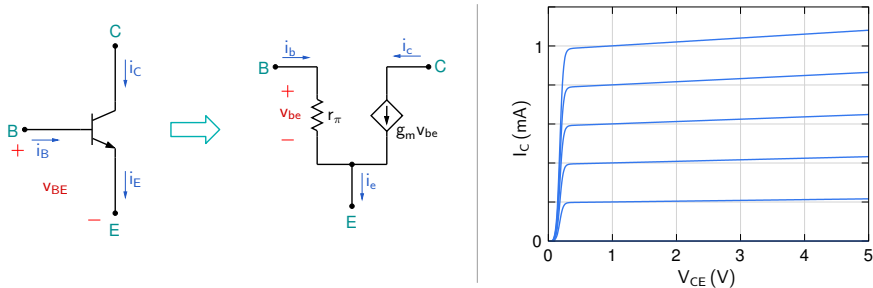


- * In the above model, note that i_c is independent of v_{ce} .
- * In practice, i_c does depend on v_{ce} because of the Early effect, and $\frac{dI_C}{dV_{CE}} \approx \text{constant} = 1/r_o$, where r_o is called the output resistance.

BJT: small-signal model

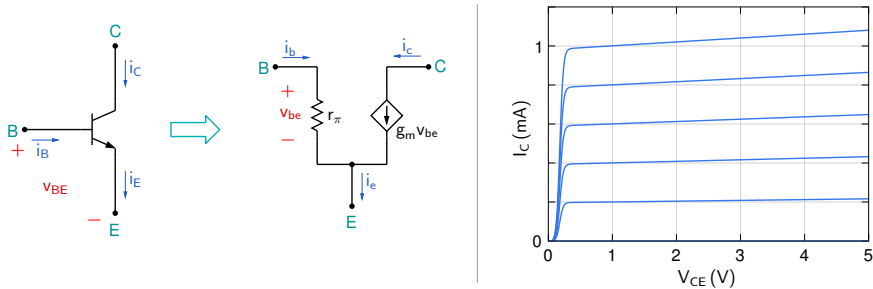


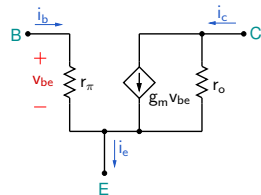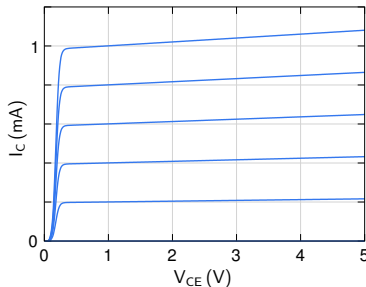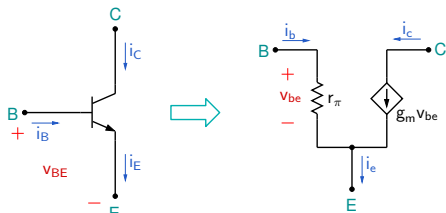- * In the above model, note that i_c is independent of v_{ce} .
- * In practice, i_c does depend on v_{ce} because of the Early effect, and $\frac{dI_C}{dV_{CE}} \approx \text{constant} = 1/r_o$, where r_o is called the output resistance.
- * A more accurate model includes r_o as well.



- * In the above model, note that i_c is independent of v_{ce} .
- * In practice, i_c does depend on v_{ce} because of the Early effect, and $\frac{dI_C}{dV_{CE}} \approx \text{constant} = 1/r_o$, where r_o is called the output resistance.
- * A more accurate model includes r_o as well.

BJT: small-signal model

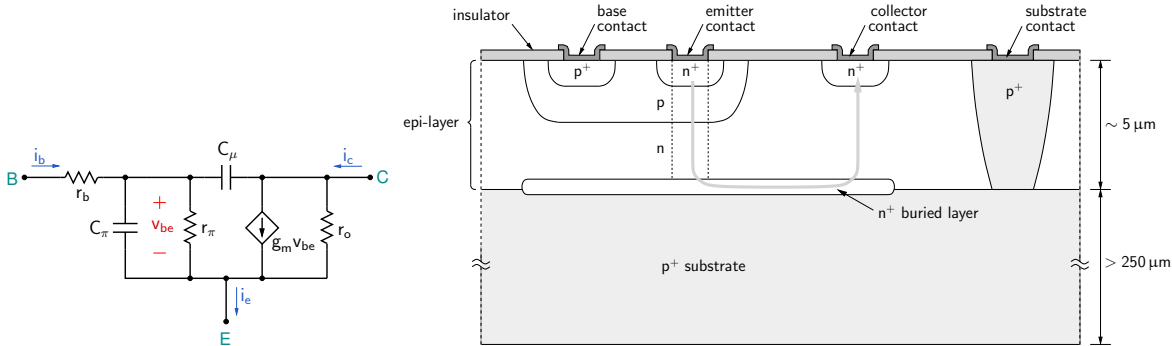



* A few other components are required to make the small-signal model complete:

r_b : base spreading resistance

C_π : base charging capacitance + B-E junction capacitance

C_μ : B-C junction capacitance

BJT: small-signal model

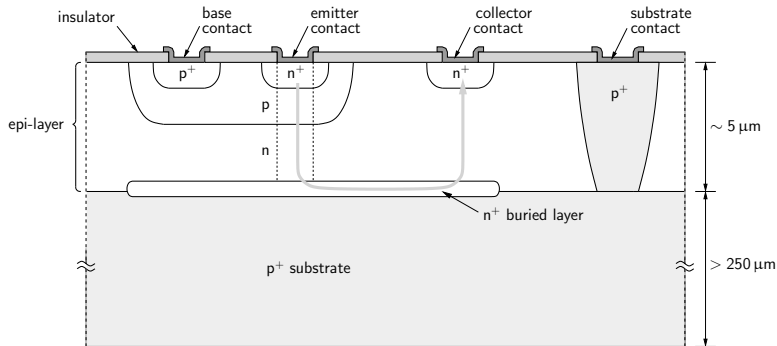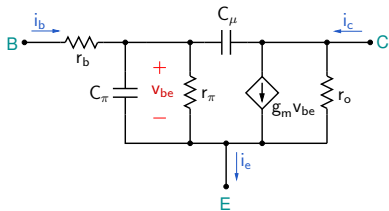

- * A few other components are required to make the small-signal model complete:


r_b : base spreading resistance

C_π : base charging capacitance + B-E junction capacitance

C_μ : B-C junction capacitance

- * The capacitances are typically in the pF range. At low frequencies, $1/\omega C$ is large, and the capacitances can be replaced by open circuits.

BJT: small-signal model

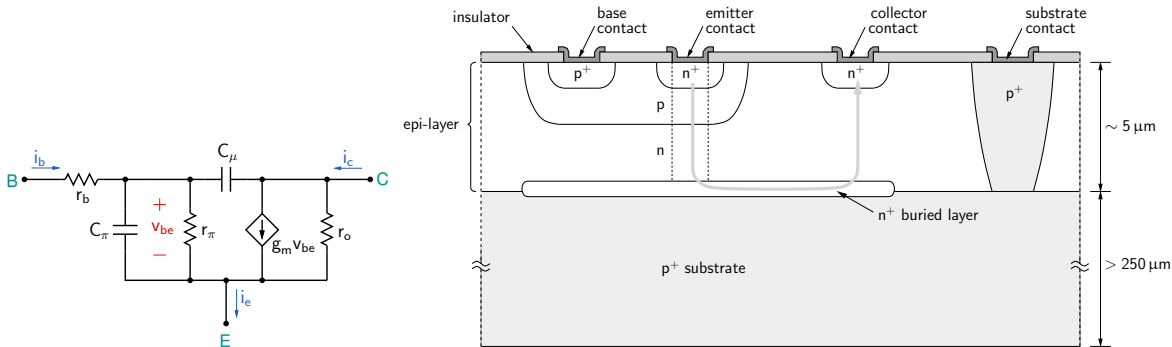

- * A few other components are required to make the small-signal model complete:
 - r_b : base spreading resistance
 - C_π : base charging capacitance + B-E junction capacitance
 - C_μ : B-C junction capacitance
- * The capacitances are typically in the pF range. At low frequencies, $1/\omega C$ is large, and the capacitances can be replaced by open circuits.
- * Note that the small-signal models we have described are valid in the active region only.