

EE240: Power Engineering LAB

Open Circuit and Short Circuit Tests on Single Phase Transformer

Instructor
Prof. B. G. Fernandes

2/2/2021, Tuesday



TRANSFORMERS

An important device used in power transmission, electronic circuits & communication systems.

⇒ consists of a magnetic circuit in which a time varying ' ϕ ' lines link two or more coils

⇒ coupling can be air → air core transformer

Iron → iron core transformer

core is made up of laminations to ↓ core loss

Purpose : Transfer electric energy from one circuit to another



No electrical connection between two circuits.

⇒ Electrically isolated

Principle of Operation:

⇒ magnetic circuit in which time varying flux links two or more coils



winding connected to source → Primary

winding connected to load → Secondary

Primary when connected to alternating source & secondary is open

⇒ no current in secondary

⇒ AT produced by secondary = 0

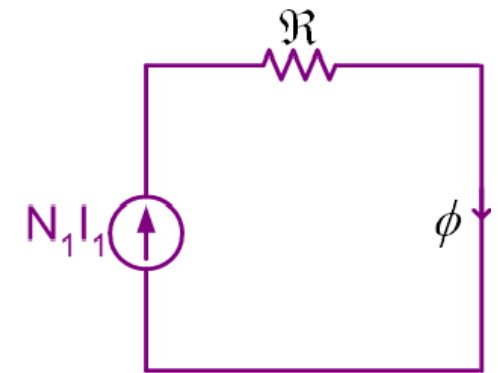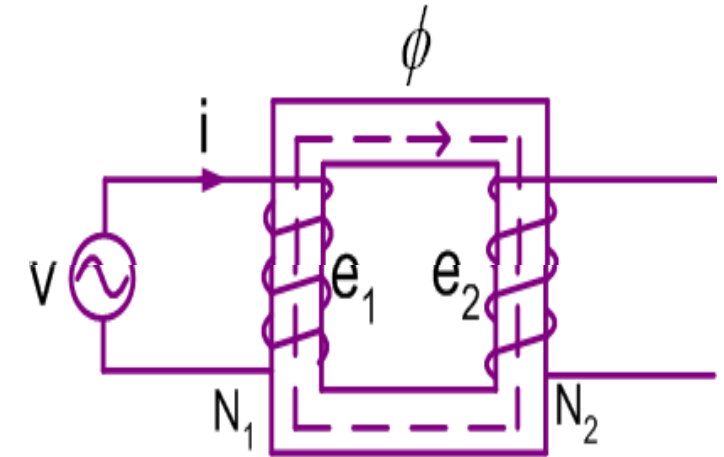

- ⇒ AT supplied is just sufficient to establish ' ϕ ' in the core
- ⇒ If core is highly permeable, this AT is small
(how small is this small?)
- ⇒ since ' ϕ ' is alternating ⇒ core loss
- ⇒ source has to supply some power
- ⇒ for the present we will neglect
- ⇒ Time varying ' ϕ ' links N_1 turns & voltage (e_1/E_1) is induced

$$E_1 = 4.44f\phi_m N_1$$

$\phi_m \rightarrow$ peak value of ' ϕ '

$$E_1 = V_1$$

- ⇒ same ϕ links the secondary



$\Rightarrow e_2 / E_2$ is the voltage induced in N_2

$$E_2 = 4.44 f \phi_m N_2$$

$\Rightarrow E_2$ & E_1 are in phase

$$\therefore \frac{E_2}{E_1} = \frac{N_2}{N_1}$$



If $N_2 > N_1 \Rightarrow$ Step up transformer

$N_2 < N_1 \Rightarrow$ Step down transformer

Connect the load to secondary

i_2 will flow

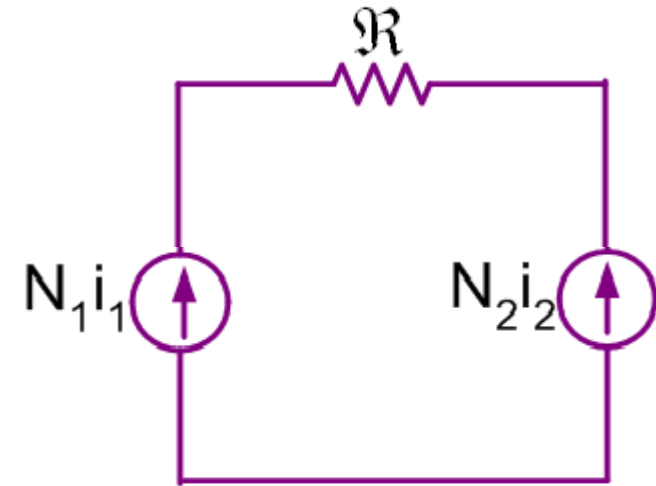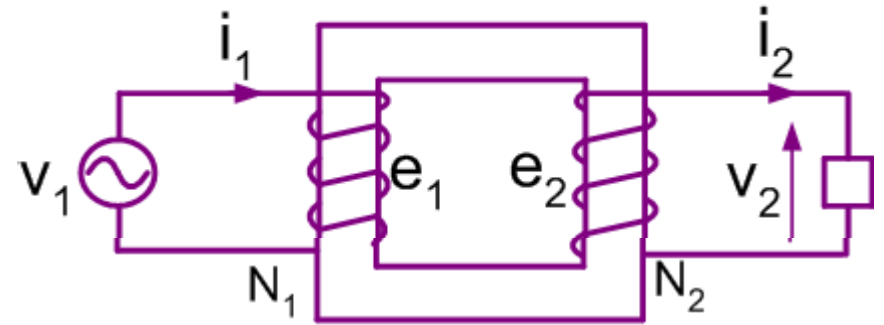\Rightarrow which sets up its own flux, ϕ_2



⇒ This ϕ_2 opposes the parent ' ϕ '

⇒ flux in the core tends to ↓

⇒ E_1 tends to ↓

∴ V_1 is held constant

$V_1 = E_1$ & ∴ ' ϕ ' in the core should remain constant

⇒ can happen when $i_1 \uparrow$ such that

$$N_1 I_1 - N_2 I_2 = \mathcal{R} \phi$$

⇒ ' ϕ ' in the core is determined by V_1 alone



Theory of Ideal Transformer

winding 'r' & leakage 'ϕ' are neglected


$$V_1 = E_1 \text{ \& \> } V_2 = E_2$$

$$\mu_r = \infty \quad \therefore \mathfrak{R} = 0 \quad \therefore \text{AT required to establish } \phi = 0$$

$$N_1 I_1 - N_2 I_2 = 0 \quad \therefore \frac{E_1}{E_2} = \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1} = a$$

$$\therefore V_1 I_1 = V_2 I_2 \Rightarrow \text{Input VA} = \text{Output VA}$$
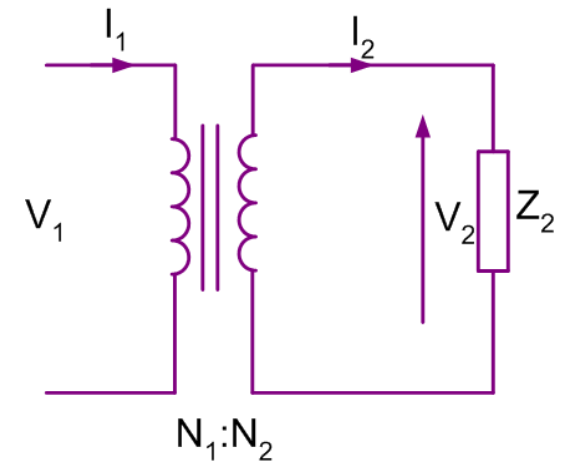
$$Z_2 = \frac{V_2}{I_2} \quad Z_1 = \frac{V_1}{I_1} = \frac{a V_2}{\frac{I_2}{a}} = a^2 \frac{V_2}{I_2} = a^2 Z_2$$



∴ Equivalent 'Z' on the primary side = $a^2 Z_2$

∴ An impedance Z_2 connected in the secondary can be transferred to the primary

∴ Eq. Secondary Z referred to the primary, $Z'_2 = a^2 Z_2$

⇒ If 'Z₁' is the primary impedance, the equivalent primary 'Z' referred to the secondary,

$$Z'_1 = \frac{Z_1}{a^2}$$

⇒ In an ideal transformer 'V' are transformed in the direct ratio, 'I' in the inverse ratio & Z/R/X in the square of the ratio

⇒ P/ S (VI) remain the same



Practical Transformer

⇒ winding 'r', leakage ϕ & core loss are present

$$\mu_r \infty \neq \therefore \mathcal{R} \text{ of the core} \neq 0$$

⇒ Source has to supply AT to establish ' ϕ ' in the core


Eq. Circuit Representation:

$$e_1 \neq v_1 \text{ \& } e_2 \neq v_2$$

r_1 & r_2 are primary & secondary resistances respectively

⇒ Total flux in the primary winding = $\phi_{l1} + \phi$

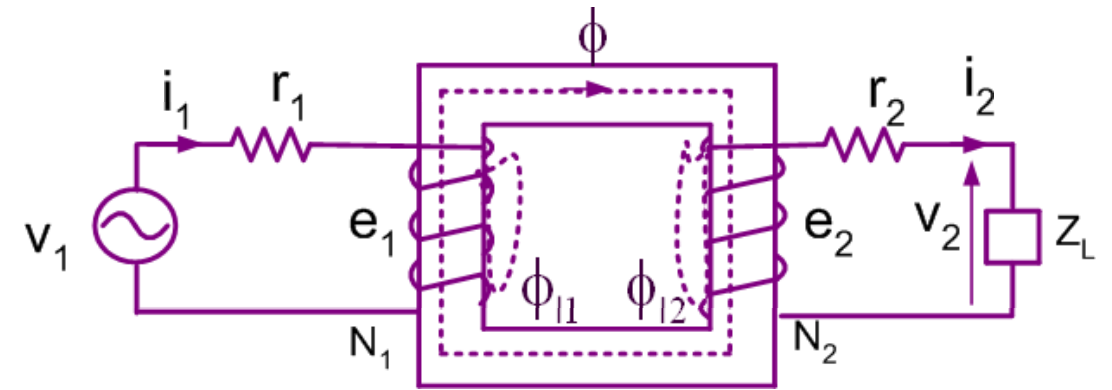⇒ Total flux in the secondary winding = $\phi_{l2} + \phi$



\therefore iron core is used $\phi_{l1} \ll \phi$


\Rightarrow represent leakage flux by leakage inductance/reactance

X_{l1} in the primary ($2\pi fL_1$), $L_1 \rightarrow$ corresponds to leakage flux in primary

X_{l2} in the secondary ($2\pi fL_2$), $L_2 \rightarrow$ corresponds to leakage flux in secondary

\Rightarrow we need to account for only mutual flux or flux in the core

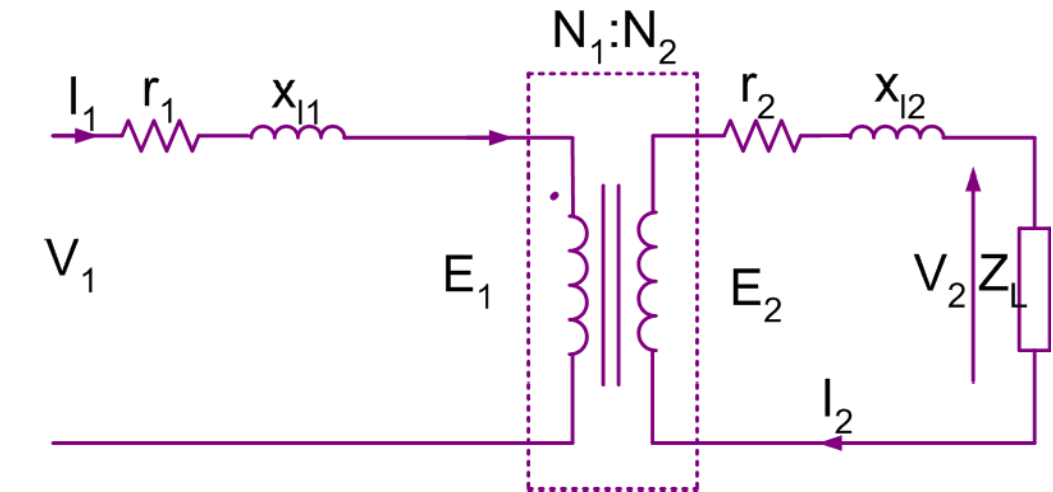
\Rightarrow This flux links primary and secondary coils




tightly coupled coils, $K=1$



∴ Equivalent Circuit:

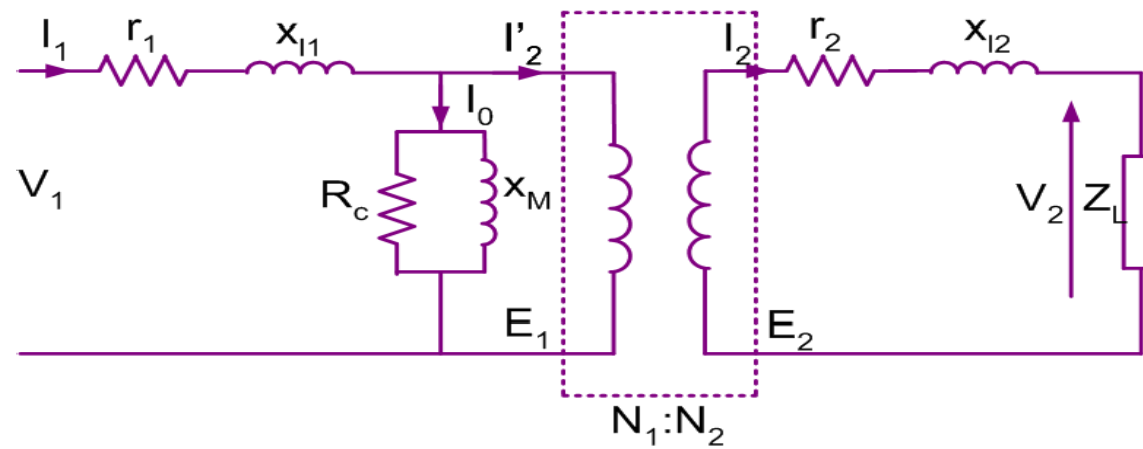

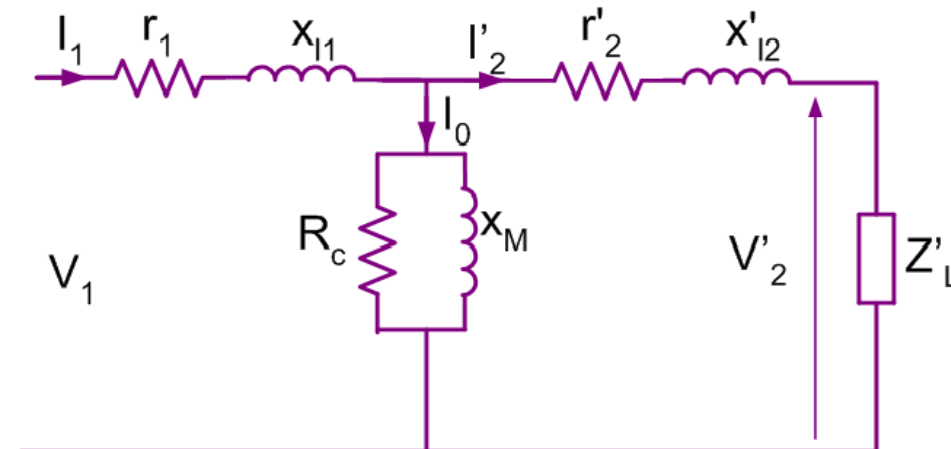Equivalent Circuit referred on primary side:




$$r_2' = r_2 \left(\frac{N_1}{N_2} \right)^2 \quad X_{l2}' = X_{l2} \left(\frac{N_1}{N_2} \right)^2$$

$$V_2' = V_2 \left(\frac{N_1}{N_2} \right) \quad I_2' = I_2 \left(\frac{N_1}{N_2} \right)$$




- ⇒ core has finite permeability
- ⇒ finite ATs are required to establish ' ϕ ' in the core
- ⇒ can be represented by magnetizing reactance, $X_M = 2\pi fL$
- ⇒ since ϕ in the core is alternating, there would be core loss, $I_C^2 R_C$

$$I_0 = I_C + I_m$$

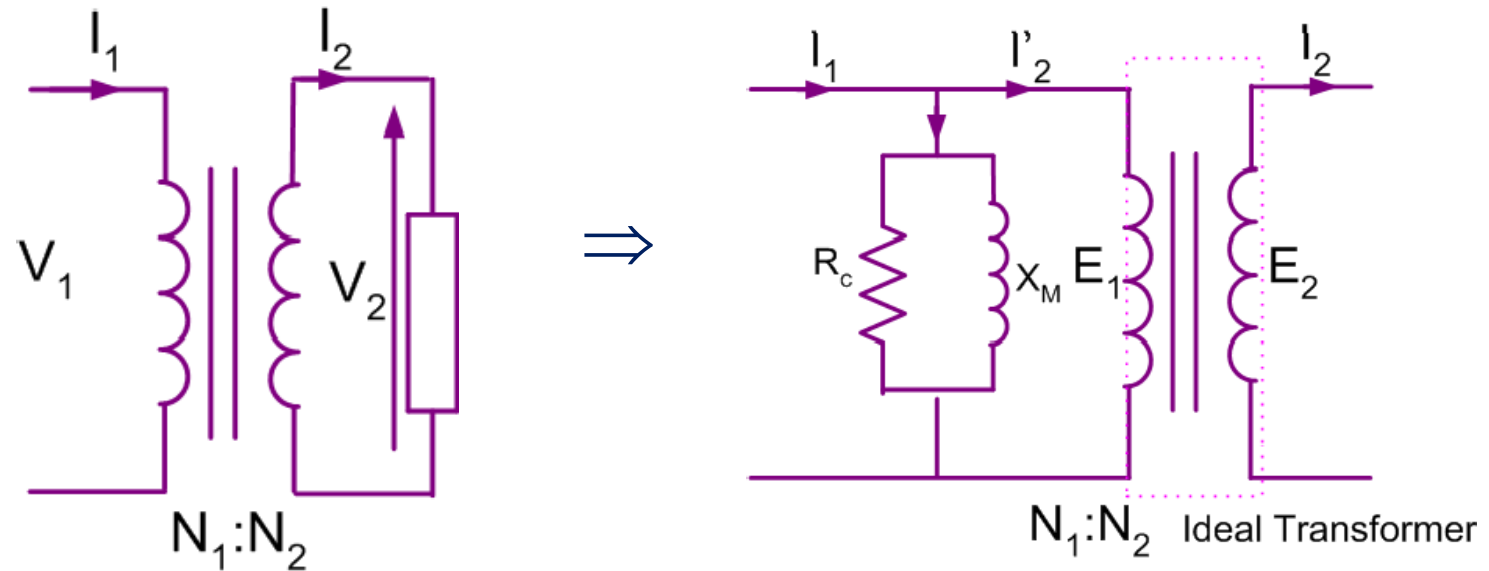


⇒ Secondary terminal 'V' changes with load

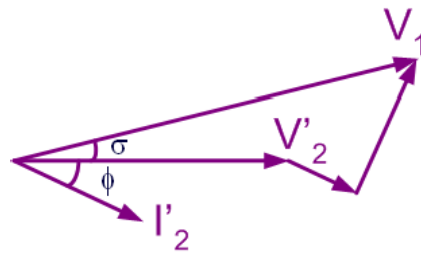
⇒ This change depends on load P.F., R_{eq} & X_{eq}




lagging P.F.

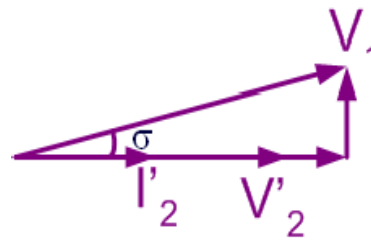

unity P.F.

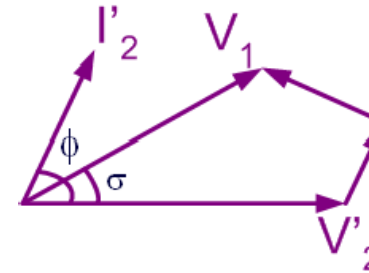

leading P.F.

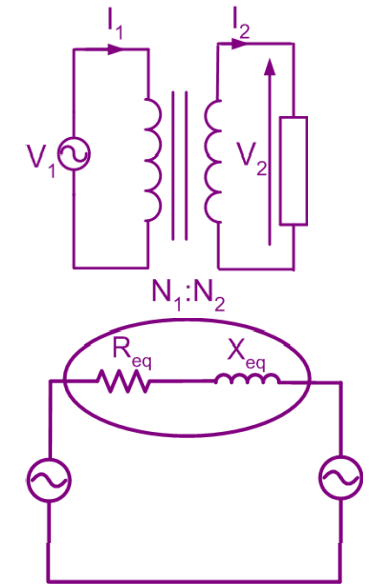

⇒ This change can be estimated if R_{eq} & X_{eq} are known



⇒ conduct S.C. test to determine these parameters

⇒ 'V' required to circulate the rated 'I' on S.C.
is a small percentage of rated V.

∴ reduced 'V' is applied to the transformer, core loss can be neglected

$$\therefore P_{\text{in}} \text{ on S.C.} = I^2 R_{\text{eq}}$$

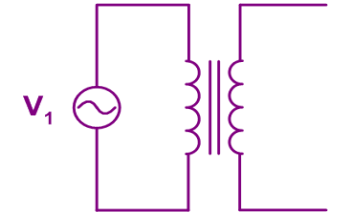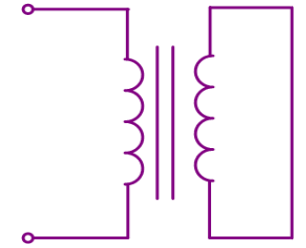⇒ shunt parameters are determined by conducting O.C. test



No load/Open Circuit Test

If power(core loss), V & I are measured, R_c & X_M can be determined


⇒ what ' V ' to apply ?

⇒ core loss depends on ' ϕ ' & \therefore ' V '

⇒ load on the transformer is an independent variable

⇒ utilities ensure that almost constant ' V ' is applied to the transformer terminals

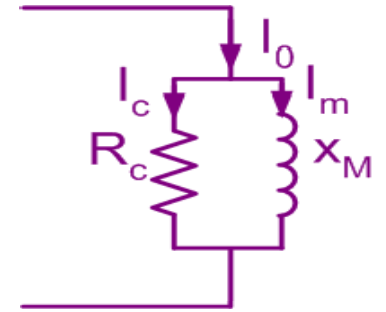⇒ apply rated ' V ' to one of the winding and measure the ' I ' drawn and ' P ' consumed



⇒ power input on no load is assumed to be dissipated in the core (core loss + $I_0 r_1$)

⇒ which side is to be kept open?

LV side or HV side?

Test condition: apply rated 'V'


⇒ Keep HV open

how to determine R_{eq} & X_{eq} ?

$$R_{eq} = r_1 + r'_2, \quad X_{eq} = x_{l1} + x'_{l2}$$

⇒ these elements come in the path of main power flow


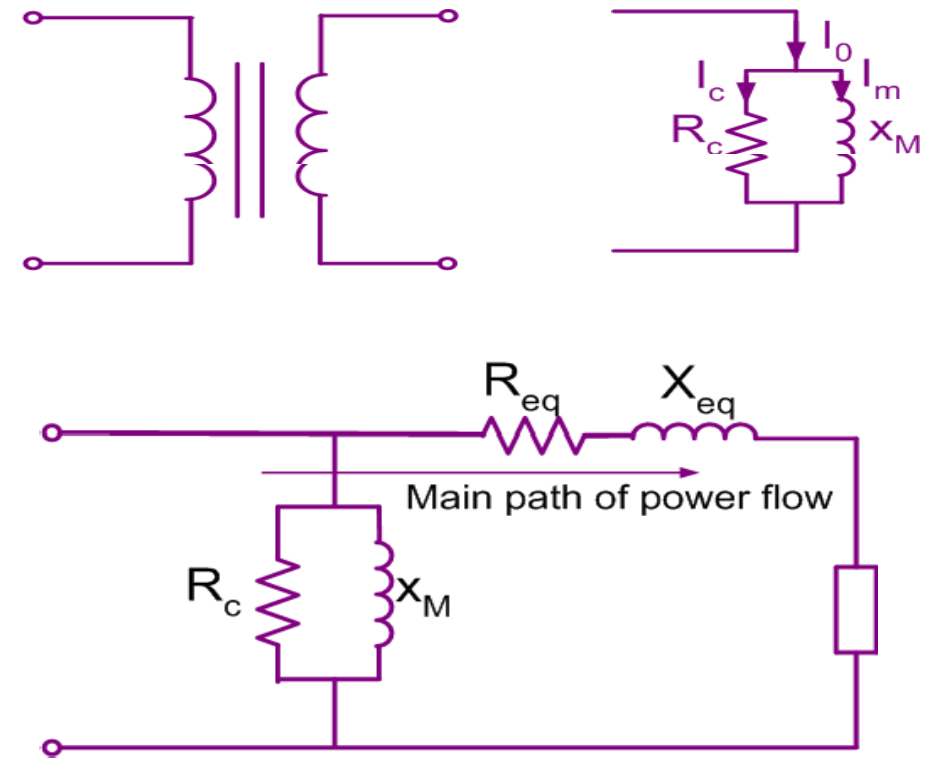
⇒ should be very small compared to shunt branch parameters



Short Circuit Test

- apply reduced V such that rated ' I ' flows in the winding. (not a necessary condition)
- V_{sc} is the applied ' V ', I_{sc} current flow & ' W ' power supplied
- magnitude of ' V ' is $\cong 10\%$ of rated V
- under this condition ' ϕ ' in the core $\cong 10\%$ of rated ' ϕ '

\Rightarrow neglect core loss

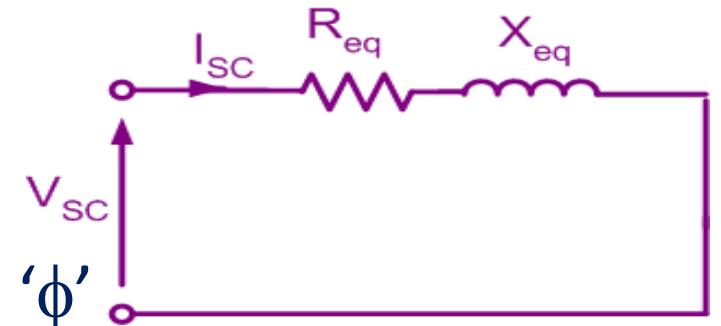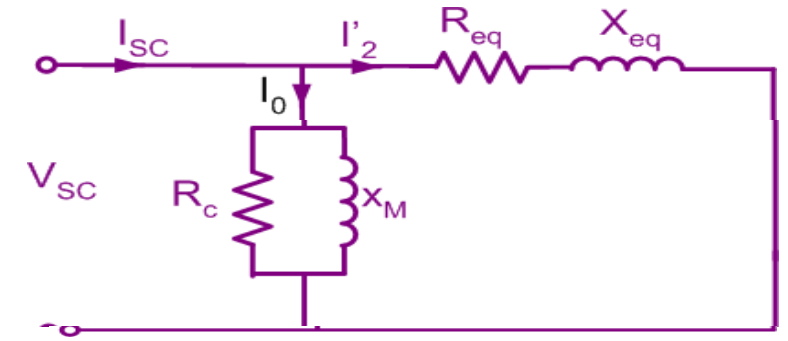

$$I_{sc}^2 R_{eq} = W \quad \therefore R_{eq} = \frac{W}{I_{sc}^2} \quad \frac{V_{sc}}{I_{sc}} = Z_{sc} \quad \therefore X_{eq} = \sqrt{Z_{sc}^2 - R_{eq}^2}$$



Efficiency: Static device

- core loss/iron loss/constant loss
- I^2R loss \Rightarrow cu.loss $R \rightarrow$ winding resistance
- 'I' depends on load & load is an independent variable
- as load changes, 'I' & \therefore cu.loss will change


\Rightarrow variable loss

\Rightarrow on no load $Z_L = \infty$, $I'_2 = 0$ or $I_2 = 0$ as load \uparrow , $Z_L \downarrow$

$$\therefore \% \eta = \frac{\text{o/p power}}{\text{i/p power}} * 100$$

if $S = \text{VA rating of the transformer}$, load P.F is $\cos \phi$,

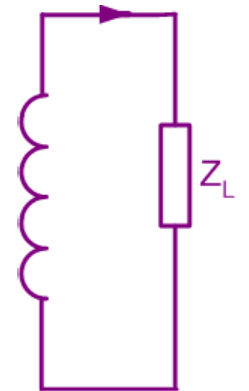$P_i \rightarrow$ iron loss & $P_c \rightarrow$ cu. loss on full load



let 'x' be the fraction of load the transformer is supplying

power output = $x S \cos\phi$

cu loss when the load is x, $P_{CX} = x^2 P_C$

on full load cu. loss, $P_C = I_{\text{rated}}^2 R_{\text{eq}}$

on 1/2 load ($x = 0.5$), $I_2 = 0.5 I_{\text{rated}}$

\therefore cu. loss(at $x = 0.5$) = $(0.5)^2 I_{\text{rated}}^2 R_{\text{eq}} = x^2 P_C$


$$\% \eta = \frac{x * S * \cos(\phi)}{x * S * \cos(\phi) + P_i + P_C * x^2} \times 100$$

1. η is function of load P.F.

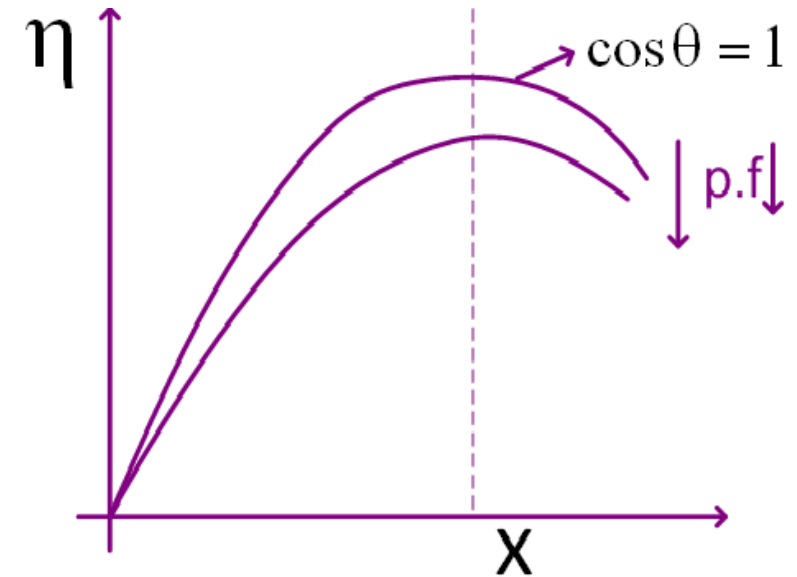2. $\eta = \eta_{\text{max}}$ when $\frac{d\eta}{dx} = 0 \Rightarrow x^2 P_C = P_i \quad \therefore x = \sqrt{\frac{P_i}{P_C}}$


\Rightarrow 'x' at which $\eta = \eta_{\text{max}}$ is independent of $\cos\phi$ but value of this η depends on $\cos\phi$

\Rightarrow generally 'η' is almost a flat curve




Utilities try to maintain \cong constant 'V' at primary terminals

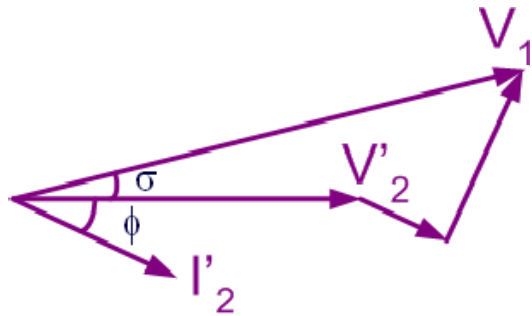
\Rightarrow depending upon the load, secondary terminal 'V' would change



lagging P.F.

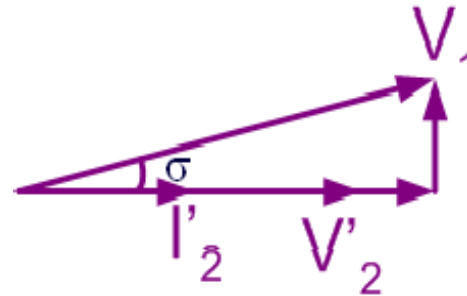

unity P.F.

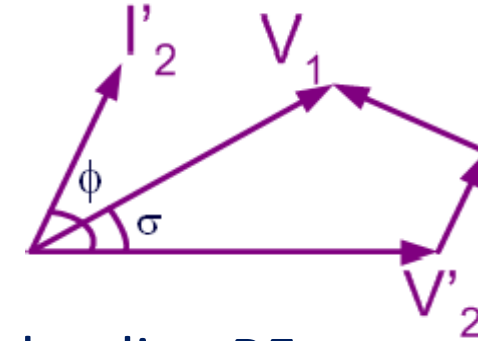

leading P.F.

\Rightarrow this change depends on R_{eq} & X_{eq}

\Rightarrow transformer is expected to maintain almost constant 'V' & it should be independent of I_2

$\Rightarrow Z_{eq} = (R_{eq} + jX_{eq}) \rightarrow 0$



Voltage Regulation

⇒ performance index deals with secondary voltage as a function of load 'I' known as regulation

Regulation: The change in secondary voltage expressed in % of rated secondary voltage which occurs when the load at specified power factor is reduced to zero, with primary 'V' maintained constant


$$\% \epsilon = \frac{V_{2(\text{no load})} - V_{2(\text{rated load})}}{V_{2(\text{no load})}} \times 100$$

V_1 - rated primary voltage,

V_2 - rated secondary voltage

$$\epsilon = \frac{V_2 - V_{2L}}{V_2} = \frac{\frac{V_1}{a} - V_{2L}}{\frac{V_1}{a}} = \frac{V_1 - aV_{2L}}{V_1} = \frac{V_1 - V'_2}{V_1}$$

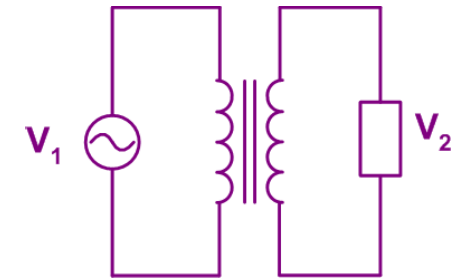
V_{2L} - secondary voltage under load condition




To determine regulation, we assume that V_1 & V'_2 are in phase & $I_1 \cong I'_2$

$$\therefore \frac{V_1 - V'_2}{V_1} = \frac{I_1 R_{eq} \cos(\phi) \pm I_1 X_{eq} \sin(\phi)}{V_1} = \varepsilon_r \cos(\phi) \pm \varepsilon_x \sin(\phi)$$

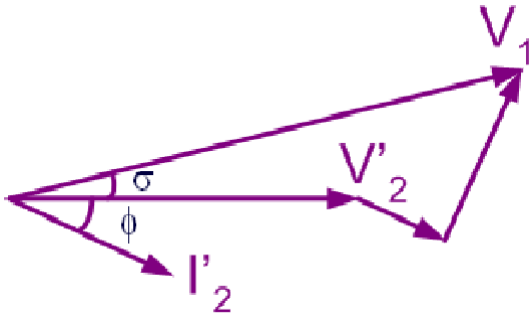
+ \rightarrow lagging P.F., - \rightarrow leading P.F.



lagging P.F.

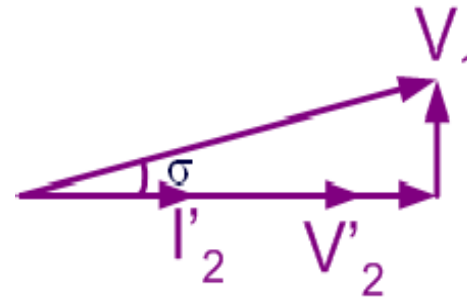

unity P.F.

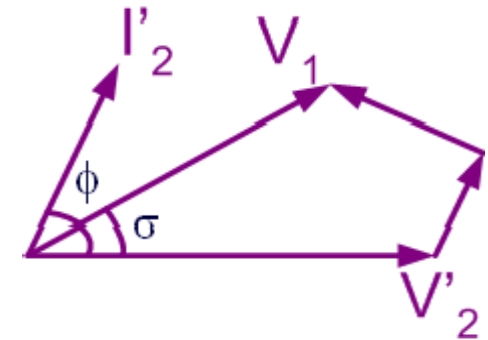

leading P.F.

% ε is always + ve for R & R-L loads

% ε could be +, 0 or - ve for R-C loads



$$\varepsilon = 0 = \varepsilon_r \cos(\phi) - \varepsilon_x \sin(\phi)$$

$$\therefore \tan(\phi) = \frac{\varepsilon_r}{\varepsilon_x} = \frac{R_{eq}}{X_{eq}}$$




$V_1 - V'_2 \rightarrow$ depends on mainly
on X_{eq} $R_{eq} \rightarrow$ low

If X_{eq} is reduced, regulation improves

\Rightarrow In case, if there is an accidental short circuit, I_{sc} is limited by leakage

\Rightarrow To protect, I_{sc} should be limited

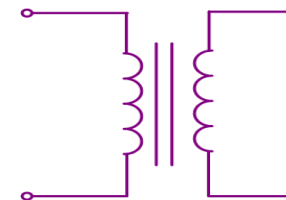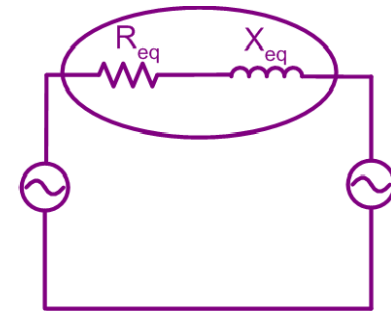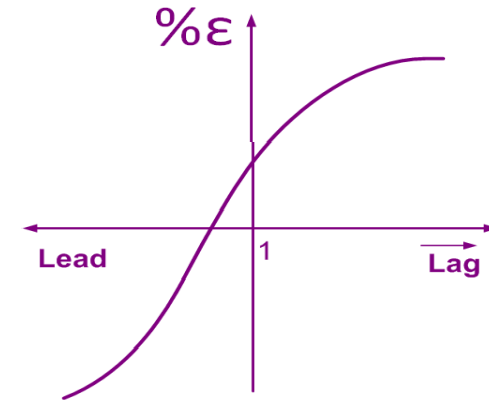\Rightarrow Law of conservation of sorrows: “Sorrows can neither be created nor destroyed”



Three phase transformer

Phase 'V' in the $\Delta = V$

\Rightarrow Induced phase 'V' in the Y = V


\therefore L-L V in the Y = $\sqrt{3}V$

what about the phasor relationship
between line 'V' in Δ & Y ?

$\Rightarrow V_L$ in Δ & V_{ph} in Y are in phase (E_1 & E_2
are in phase)


$\Rightarrow V_L$ leads V_{ph} by 30° in Y connection

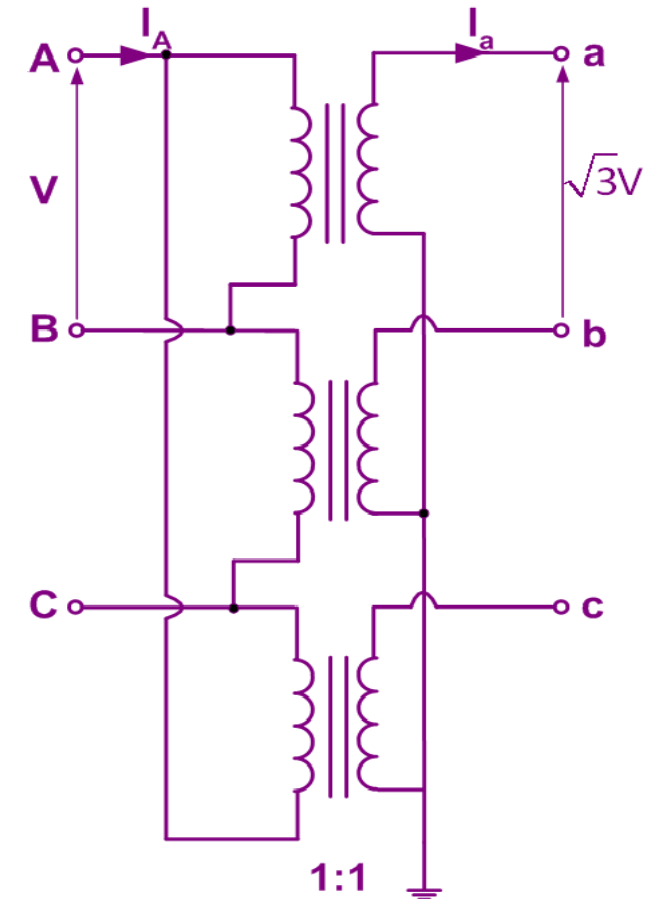\therefore There is 30° phase shift between V_L in Δ & Y




how to connect 3- ϕ , 3 wire system to 3- ϕ , 4 wire system ?

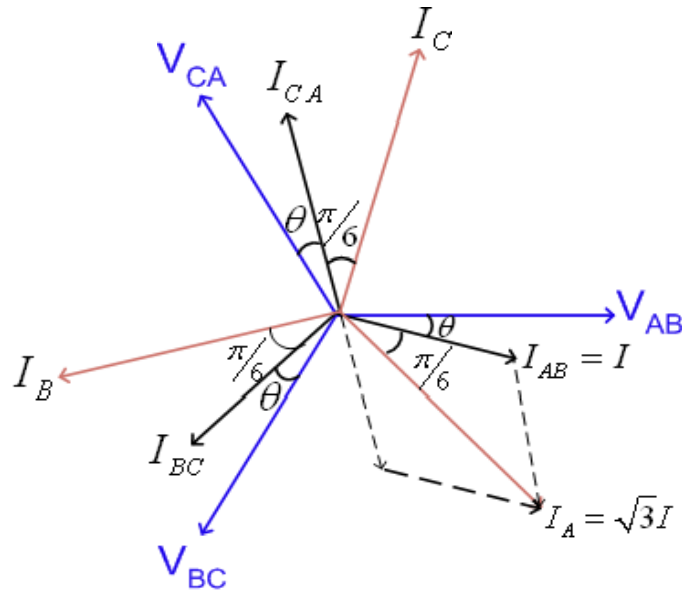
\Rightarrow use Y - Δ connection and ground the star point



Phasor for delta connection

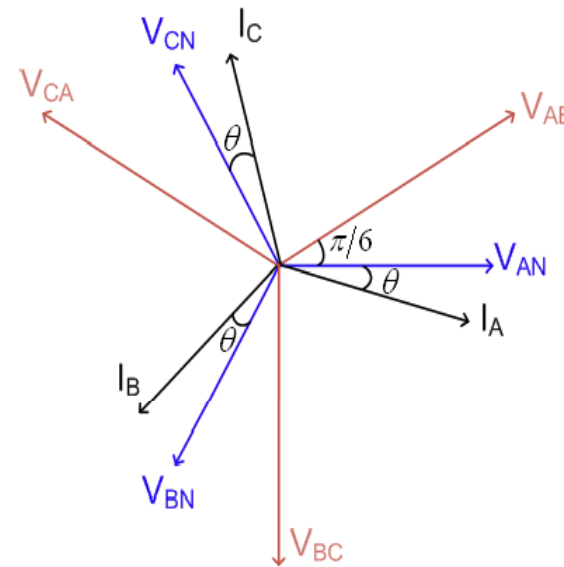

Phasor for Y connection

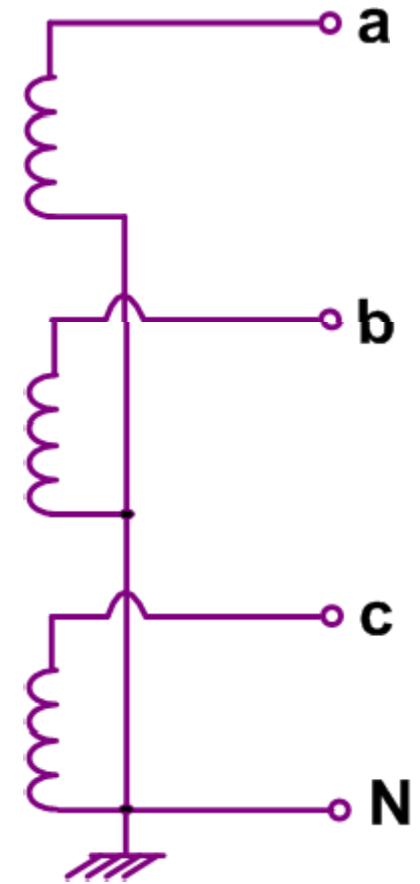

Single Phase Transformer Used for Experiment

