

EE240: Power Engineering LAB

Power measurement in balanced 3 phase circuit and power factor improvement

Instructor

Prof. B. G. Fernandes

19/1/2021, Tuesday




Power in 1- ϕ circuit:

Let $v = \sqrt{2}V \sin(\omega t)$

$\bar{V} = V \angle 0$ is the applied voltage &
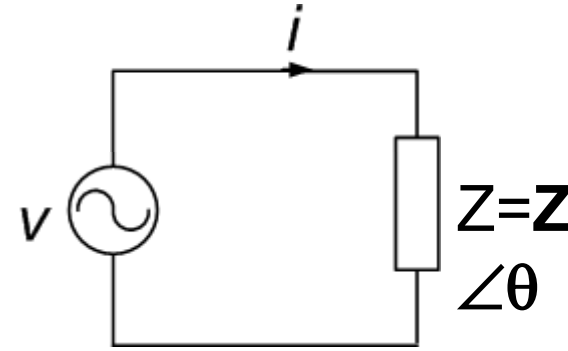
$$i = \frac{v}{Z} = \sqrt{2}I \sin(\omega t - \theta), \quad \bar{I} = \frac{\bar{V}}{Z} \angle -\theta = I e^{-j\theta}$$



Instantaneous power delivered to the load,

$$p = vi$$

$$= 2VI \sin \omega t \sin(\omega t - \theta)$$

$$= VI [\cos \theta - \cos(2\omega t - \theta)]$$

↓
constant term

↪ alternating at twice the supply F

$$= VI \cos \theta - VI \cos \theta \cos 2\omega t - VI \sin \theta \sin 2\omega t$$



∴ Average power, $P = VI \cos \theta$ W

$$\cos \theta = \frac{P}{VI}$$

⇒ $\theta = 0$, load = R, 'p' is always +ve


⇒ $\theta \neq 0$, instantaneous power is negative, even though load is passive

⇒ Energy stored in L/C is returned back to source

⇒ 'p' pulsates at 2f. Load may experience vibration

⇒ Requires resilient mountings



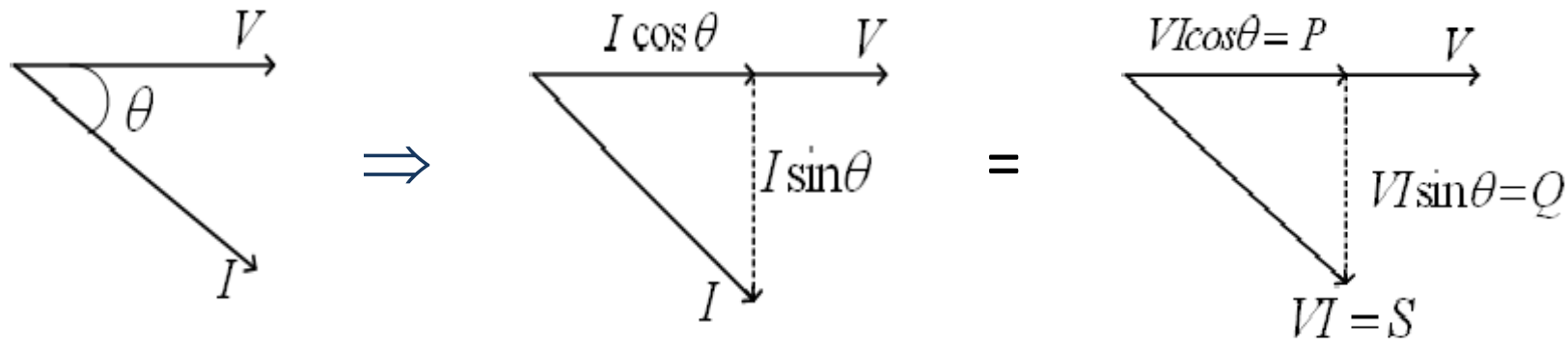


Complex power: $S = P + jQ$

↳ Dimensions same as P & Q
 \Rightarrow VA (Volt-Ampere)


$$S = VI \cos \theta + jVI \sin \theta$$

$$= VI e^{j\theta} = VI^*$$

Inductive circuit: Source supplies 'Q'

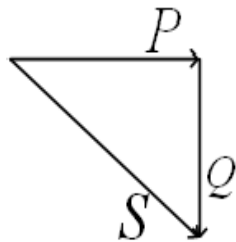


Capacitive circuit: Source receives 'Q'

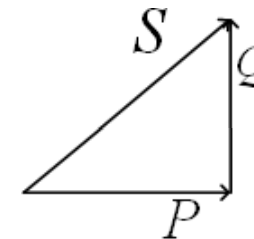

Three Phase AC Circuits

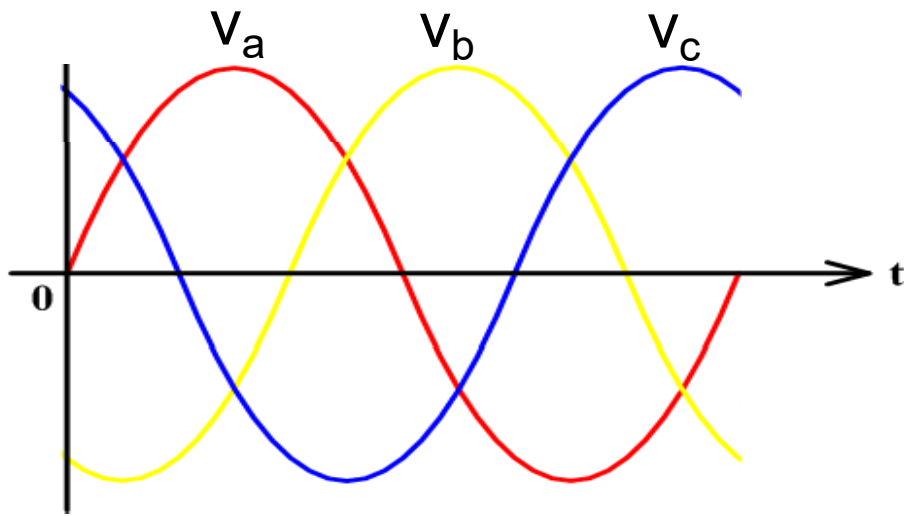- ⇒ Generation, Transmission, Distribution & utilization of large blocks of power are accomplished by means of 3- \emptyset circuits.
- ⇒ 1- \emptyset supply is generated from 3- \emptyset supply.
- ⇒ A balanced 3- \emptyset system consists of 3 single phase voltages having same amplitude & f , but out of phase with each other by 120° .






⇒ 'v' in coil AA' reaches peak followed by BB' & CC'

⇒ Phase relationship is ABC ⇒

⇒ Also known as 'phase sequence'

⇒ phase relationship is ACB ⇒

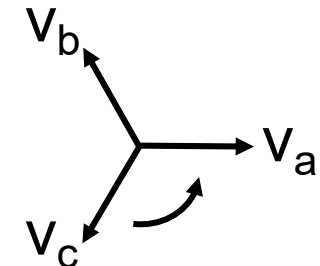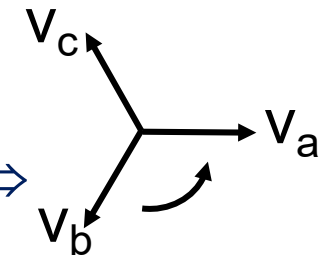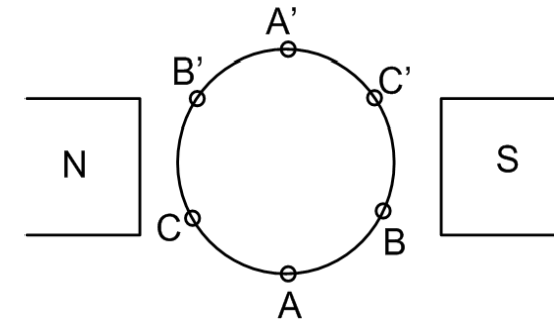

$$v_{aa'} = \sqrt{2}V \sin \omega t$$

$$\bar{V}_{aa'} = V \angle 0 = \bar{V}_a$$

$$v_{bb'} = \sqrt{2}V \sin(\omega t - \frac{2\pi}{3}) \quad \bar{V}_{bb'} = V \angle -\frac{2\pi}{3} = \bar{V}_b$$

$$v_{cc'} = \sqrt{2}V \sin(\omega t - \frac{4\pi}{3}) \quad \bar{V}_{cc'} = V \angle -\frac{4\pi}{3} = \bar{V}_c$$

$$v_{aa} + v_{bb} + v_{cc} = 0 \text{ or } \bar{V}_a + \bar{V}_b + \bar{V}_c = 0$$

⇒ In balanced 3-phase system, sum of three phase voltages is zero



Three Phase connection

Y Connection:



⇒ Potential difference between any line and common point (also known as neutral) known as phase voltage

$$\bar{V}_{an}, \bar{V}_{bn} \text{ \& } \bar{V}_{cn}$$

⇒ Potential difference between any two lines = Line voltage or line-line voltage

$$\begin{aligned}\bar{V}_{AB} &= \text{pot. of } A \text{ w.r.t } B \\ &= -V_{bn} + V_{an} = V_{an} - V_{bn}\end{aligned}$$
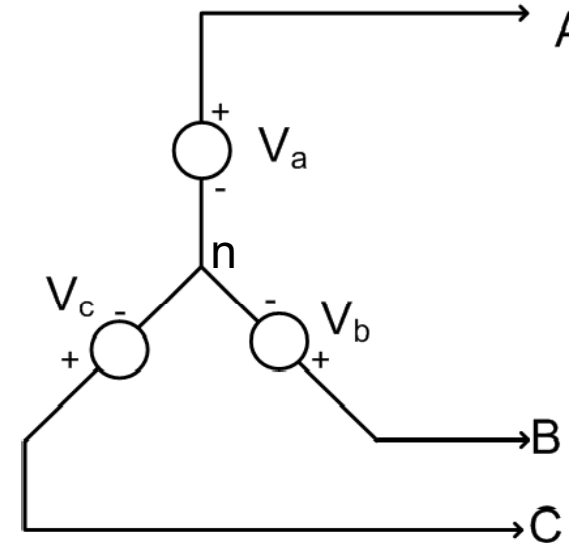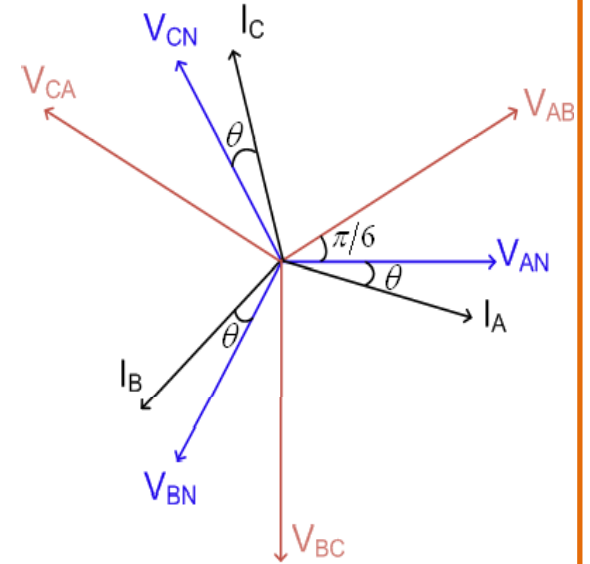
$$V_{BC} = V_{bn} + V_{nc}, \quad V_{CA} = V_{cn} + V_{na}$$



Y connected load -Balanced Load:

Magnitude & phase angle are the same in all 3 phases



Assume ABC phase sequence

and $V_{AN} = V \angle 0$ as the reference phasor

$$\therefore V_{AN} = V \angle 0$$

$$V_{BN} = V \angle \frac{-2\pi}{3}$$

$$V_{CN} = V \angle \frac{-4\pi}{3}$$

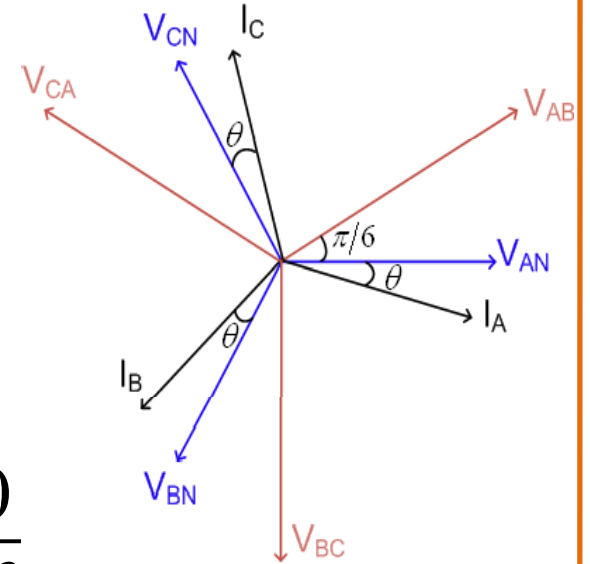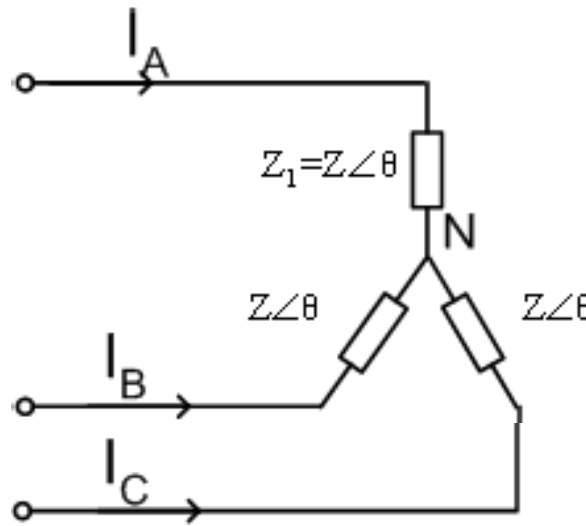

$$\bar{I}_A = \frac{\bar{V}_{AN}}{Z_A} = \frac{V \angle 0}{Z \angle \theta}$$

$$\bar{I}_B = \frac{\bar{V}_{BN}}{Z_B} = I \angle -\left(\frac{2\pi}{3} + \theta\right)$$

$$\bar{I}_C = \frac{\bar{V}_{CN}}{Z_C} = I \angle -\left(\frac{4}{3} + \theta\right)$$

\Rightarrow Line 'I' = Phase 'I'



Δ -Connection:

Line V = Phase V

Assume, $V_{AB} = V \angle 0$,




$V_{BC} = V \angle -2\pi/3$, $V_{CA} = V \angle -4\pi/3$

Load connection:

$$\bar{I}_{AB} = \frac{\bar{V}_{AB}}{Z_{AB}} = \frac{V \angle 0}{Z \angle \theta} = I \angle -\theta$$

$$\bar{I}_{BC} = \frac{\bar{V}_{BC}}{Z_{BC}} = I \angle -\left(\frac{2\pi}{3} + \theta\right)$$
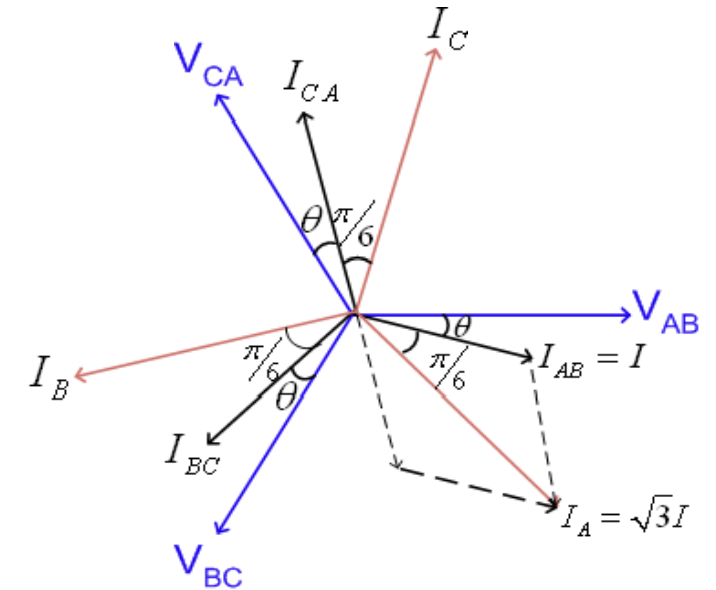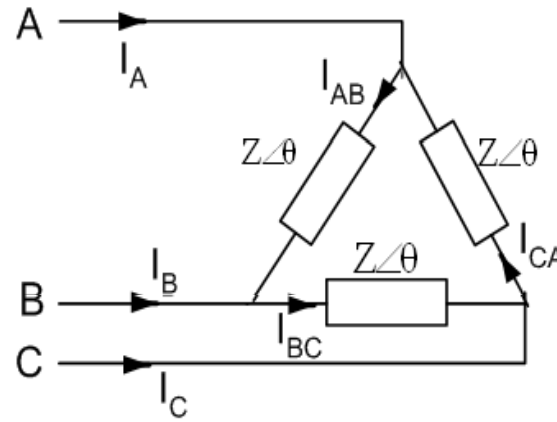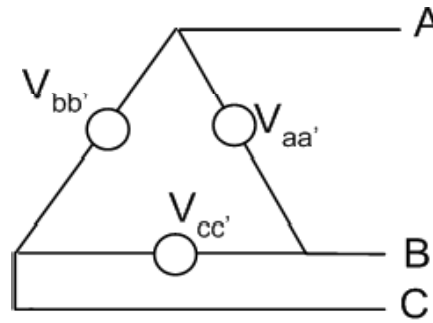
$$\bar{I}_{CA} = \frac{\bar{V}_{CA}}{Z_{CA}} = I \angle -\left(\frac{4\pi}{3} + \theta\right)$$



$$\begin{aligned} \therefore I_A &= I_{AB} - I_{CA} \\ &= I \left[1 \angle -\theta - 1 \angle -\left(\frac{4\pi}{3} + \theta\right) \right] \\ &= \sqrt{3}I \angle -\left(\frac{\pi}{6} + \theta\right) \\ |Line I| &= \sqrt{3} |I_{Phase}| \end{aligned}$$

Line I lags the phase I by $\pi/6$

Power in 3- Φ circuits:

\Rightarrow Recall p in 1 Φ circuits pulsates at $2f$

\therefore 1- Φ motors require special resilient mountings

$$v_a = \sqrt{2}V \sin \omega t, v_b = \sqrt{2}V \sin(\omega t - \frac{2\pi}{3}), v_c = \sqrt{2}V \sin(\omega t - \frac{4\pi}{3})$$

$$i_a = \sqrt{2}I \sin(\omega t - \theta), i_b = \sqrt{2}I \sin(\omega t - \frac{2\pi}{3} - \theta), i_c = \sqrt{2}I \sin(\omega t - \frac{4\pi}{3} - \theta)$$

\therefore Instantaneous power

$$p_a = v_a i_a = VI [\cos \theta - \cos(2\omega t - \theta)]$$

$$p_b = v_b i_b = VI [\cos \theta - \cos(2\omega t - \theta - 240^\circ)]$$

$$p_c = v_c i_c = VI [\cos \theta - \cos(2\omega t - \theta - 480^\circ)]$$



$$\begin{aligned}
 \therefore \text{Total instantaneous 3-}\Phi \text{ power} &= 3VI \cos\theta \\
 &= 3V_{ph}I_{ph}\cos\theta \\
 &= \text{Average power} \\
 &= \text{Constant}
 \end{aligned}$$

$$\theta = \angle \begin{matrix} I_{ph} \\ V_{ph} \end{matrix}$$

If system is 'Y' connected

$$V_{ph} = \frac{V_L}{\sqrt{3}}, \quad I_{ph} = I_L \quad \therefore P = \sqrt{3}V_L I_L \cos\theta$$

If Load is delta connected $V_L = V_{Ph}, \quad I_L = \sqrt{3}I_{Ph}$

$$\therefore P = \sqrt{3} V_L I_L \cos\theta \text{ W}$$

Independent of type of connection

$$\therefore Q = \sqrt{3} V I \sin\theta \text{ VAr} \quad S = \sqrt{3} V I^* \text{ VA}$$




Measurement of Power



⇒ Using wattmeter

⇒ Has 2 coils: — $\begin{cases} \text{Current coil} \\ \text{Voltage coil} \end{cases}$

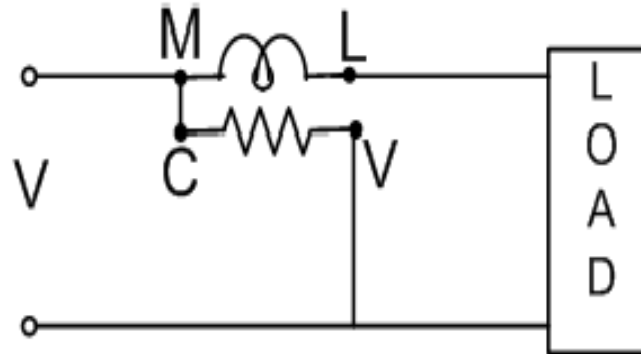M → Mains
L → Load
C → Common
V → Voltage




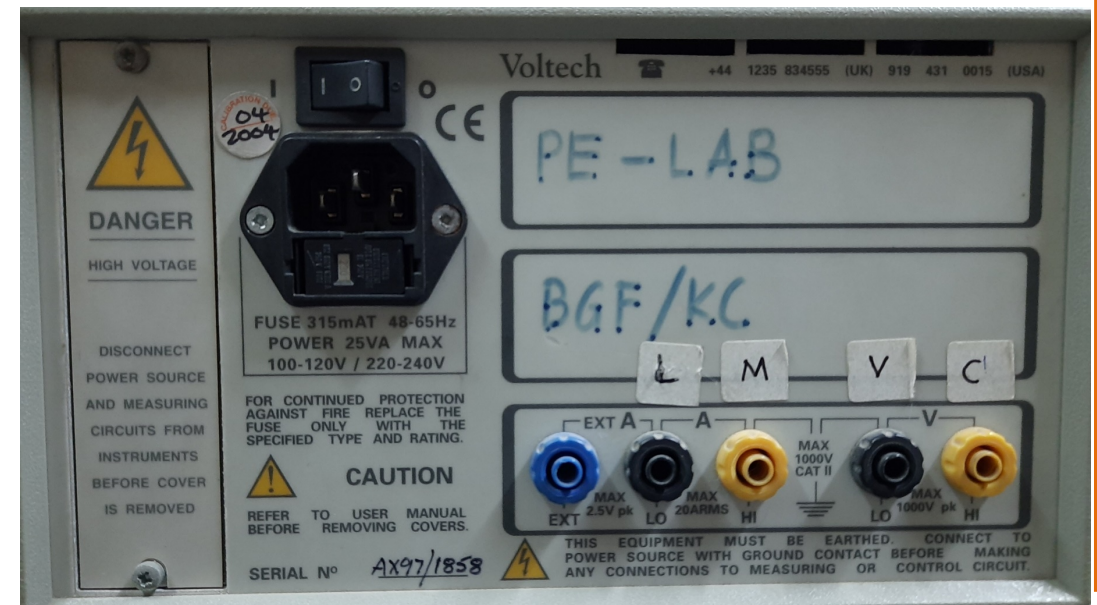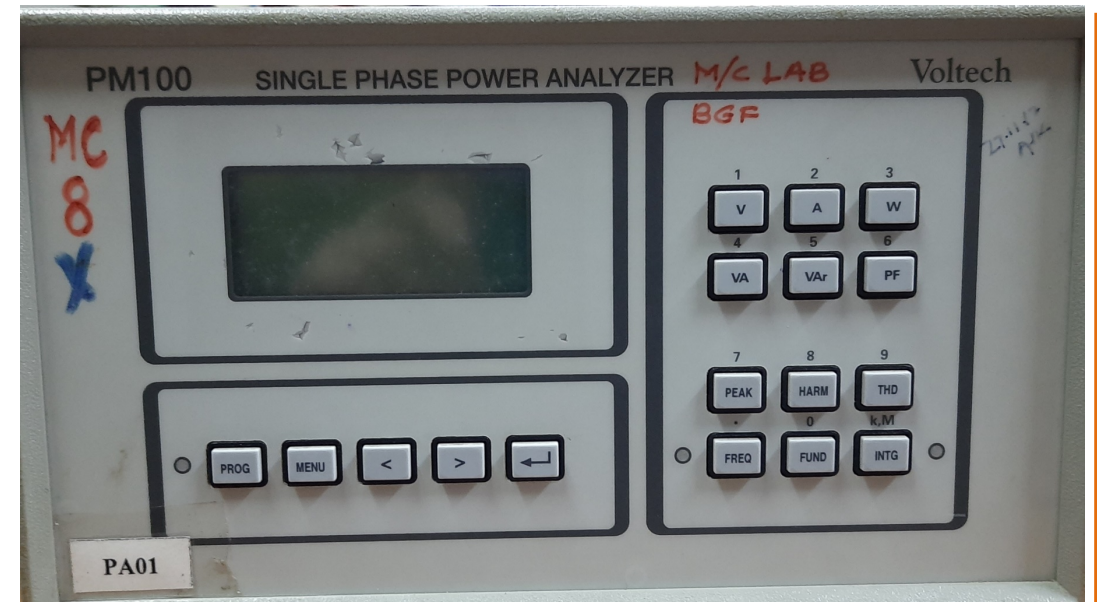
$$\text{'W' reading} = I_{\text{Flowing}} V_{\text{Applied}} \cos \angle \begin{matrix} I_{\text{Flowing}} \\ V_{\text{Applied}} \end{matrix}$$




In case of 3-phase 3 wire load:

Two wattmeter method:

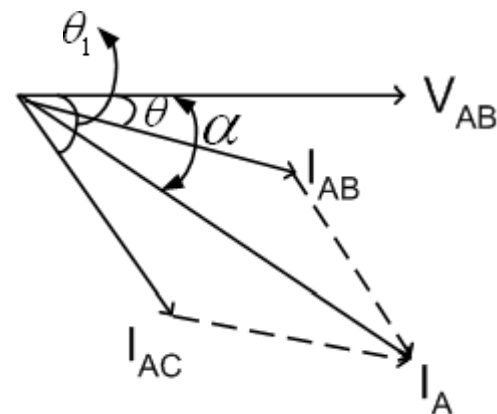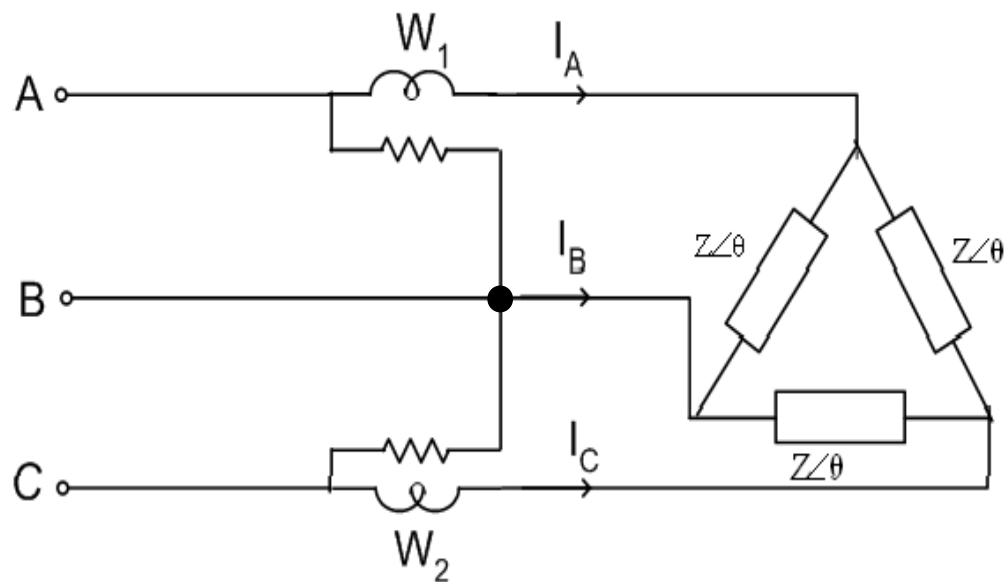

$$W_1 = V_{AB} I_A \cos \alpha$$

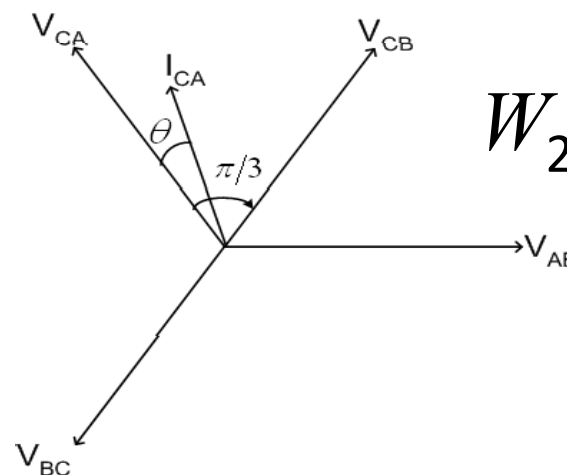

$$W_2 = V_{CB} I_C \cos \angle I_C V_{CB}$$

Observations:

If load is balanced

$$\Rightarrow \sqrt{3} V_L I_L \cos \theta = W_1 + W_2$$

$$\theta = \angle I_{ph} V_{ph}$$

If load is unbalanced

$$W_1 + W_2 = P_A + P_B + P_C \neq \sqrt{3} V_L I_L \cos \theta$$

Power in phase A



$$W_1 = V_{AB} I_A \cos \angle_{V_{AB}}^{I_A}$$

$$= V_L I_L \cos(30 + \theta)$$

$$W_2 = V_{CB} I_C \cos \angle_{V_{CB}}^{I_C}$$



$$= V_L I_L \cos(30 - \theta)$$

If $\theta = 0 \Rightarrow$ Load is 'R', $W_1 = W_2$

If $\theta = \pi/3$, one of the Wattmeter would read zero

\Rightarrow If $\theta > \pi/3$, read -ve
(interchange M & L)
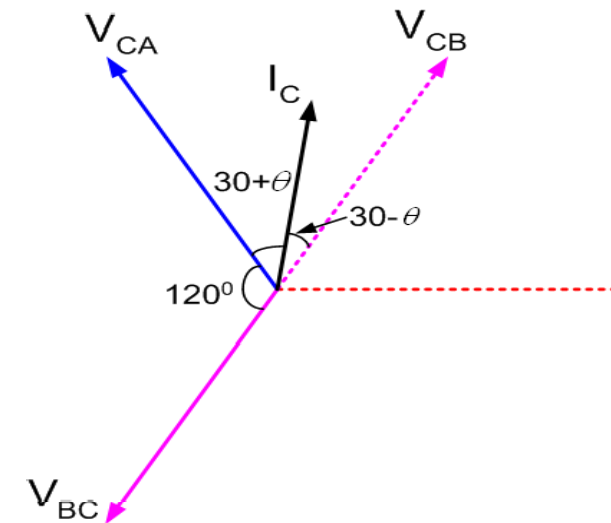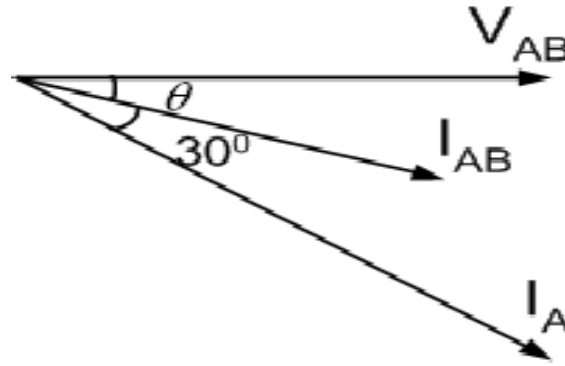
$$\theta = \tan^{-1} \sqrt{3} \left[\frac{W_2 - W_1}{W_1 + W_2} \right]$$



Note: Phase sequence & lines in which they are connected should be known to determine whether θ is +ve or -ve



Concept of Reactive Power

1 kVA, 200V, 50 Hz Generator

⇒ Rated current = 5A

⇒ Assume load = 1 kVAr, 200V


⇒ Current drawn by the load = 5A
= rated current of generator

⇒ Power consumed by the load = 0

Assume generator is ideal (losses = 0)

∴ Input power = o/p power + loss = 0

⇒ No input is required.

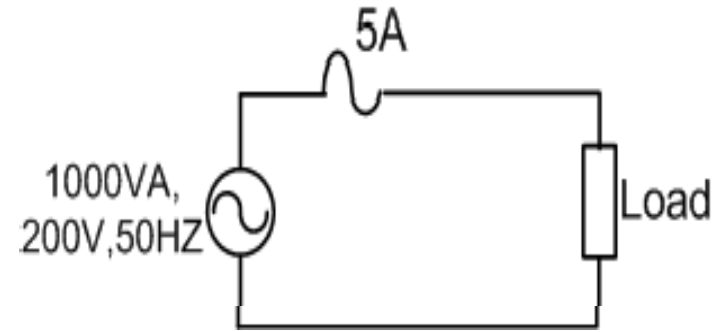

⇒ Source has the capability to supply P

⇒ If additional load (P) is connected

⇒ If losses are taken into account, I/P
power = losses

For any $I \neq 0 \Rightarrow I_s = \sqrt{I_a^2 + 5^2} \geq 5$

⇒ Fuse will operate


⇒ Else I^2R losses ↑,
└→ RMS value

⇒ Temperature rise

⇒ Cooling requirement



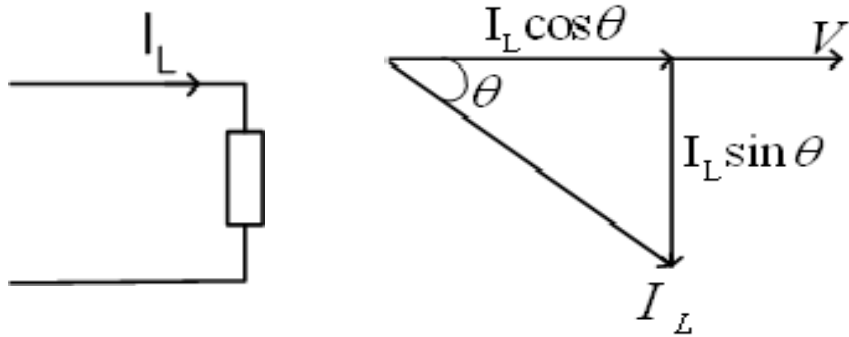- ⇒ Though 'L' does not consume any P_{source} capacity can not be utilized to cater other loads
- ⇒ Energy meter reading \propto power $\propto VI \cos\theta \propto I \cos\theta$



Load is drawing I_L

- ⇒ Energy Meter reading $\propto I_L \cos\theta$

\therefore Tariff $\propto I_L \cos\theta$

Who pays for $I_L \sin\theta$?

- ⇒ Fuel (power input) to supply Q may not be required

- ⇒ Utilities may not be able to cater other loads
- ⇒ Returns are low
- ⇒ Utilization and returns are maximum at unity p.f
- ⇒ Load requires reactive power
- ⇒ Generate reactive power locally
- ⇒ Capacitor draws leading I
- ⇒ If $I_C = I_L \sin\theta$, $I_s = I_L \cos\theta$
- ⇒ Overhead line loss & drop
- ⇒ Voltage profile at the load end also improves



Power factor Correction

- In DC, if P & V are known, I can be determined
- However in AC, P, V & $\cos\theta$ or V & S should be known to determine I

For a given P

- I drawn by load \uparrow as $\cos\theta$ (P.F.) \downarrow

\Rightarrow Drop in the line \uparrow

$\Rightarrow I^2R, I^2X$ in the line \uparrow and therefore 'S' of source \uparrow

$\Rightarrow I^2R$ loss in source also increases

- $V_L < V_s$ for lagging & unity P.F.
- $V_L \leq V_s$ or $V_L > V_s$ for leading P.F.

