

Some implications of the Shockley diode equation

$$I = qA \left(\frac{D_p p_{n0}}{L_p} + \frac{D_n n_{p0}}{L_n} \right) (e^{V_a/V_T} - 1)$$

Some implications of the Shockley diode equation

$$\begin{aligned} I &= qA \left(\frac{D_p p_{n0}}{L_p} + \frac{D_n n_{p0}}{L_n} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{D_p n_i^2}{N_d \sqrt{D_p \tau_p}} + \frac{D_n n_i^2}{N_a \sqrt{D_n \tau_n}} \right) (e^{V_a/V_T} - 1) \end{aligned}$$

Some implications of the Shockley diode equation

$$\begin{aligned} I &= qA \left(\frac{D_p p_{n0}}{L_p} + \frac{D_n n_{p0}}{L_n} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{D_p n_i^2}{N_d \sqrt{D_p \tau_p}} + \frac{D_n n_i^2}{N_a \sqrt{D_n \tau_n}} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right) (e^{V_a/V_T} - 1). \end{aligned}$$

Some implications of the Shockley diode equation

$$\begin{aligned} I &= qA \left(\frac{D_p p_{n0}}{L_p} + \frac{D_n n_{p0}}{L_n} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{D_p n_i^2}{N_d \sqrt{D_p \tau_p}} + \frac{D_n n_i^2}{N_a \sqrt{D_n \tau_n}} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right) (e^{V_a/V_T} - 1). \end{aligned}$$

Different materials ($T = 300$ K):

Some implications of the Shockley diode equation

$$\begin{aligned} I &= qA \left(\frac{D_p p_{n0}}{L_p} + \frac{D_n n_{p0}}{L_n} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{D_p n_i^2}{N_d \sqrt{D_p \tau_p}} + \frac{D_n n_i^2}{N_a \sqrt{D_n \tau_n}} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right) (e^{V_a/V_T} - 1). \end{aligned}$$

Different materials ($T = 300 \text{ K}$):

Semiconductor	$N_c \text{ (cm}^{-3}\text{)}$	$N_v \text{ (cm}^{-3}\text{)}$	$E_g \text{ (eV)}$	$n_i \text{ (cm}^{-3}\text{)}$
Ge	1.04×10^{19}	6.0×10^{18}	0.664	2.33×10^{13}
Si	2.8×10^{19}	1.04×10^{19}	1.12	1.02×10^{10}
GaAs	4.7×10^{17}	7.0×10^{18}	1.424	2.1×10^6

Some implications of the Shockley diode equation

$$\begin{aligned} I &= qA \left(\frac{D_p p_{n0}}{L_p} + \frac{D_n n_{p0}}{L_n} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{D_p n_i^2}{N_d \sqrt{D_p \tau_p}} + \frac{D_n n_i^2}{N_a \sqrt{D_n \tau_n}} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right) (e^{V_a/V_T} - 1). \end{aligned}$$

Different materials ($T = 300$ K):

Semiconductor	N_c (cm ⁻³)	N_v (cm ⁻³)	E_g (eV)	n_i (cm ⁻³)
Ge	1.04×10^{19}	6.0×10^{18}	0.664	2.33×10^{13}
Si	2.8×10^{19}	1.04×10^{19}	1.12	1.02×10^{10}
GaAs	4.7×10^{17}	7.0×10^{18}	1.424	2.1×10^6


Since $I \propto n_i^2$, the I - V curves (for the same diode area) are substantially different.

Some implications of the Shockley diode equation

$$\begin{aligned} I &= qA \left(\frac{D_p p_{n0}}{L_p} + \frac{D_n n_{p0}}{L_n} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{D_p n_i^2}{N_d \sqrt{D_p \tau_p}} + \frac{D_n n_i^2}{N_a \sqrt{D_n \tau_n}} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right) (e^{V_a/V_T} - 1). \end{aligned}$$

Different materials ($T = 300$ K):

Semiconductor	N_c (cm ⁻³)	N_v (cm ⁻³)	E_g (eV)	n_i (cm ⁻³)
Ge	1.04×10^{19}	6.0×10^{18}	0.664	2.33×10^{13}
Si	2.8×10^{19}	1.04×10^{19}	1.12	1.02×10^{10}
GaAs	4.7×10^{17}	7.0×10^{18}	1.424	2.1×10^6

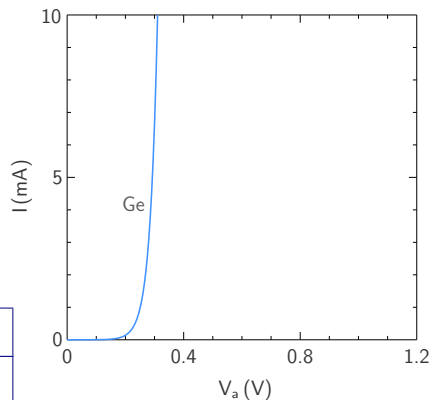


Since $I \propto n_i^2$, the I - V curves (for the same diode area) are substantially different.

Some implications of the Shockley diode equation

$$\begin{aligned} I &= qA \left(\frac{D_p p_{n0}}{L_p} + \frac{D_n n_{p0}}{L_n} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{D_p n_i^2}{N_d \sqrt{D_p \tau_p}} + \frac{D_n n_i^2}{N_a \sqrt{D_n \tau_n}} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right) (e^{V_a/V_T} - 1). \end{aligned}$$

Different materials ($T = 300$ K):

Semiconductor	N_c (cm ⁻³)	N_v (cm ⁻³)	E_g (eV)	n_i (cm ⁻³)
Ge	1.04×10^{19}	6.0×10^{18}	0.664	2.33×10^{13}
Si	2.8×10^{19}	1.04×10^{19}	1.12	1.02×10^{10}
GaAs	4.7×10^{17}	7.0×10^{18}	1.424	2.1×10^6

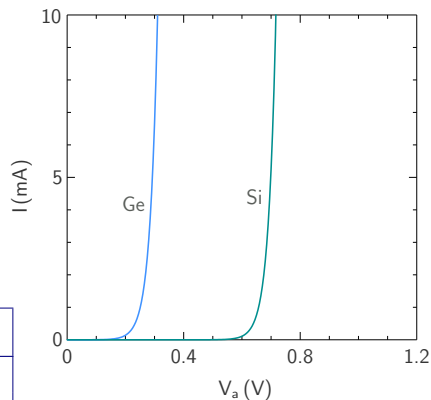


Since $I \propto n_i^2$, the I - V curves (for the same diode area) are substantially different.

Some implications of the Shockley diode equation

$$\begin{aligned} I &= qA \left(\frac{D_p p_{n0}}{L_p} + \frac{D_n n_{p0}}{L_n} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{D_p n_i^2}{N_d \sqrt{D_p \tau_p}} + \frac{D_n n_i^2}{N_a \sqrt{D_n \tau_n}} \right) (e^{V_a/V_T} - 1) \\ &= qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right) (e^{V_a/V_T} - 1). \end{aligned}$$

Different materials ($T = 300$ K):

Semiconductor	N_c (cm ⁻³)	N_v (cm ⁻³)	E_g (eV)	n_i (cm ⁻³)
Ge	1.04×10^{19}	6.0×10^{18}	0.664	2.33×10^{13}
Si	2.8×10^{19}	1.04×10^{19}	1.12	1.02×10^{10}
GaAs	4.7×10^{17}	7.0×10^{18}	1.424	2.1×10^6

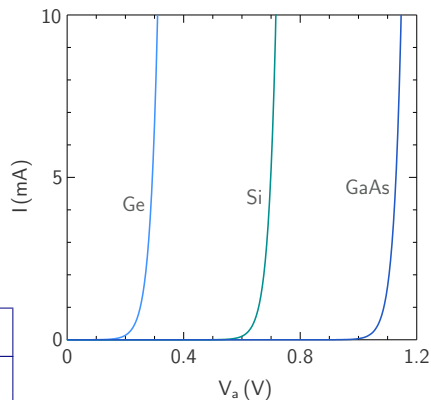

Since $I \propto n_i^2$, the I - V curves (for the same diode area) are substantially different.

Temperature dependence

$I = I_s (e^{V_a/V_T} - 1)$, where

$$I_s = qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right).$$

The temperature dependence of I_s comes mainly from $n_i(T)$.

Temperature dependence

$I = I_s (e^{V_a/V_T} - 1)$, where

$$I_s = qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right).$$

The temperature dependence of I_s comes mainly from $n_i(T)$.

$$n_i(T) = \sqrt{N_c(T)N_v(T)} \exp\left(-\frac{E_g(T)}{2kT}\right),$$

where $N_c \propto T^{3/2}$, $N_v \propto T^{3/2}$.

Temperature dependence

$I = I_s (e^{V_a/V_T} - 1)$, where

$$I_s = qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right).$$

The temperature dependence of I_s comes mainly from $n_i(T)$.

$$n_i(T) = \sqrt{N_c(T)N_v(T)} \exp\left(-\frac{E_g(T)}{2kT}\right),$$

where $N_c \propto T^{3/2}$, $N_v \propto T^{3/2}$.

$$E_g(T) \text{ for silicon is given by } E_g(T) = E_g(0) - \frac{\alpha T^2}{T + \beta} \text{ (eV),}$$

with $E_g(0) = 1.17 \text{ eV}$, $\alpha = 4.73 \times 10^{-4}$, $\beta = 636$.

Temperature dependence

$I = I_s (e^{V_a/V_T} - 1)$, where

$$I_s = qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right).$$


The temperature dependence of I_s comes mainly from $n_i(T)$.

$$n_i(T) = \sqrt{N_c(T)N_v(T)} \exp\left(-\frac{E_g(T)}{2kT}\right),$$

where $N_c \propto T^{3/2}$, $N_v \propto T^{3/2}$.

$$E_g(T) \text{ for silicon is given by } E_g(T) = E_g(0) - \frac{\alpha T^2}{T + \beta} \text{ (eV),}$$

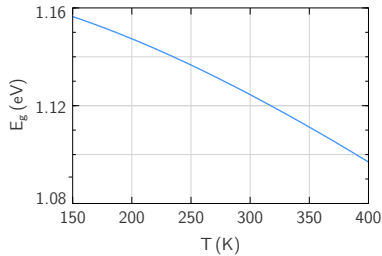with $E_g(0) = 1.17 \text{ eV}$, $\alpha = 4.73 \times 10^{-4}$, $\beta = 636$.



Temperature dependence

$I = I_s (e^{V_a/V_T} - 1)$, where

$$I_s = qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right).$$

The temperature dependence of I_s comes mainly from $n_i(T)$.


$$n_i(T) = \sqrt{N_c(T)N_v(T)} \exp\left(-\frac{E_g(T)}{2kT}\right),$$

where $N_c \propto T^{3/2}$, $N_v \propto T^{3/2}$.

$$E_g(T) \text{ for silicon is given by } E_g(T) = E_g(0) - \frac{\alpha T^2}{T + \beta} \text{ (eV),}$$

with $E_g(0) = 1.17 \text{ eV}$, $\alpha = 4.73 \times 10^{-4}$, $\beta = 636$.

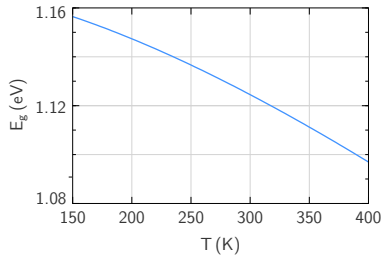As T increases, $E_g/2kT$ decreases, and n_i increases substantially because of the exponential function $\rightarrow I$ increases.



Temperature dependence

$I = I_s (e^{V_a/V_T} - 1)$, where

$$I_s = qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right).$$

The temperature dependence of I_s comes mainly from $n_i(T)$.



$$n_i(T) = \sqrt{N_c(T)N_v(T)} \exp\left(-\frac{E_g(T)}{2kT}\right),$$

where $N_c \propto T^{3/2}$, $N_v \propto T^{3/2}$.

$$E_g(T) \text{ for silicon is given by } E_g(T) = E_g(0) - \frac{\alpha T^2}{T + \beta} \text{ (eV),}$$

with $E_g(0) = 1.17 \text{ eV}$, $\alpha = 4.73 \times 10^{-4}$, $\beta = 636$.

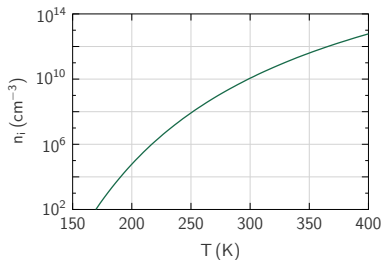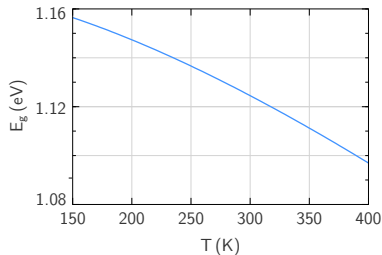As T increases, $E_g/2kT$ decreases, and n_i increases substantially because of the exponential function $\rightarrow I$ increases.



Temperature dependence

$I = I_s (e^{V_a/V_T} - 1)$, where

$$I_s = qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right).$$

The temperature dependence of I_s comes mainly from $n_i(T)$.




$$n_i(T) = \sqrt{N_c(T)N_v(T)} \exp\left(-\frac{E_g(T)}{2kT}\right),$$

where $N_c \propto T^{3/2}$, $N_v \propto T^{3/2}$.

$E_g(T)$ for silicon is given by $E_g(T) = E_g(0) - \frac{\alpha T^2}{T + \beta}$ (eV),

with $E_g(0) = 1.17$ eV, $\alpha = 4.73 \times 10^{-4}$, $\beta = 636$.

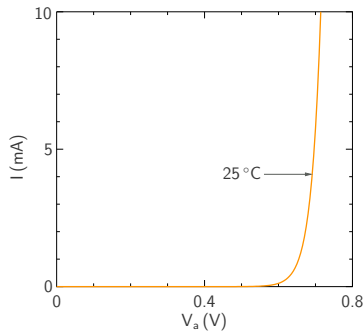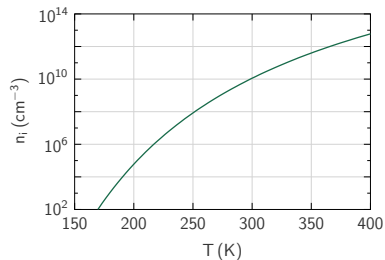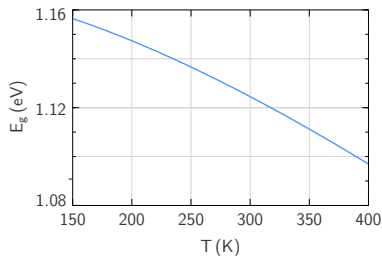As T increases, $E_g/2kT$ decreases, and n_i increases substantially because of the exponential function $\rightarrow I$ increases.



Temperature dependence

$I = I_s (e^{V_a/V_T} - 1)$, where

$$I_s = qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right).$$

The temperature dependence of I_s comes mainly from $n_i(T)$.




$$n_i(T) = \sqrt{N_c(T)N_v(T)} \exp\left(-\frac{E_g(T)}{2kT}\right),$$

where $N_c \propto T^{3/2}$, $N_v \propto T^{3/2}$.

$E_g(T)$ for silicon is given by $E_g(T) = E_g(0) - \frac{\alpha T^2}{T + \beta}$ (eV),

with $E_g(0) = 1.17$ eV, $\alpha = 4.73 \times 10^{-4}$, $\beta = 636$.

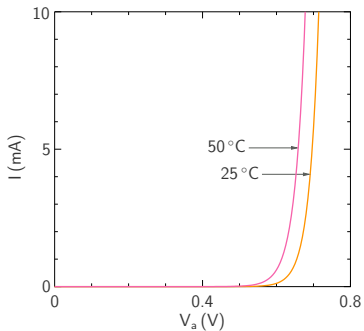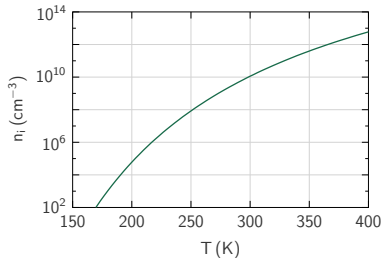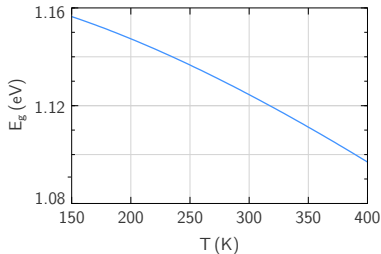As T increases, $E_g/2kT$ decreases, and n_i increases substantially because of the exponential function $\rightarrow I$ increases.



Temperature dependence

$I = I_s (e^{V_a/V_T} - 1)$, where

$$I_s = qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right).$$

The temperature dependence of I_s comes mainly from $n_i(T)$.




$$n_i(T) = \sqrt{N_c(T)N_v(T)} \exp\left(-\frac{E_g(T)}{2kT}\right),$$

where $N_c \propto T^{3/2}$, $N_v \propto T^{3/2}$.

$E_g(T)$ for silicon is given by $E_g(T) = E_g(0) - \frac{\alpha T^2}{T + \beta}$ (eV),

with $E_g(0) = 1.17$ eV, $\alpha = 4.73 \times 10^{-4}$, $\beta = 636$.

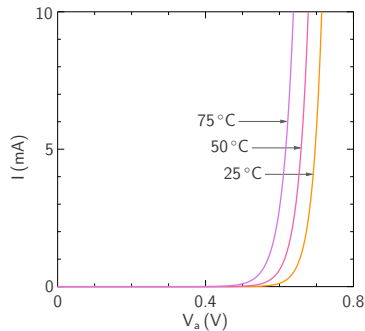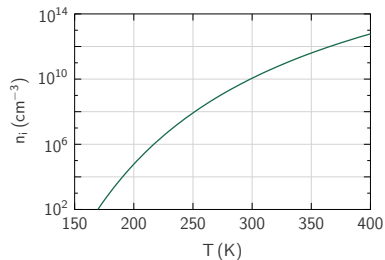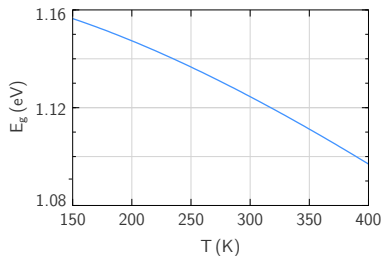As T increases, $E_g/2kT$ decreases, and n_i increases substantially because of the exponential function $\rightarrow I$ increases.



Temperature dependence

$I = I_s (e^{V_a/V_T} - 1)$, where

$$I_s = qA \left(\frac{n_i^2}{N_d} \sqrt{\frac{D_p}{\tau_p}} + \frac{n_i^2}{N_a} \sqrt{\frac{D_n}{\tau_n}} \right).$$

The temperature dependence of I_s comes mainly from $n_i(T)$.

$$n_i(T) = \sqrt{N_c(T)N_v(T)} \exp\left(-\frac{E_g(T)}{2kT}\right),$$




where $N_c \propto T^{3/2}$, $N_v \propto T^{3/2}$.

$E_g(T)$ for silicon is given by $E_g(T) = E_g(0) - \frac{\alpha T^2}{T + \beta}$ (eV),



with $E_g(0) = 1.17$ eV, $\alpha = 4.73 \times 10^{-4}$, $\beta = 636$.



As T increases, $E_g/2kT$ decreases, and n_i increases substantially because of the exponential function $\rightarrow I$ increases.

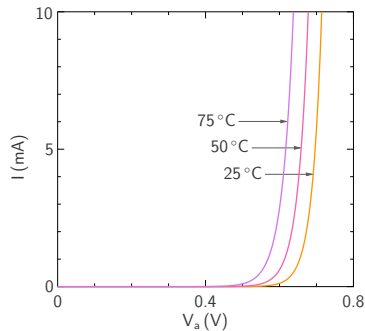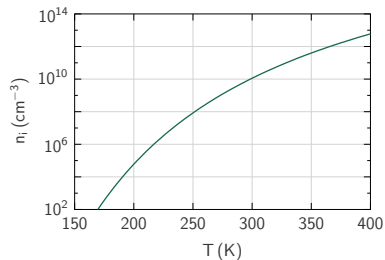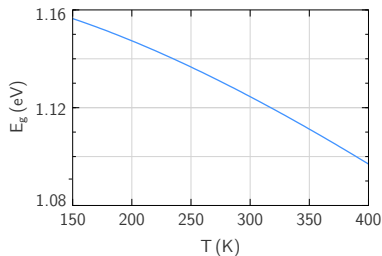For silicon, the I - V curve shifts by about -2 mV/ $^{\circ}\text{C}$ as the temperature is increased.





Reverse breakdown

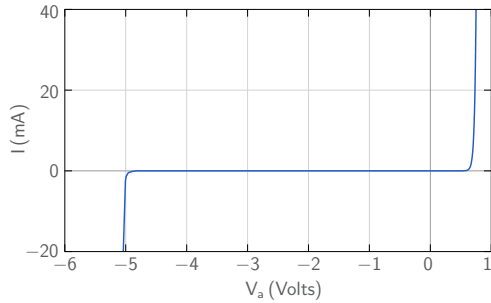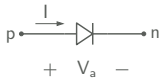

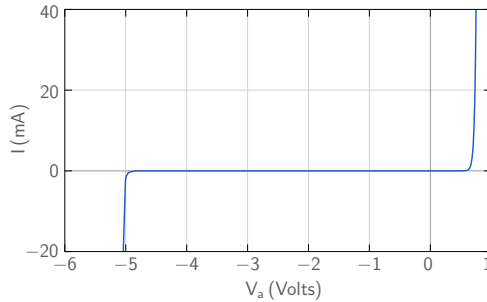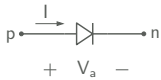

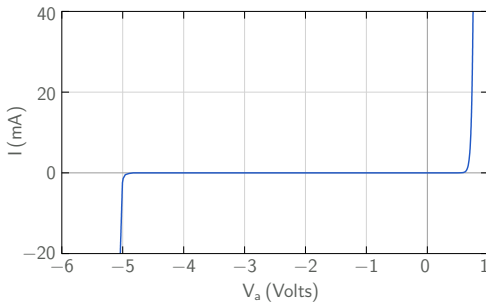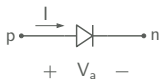- * A real diode cannot withstand indefinitely large reverse voltages and “breaks down” at some point as V_R is increased.




- * A real diode cannot withstand indefinitely large reverse voltages and “breaks down” at some point as V_R is increased.
- * Reverse breakdown can be due to
 - impact ionisation (avalanche breakdown)
 - tunneling (Zener breakdown)


- * We have looked at the DC behaviour of a *pn* junction diode so far. We now want to consider V_a (the applied voltage) varying with time.

- * We have looked at the DC behaviour of a *pn* junction diode so far. We now want to consider V_a (the applied voltage) varying with time.
- * Two situations are of interest:
 - * Small-signal behaviour (AC): With $V_a(t) = V_{DC} + V_m \sin \omega t$, how does the current vary with time when V_m is “small?”
 - * Large-signal behaviour: The variation in the applied voltage is not small. In particular, we are interested in the turn-off and turn-on transients.

Small-signal behaviour

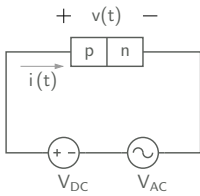


Small-signal behaviour

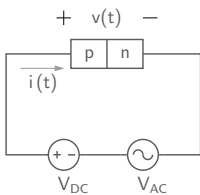


* Let $v(t) = V_{DC} + V_m \sin \omega t$.

Small-signal behaviour

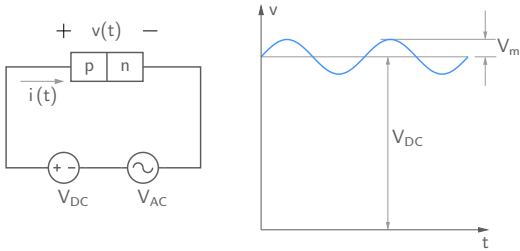


* Let $v(t) = V_{DC} + V_m \sin \omega t$.

Small-signal behaviour

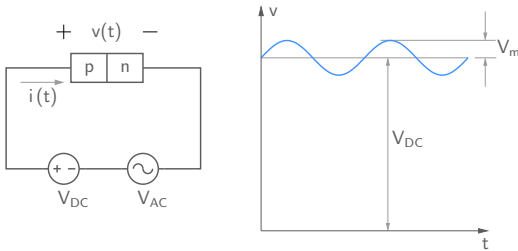


- * Let $v(t) = V_{DC} + V_m \sin \omega t$.
- * If V_m is “small,” the current is also sinusoidal, i.e., $i(t) = I_{DC} + I_m \sin(\omega t + \phi)$.

Small-signal behaviour

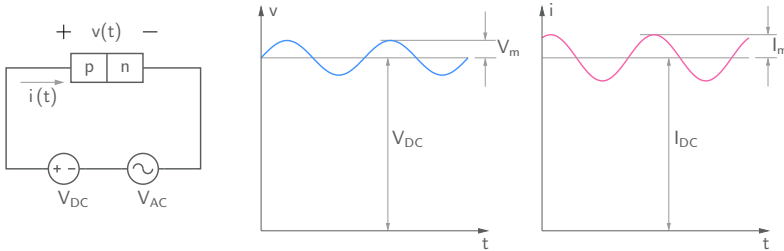

- * Let $v(t) = V_{DC} + V_m \sin \omega t$.
- * If V_m is “small,” the current is also sinusoidal, i.e., $i(t) = I_{DC} + I_m \sin(\omega t + \phi)$.

Small-signal behaviour

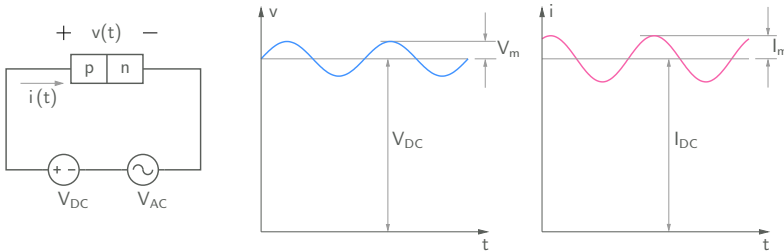

- * Let $v(t) = V_{DC} + V_m \sin \omega t$.
- * If V_m is “small,” the current is also sinusoidal, i.e., $i(t) = I_{DC} + I_m \sin(\omega t + \phi)$.
- * In small-signal analysis, we are interested in the relationship between the sinusoidal parts of the current and voltage, in particular, the ratio of the current and voltage phasors, $I_m \angle \phi / V_m \angle 0$.

Small-signal behaviour: reverse bias

- * A pn junction diode conducts negligibly small current with a DC reverse bias.

Small-signal behaviour: reverse bias


- * A pn junction diode conducts negligibly small current with a DC reverse bias.
- * With a time-varying applied reverse bias, it can conduct an appreciable current.

Small-signal behaviour: reverse bias

- * A pn junction diode conducts negligibly small current with a DC reverse bias.
- * With a time-varying applied reverse bias, it can conduct an appreciable current.
- * Consider a pn junction with $V_a = -V_R$, i.e., a reverse bias of V_R . If V_R is increased to $V_R + \Delta V_R$, the depletion width must change from W to $W + \Delta W$.


Small-signal behaviour: reverse bias

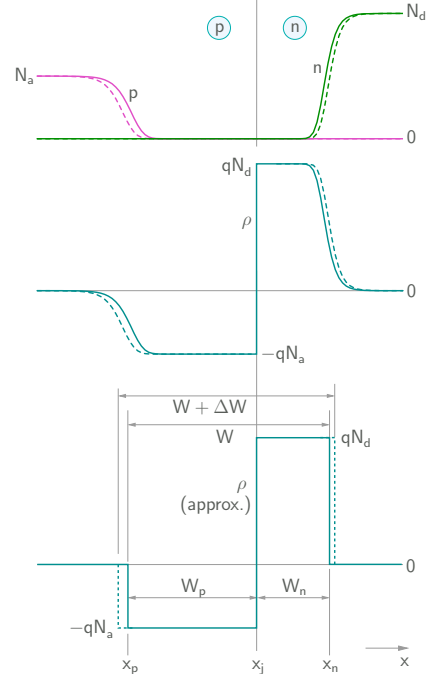- * A pn junction diode conducts negligibly small current with a DC reverse bias.
- * With a time-varying applied reverse bias, it can conduct an appreciable current.
- * Consider a pn junction with $V_a = -V_R$, i.e., a reverse bias of V_R . If V_R is increased to $V_R + \Delta V_R$, the depletion width must change from W to $W + \Delta W$.




Small-signal behaviour: reverse bias


- * A *pn* junction diode conducts negligibly small current with a DC reverse bias.
- * With a time-varying applied reverse bias, it can conduct an appreciable current.
- * Consider a *pn* junction with $V_a = -V_R$, i.e., a reverse bias of V_R . If V_R is increased to $V_R + \Delta V_R$, the depletion width must change from W to $W + \Delta W$.
- * This change is made possible by removal of majority carriers.

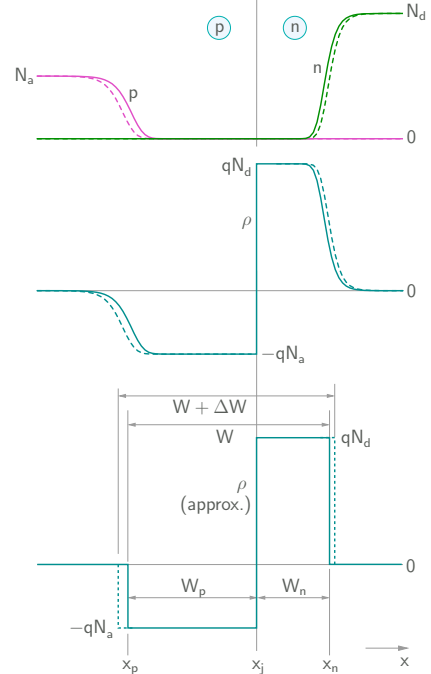

Small-signal behaviour: reverse bias

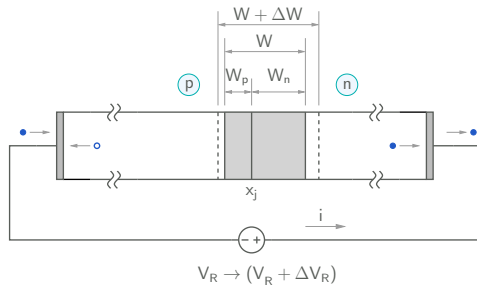


Small-signal behaviour: reverse bias

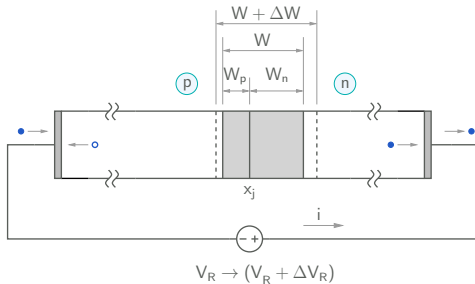

- * Movement of majority carriers is relatively fast, and the time scale involved is $\sim \tau = \frac{\epsilon_s}{q\mu_n n}$ for electrons.

For $n = 10^{16} \text{ cm}^{-3}$, $\mu_n = 1000 \text{ cm}^2/\text{V-s}$, $\epsilon_s = 11.7\epsilon_0$, $\tau = 0.6 \text{ ps}$, which is negligibly small for all practical purposes.

Small-signal behaviour: reverse bias

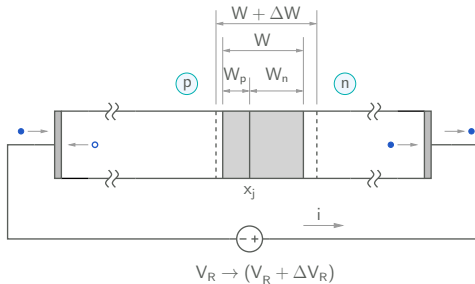


- * Movement of majority carriers is relatively fast, and the time scale involved is $\sim \tau = \frac{\epsilon_s}{q\mu_n n}$ for electrons.

For $n = 10^{16} \text{ cm}^{-3}$, $\mu_n = 1000 \text{ cm}^2/\text{V-s}$, $\epsilon_s = 11.7\epsilon_0$, $\tau = 0.6 \text{ ps}$, which is negligibly small for all practical purposes.

- * The situation is similar to a parallel-plate capacitor.

Small-signal behaviour: reverse bias

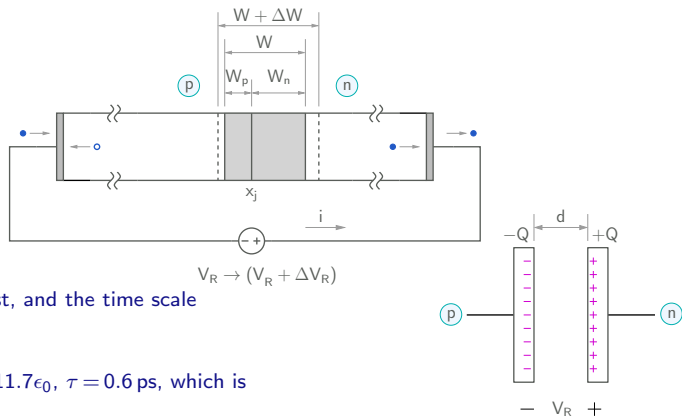


- * Movement of majority carriers is relatively fast, and the time scale involved is $\sim \tau = \frac{\epsilon_s}{q\mu_n n}$ for electrons.

For $n = 10^{16} \text{ cm}^{-3}$, $\mu_n = 1000 \text{ cm}^2/\text{V-s}$, $\epsilon_s = 11.7\epsilon_0$, $\tau = 0.6 \text{ ps}$, which is negligibly small for all practical purposes.

- * The situation is similar to a parallel-plate capacitor.
- * $V_a = V_R$: $Q = \text{Area} \times \int_{x_j}^{x_n} \rho dx = \text{Area} \times qN_d W_n$.

Small-signal behaviour: reverse bias

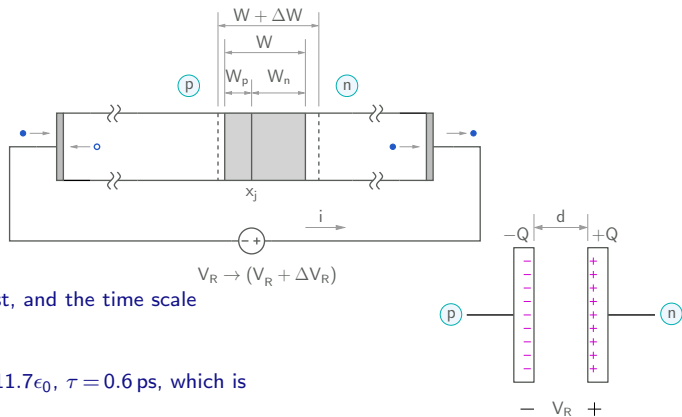


- * Movement of majority carriers is relatively fast, and the time scale involved is $\sim \tau = \frac{\epsilon_s}{q\mu_n n}$ for electrons.

For $n = 10^{16} \text{ cm}^{-3}$, $\mu_n = 1000 \text{ cm}^2/\text{V-s}$, $\epsilon_s = 11.7\epsilon_0$, $\tau = 0.6 \text{ ps}$, which is negligibly small for all practical purposes.

- * The situation is similar to a parallel-plate capacitor.
- * $V_a = V_R$: $Q = \text{Area} \times \int_{x_j}^{x_n} \rho dx = \text{Area} \times qN_d W_n$.
- * $V_R \rightarrow V_R + \Delta V_R \Rightarrow Q \rightarrow Q + \Delta Q$.

Small-signal behaviour: reverse bias

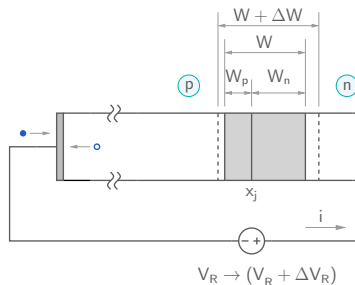



- * Movement of majority carriers is relatively fast, and the time scale involved is $\sim \tau = \frac{\epsilon_s}{q\mu_n n}$ for electrons.

For $n = 10^{16} \text{ cm}^{-3}$, $\mu_n = 1000 \text{ cm}^2/\text{V-s}$, $\epsilon_s = 11.7\epsilon_0$, $\tau = 0.6 \text{ ps}$, which is negligibly small for all practical purposes.


- * The situation is similar to a parallel-plate capacitor.

$$* V_a = V_R: Q = \text{Area} \times \int_{x_j}^{x_n} \rho dx = \text{Area} \times qN_d W_n.$$
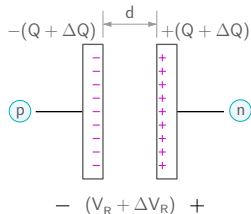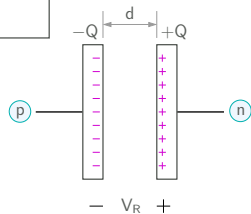
$$* V_R \rightarrow V_R + \Delta V_R \Rightarrow Q \rightarrow Q + \Delta Q.$$



Small-signal behaviour: reverse bias

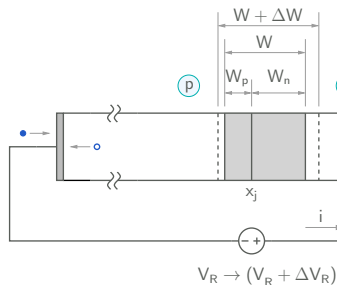

- * Movement of majority carriers is relatively fast, and the time scale involved is $\sim \tau = \frac{\epsilon_s}{q\mu_n n}$ for electrons.



For $n = 10^{16} \text{ cm}^{-3}$, $\mu_n = 1000 \text{ cm}^2/\text{V-s}$, $\epsilon_s = 11.7\epsilon_0$, $\tau = 0.6 \text{ ps}$, which is negligibly small for all practical purposes.

- * The situation is similar to a parallel-plate capacitor.


$$* V_a = V_R: Q = \text{Area} \times \int_{x_j}^{x_n} \rho dx = \text{Area} \times qN_d W_n.$$

$$* V_R \rightarrow V_R + \Delta V_R \Rightarrow Q \rightarrow Q + \Delta Q.$$

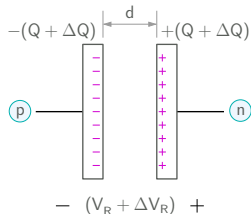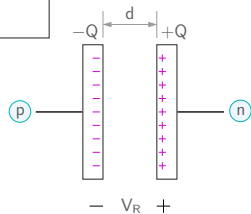
Note: For simplicity, we have not shown V_{bi} in the figure; the drop across the junction is actually $V_{bi} + V_R$, as seen before.



Small-signal behaviour: reverse bias

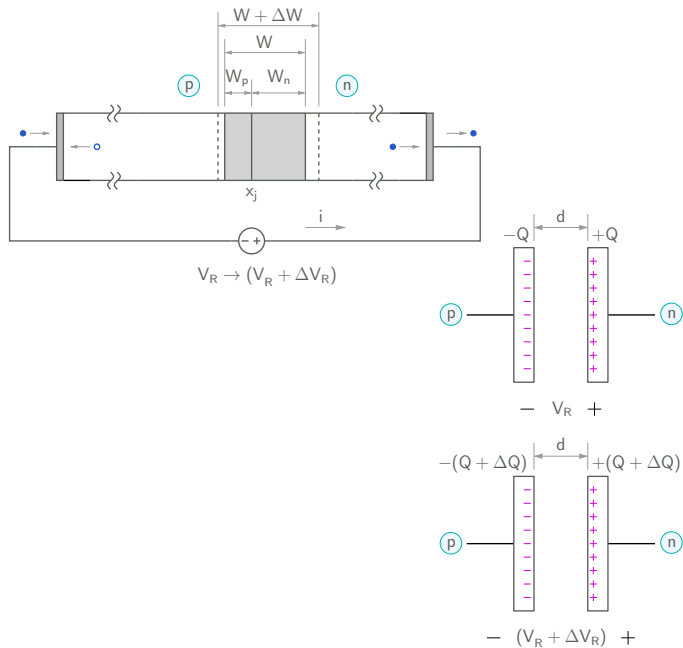


Small-signal behaviour: reverse bias

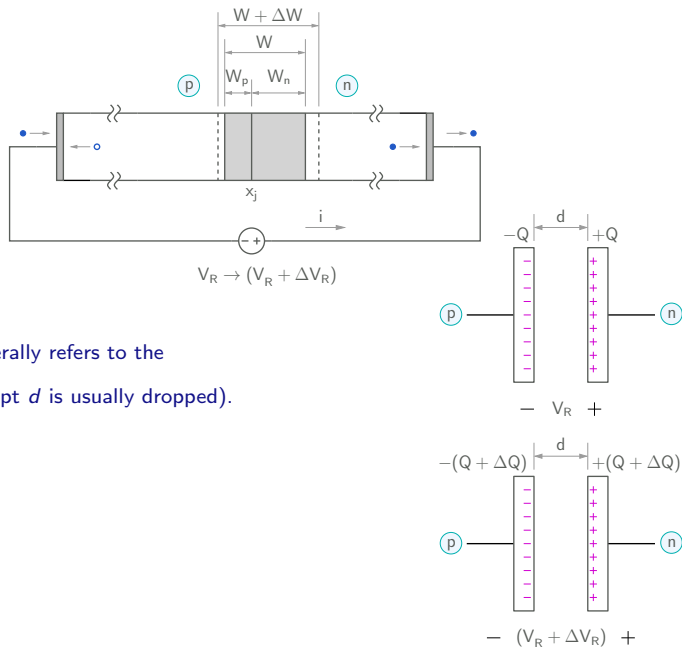

- * In semiconductor devices, “capacitance” generally refers to the differential capacitance $C_d = \frac{dQ}{dV}$ (the subscript d is usually dropped).


Small-signal behaviour: reverse bias

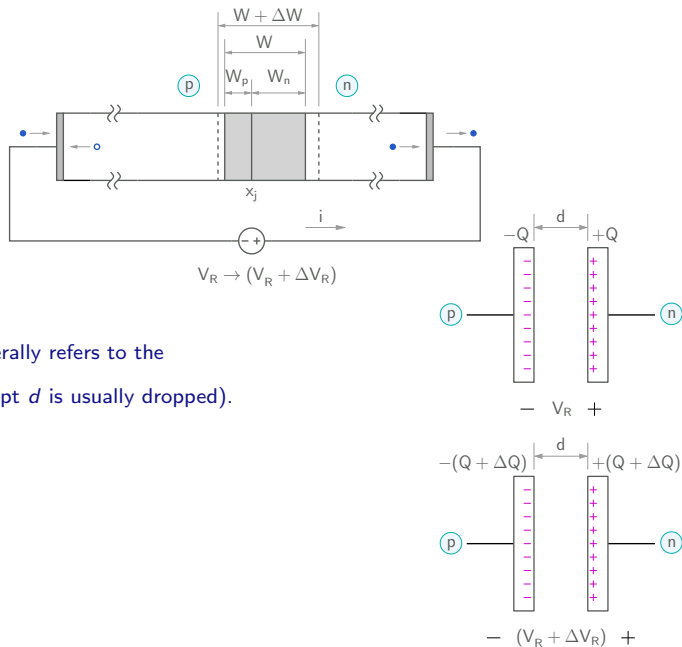

- * In semiconductor devices, “capacitance” generally refers to the differential capacitance $C_d = \frac{dQ}{dV}$ (the subscript d is usually dropped).
- * For a reverse-biased pn junction, $C = \frac{\Delta Q}{\Delta V_R}$.

Small-signal behaviour: reverse bias

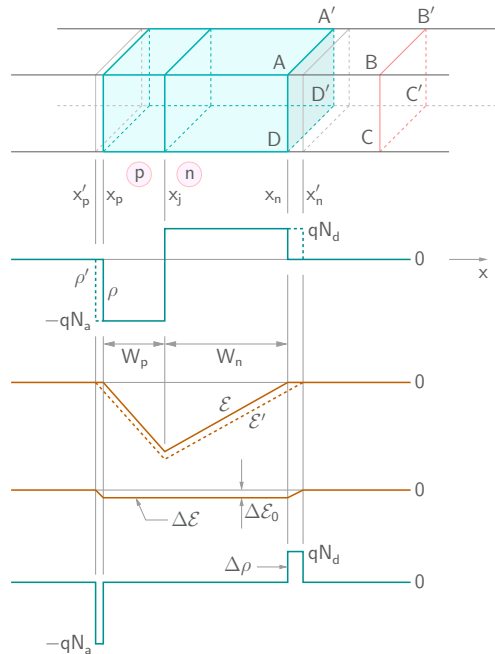
$$V_{bi} + V_R = - \int_{x_p}^{x_n} \mathcal{E}(x) dx$$



Small-signal behaviour: reverse bias

$$V_{bi} + V_R = - \int_{x_p}^{x_n} \mathcal{E}(x) dx$$
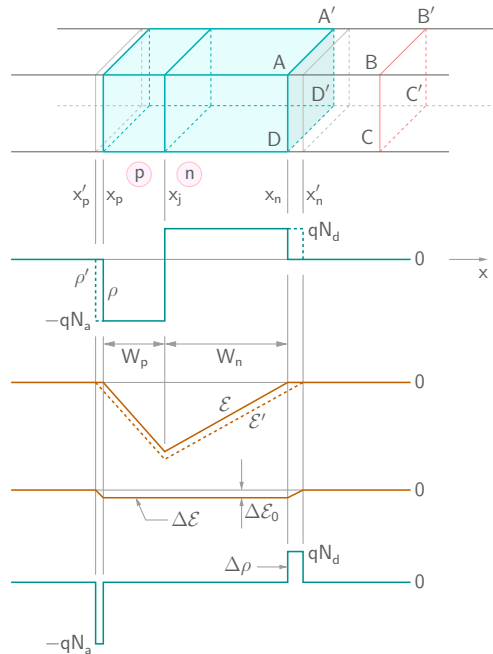
$$V_{bi} + V_R + \Delta V_R = - \int_{x'_p}^{x'_n} \mathcal{E}'(x) dx$$




Small-signal behaviour: reverse bias

$$V_{bi} + V_R = - \int_{x_p}^{x_n} \mathcal{E}(x) dx$$

$$V_{bi} + V_R + \Delta V_R = - \int_{x'_p}^{x'_n} \mathcal{E}'(x) dx$$
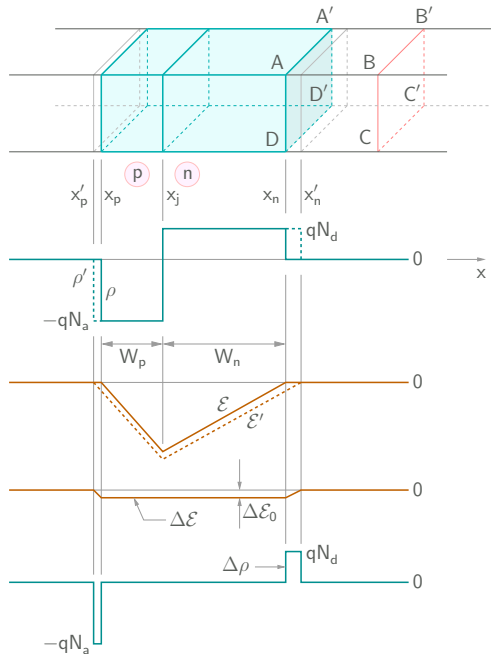
$$\rightarrow \Delta V_R = - \int_{x'_p}^{x'_n} (\mathcal{E}'(x) - \mathcal{E}(x)) dx = - \int_{x'_p}^{x'_n} \Delta \mathcal{E}(x) dx$$




Small-signal behaviour: reverse bias

$$V_{bi} + V_R = - \int_{x_p}^{x_n} \mathcal{E}(x) dx$$

$$V_{bi} + V_R + \Delta V_R = - \int_{x'_p}^{x'_n} \mathcal{E}'(x) dx$$
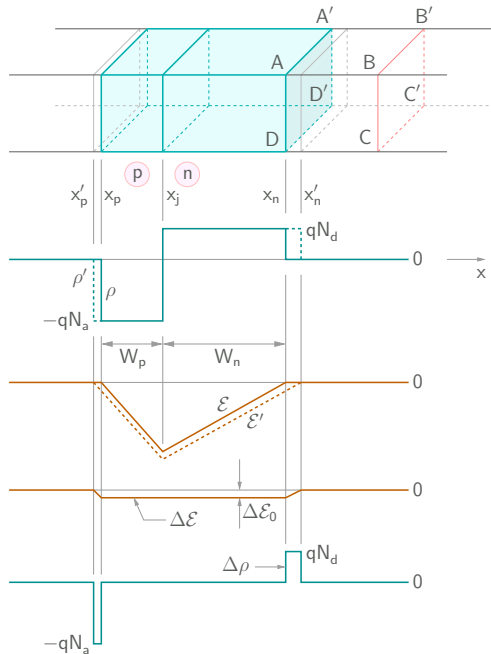
$$\begin{aligned} \rightarrow \Delta V_R &= - \int_{x'_p}^{x'_n} (\mathcal{E}'(x) - \mathcal{E}(x)) dx = - \int_{x'_p}^{x'_n} \Delta \mathcal{E}(x) dx \\ &= \Delta \mathcal{E}_0 W \text{ as } \Delta V_R \rightarrow 0 \text{ V.} \end{aligned}$$



Small-signal behaviour: reverse bias

$$V_{bi} + V_R = - \int_{x_p}^{x_n} \mathcal{E}(x) dx$$


$$V_{bi} + V_R + \Delta V_R = - \int_{x'_p}^{x'_n} \mathcal{E}'(x) dx$$

$$\rightarrow \Delta V_R = - \int_{x'_p}^{x'_n} (\mathcal{E}'(x) - \mathcal{E}(x)) dx = - \int_{x'_p}^{x'_n} \Delta \mathcal{E}(x) dx$$

$$= \Delta \mathcal{E}_0 W \text{ as } \Delta V_R \rightarrow 0 V.$$

ΔQ , the total charge in the Gaussian box between $AA'D'D$ and $BB'C'C$, is given by
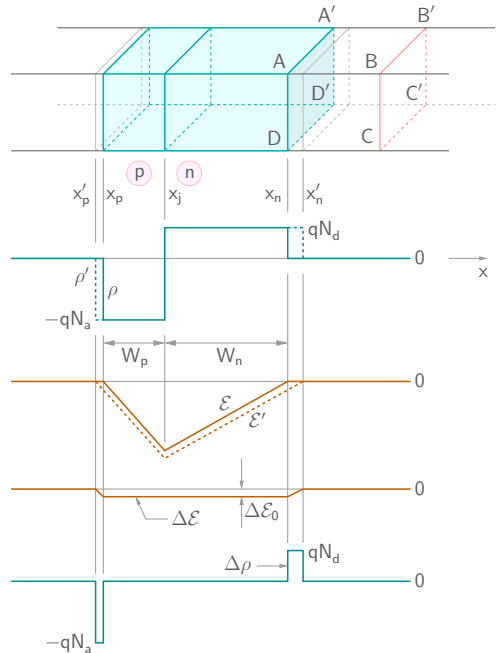
$$\Delta Q = \epsilon_s \oint \mathbf{E} \cdot d\mathbf{S} = A \epsilon_s \Delta \mathcal{E}_0.$$



Small-signal behaviour: reverse bias

$$V_{bi} + V_R = - \int_{x_p}^{x_n} \mathcal{E}(x) dx$$

$$V_{bi} + V_R + \Delta V_R = - \int_{x'_p}^{x'_n} \mathcal{E}'(x) dx$$

$$\rightarrow \Delta V_R = - \int_{x'_p}^{x'_n} (\mathcal{E}'(x) - \mathcal{E}(x)) dx = - \int_{x'_p}^{x'_n} \Delta \mathcal{E}(x) dx$$


$$= \Delta \mathcal{E}_0 W \text{ as } \Delta V_R \rightarrow 0 V.$$

ΔQ , the total charge in the Gaussian box between $AA'D'D$ and $BB'C'C$, is given by


$$\Delta Q = \epsilon_s \oint \mathbf{E} \cdot d\mathbf{S} = A \epsilon_s \Delta \mathcal{E}_0.$$

$$\rightarrow C_J = \left. \frac{\Delta Q}{\Delta V_R} \right|_{\Delta V_R \rightarrow 0} = \frac{A \epsilon_s}{W}.$$

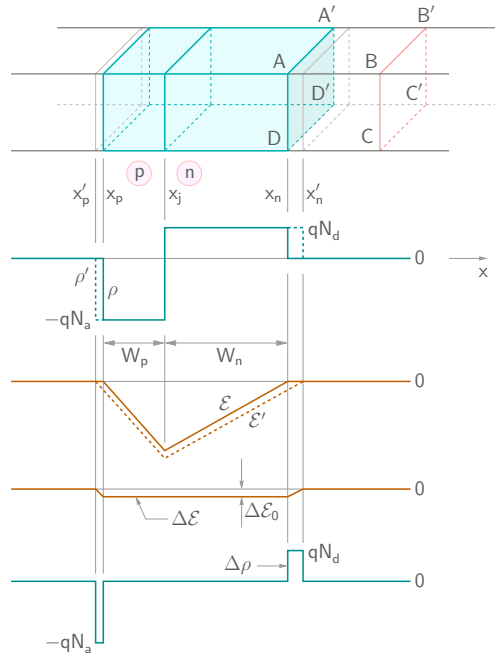C_J is called the “junction capacitance” or “depletion layer capacitance.”




Example

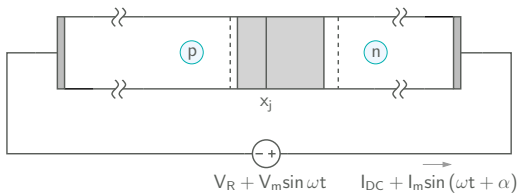

For an abrupt, uniformly doped silicon *pn* junction, with $N_a = 10^{17} \text{ cm}^{-3}$ and $N_d = 2 \times 10^{16} \text{ cm}^{-3}$, and area = 0.01 cm^2 , calculate the capacitance (i.e., the differential capacitance) for an applied reverse bias of $V_R = 2 \text{ V}$ ($T = 300 \text{ K}$).

Example

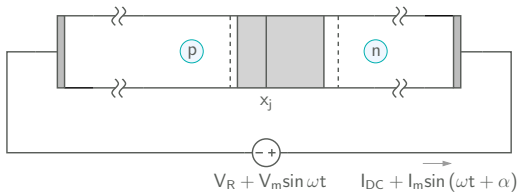


For an abrupt, uniformly doped silicon *pn* junction, with $N_a = 10^{17} \text{ cm}^{-3}$ and $N_d = 2 \times 10^{16} \text{ cm}^{-3}$, and area = 0.01 cm^2 , calculate the capacitance (i.e., the differential capacitance) for an applied reverse bias of $V_R = 2 \text{ V}$ ($T = 300 \text{ K}$).

Solution: The built-in voltage is

$$V_{bi} = \frac{kT}{q} \log \left(\frac{N_a N_d}{n_i^2} \right) = 0.77 \text{ V}.$$

Example

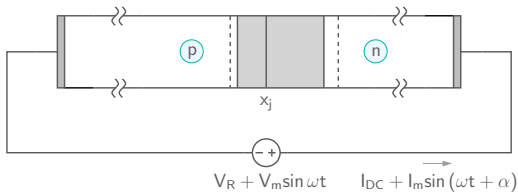


For an abrupt, uniformly doped silicon *pn* junction, with $N_a = 10^{17} \text{ cm}^{-3}$ and $N_d = 2 \times 10^{16} \text{ cm}^{-3}$, and area = 0.01 cm^2 , calculate the capacitance (i.e., the differential capacitance) for an applied reverse bias of $V_R = 2 \text{ V}$ ($T = 300 \text{ K}$).

Solution: The built-in voltage is

$$V_{bi} = \frac{kT}{q} \log \left(\frac{N_a N_d}{n_i^2} \right) = 0.77 \text{ V}.$$

The depletion width for $V_R = 2 \text{ V}$ is $W = \sqrt{\frac{2\epsilon}{q} \frac{N_a + N_d}{N_a N_d} (V_{bi} + V_R)} = 0.464 \mu\text{m}.$

Example

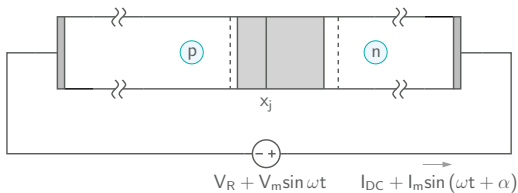

For an abrupt, uniformly doped silicon *pn* junction, with $N_a = 10^{17} \text{ cm}^{-3}$ and $N_d = 2 \times 10^{16} \text{ cm}^{-3}$, and area $= 0.01 \text{ cm}^2$, calculate the capacitance (i.e., the differential capacitance) for an applied reverse bias of $V_R = 2 \text{ V}$ ($T = 300 \text{ K}$).


Solution: The built-in voltage is

$$V_{bi} = \frac{kT}{q} \log \left(\frac{N_a N_d}{n_i^2} \right) = 0.77 \text{ V}.$$

The depletion width for $V_R = 2 \text{ V}$ is $W = \sqrt{\frac{2\epsilon}{q} \frac{N_a + N_d}{N_a N_d} (V_{bi} + V_R)} = 0.464 \mu\text{m}$.

$$\text{Capacitance } C_J = \frac{A \epsilon_s}{W} = \frac{0.01 \text{ cm}^2 \times 11.7 \times 8.85 \times 10^{-14} \text{ F/cm}}{0.464 \times 10^{-4} \text{ cm}}$$

Example

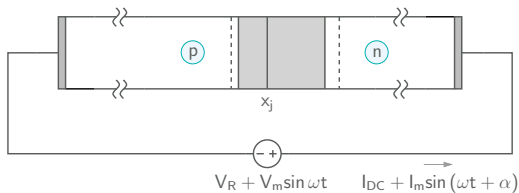

For an abrupt, uniformly doped silicon *pn* junction, with $N_a = 10^{17} \text{ cm}^{-3}$ and $N_d = 2 \times 10^{16} \text{ cm}^{-3}$, and area = 0.01 cm^2 , calculate the capacitance (i.e., the differential capacitance) for an applied reverse bias of $V_R = 2 \text{ V}$ ($T = 300 \text{ K}$).


Solution: The built-in voltage is

$$V_{bi} = \frac{kT}{q} \log \left(\frac{N_a N_d}{n_i^2} \right) = 0.77 \text{ V}.$$

The depletion width for $V_R = 2 \text{ V}$ is $W = \sqrt{\frac{2\epsilon}{q} \frac{N_a + N_d}{N_a N_d} (V_{bi} + V_R)} = 0.464 \text{ } \mu\text{m}$.

$$\begin{aligned} \text{Capacitance } C_J &= \frac{A \epsilon_s}{W} = \frac{0.01 \text{ cm}^2 \times 11.7 \times 8.85 \times 10^{-14} \text{ F/cm}}{0.464 \times 10^{-4} \text{ cm}} \\ &= 2.23 \times 10^{-10} \text{ F} \end{aligned}$$

Example

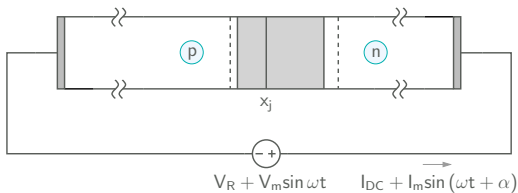

For an abrupt, uniformly doped silicon *pn* junction, with $N_a = 10^{17} \text{ cm}^{-3}$ and $N_d = 2 \times 10^{16} \text{ cm}^{-3}$, and area = 0.01 cm^2 , calculate the capacitance (i.e., the differential capacitance) for an applied reverse bias of $V_R = 2 \text{ V}$ ($T = 300 \text{ K}$).


Solution: The built-in voltage is

$$V_{bi} = \frac{kT}{q} \log \left(\frac{N_a N_d}{n_i^2} \right) = 0.77 \text{ V}.$$

The depletion width for $V_R = 2 \text{ V}$ is $W = \sqrt{\frac{2\epsilon}{q} \frac{N_a + N_d}{N_a N_d} (V_{bi} + V_R)} = 0.464 \mu\text{m}$.


$$\begin{aligned} \text{Capacitance } C_J &= \frac{A \epsilon_s}{W} = \frac{0.01 \text{ cm}^2 \times 11.7 \times 8.85 \times 10^{-14} \text{ F/cm}}{0.464 \times 10^{-4} \text{ cm}} \\ &= 2.23 \times 10^{-10} \text{ F} \\ &= 0.223 \text{ nF}. \end{aligned}$$

Example

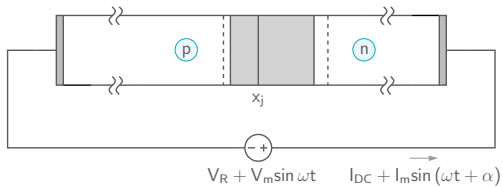

For a silicon n^+p junction, $N_a = 10^{16} \text{ cm}^{-3}$, and area = 0.01 cm^2 . Plot C_J versus V_a for $-5 \text{ V} < V_a < -0.1 \text{ V}$. Also, plot $1/C_J^2$ versus V_a . What information can one obtain from the second plot? Take $V_{bi} \approx 0.9 \text{ V}$. ($T = 300 \text{ K}$)

Example

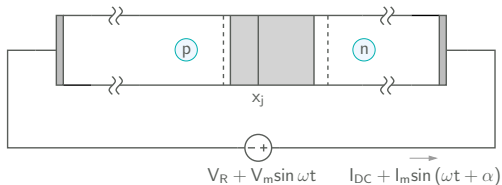


For a silicon n^+p junction, $N_a = 10^{16} \text{ cm}^{-3}$, and area = 0.01 cm^2 . Plot C_J versus V_a for $-5 \text{ V} < V_a < -0.1 \text{ V}$. Also, plot $1/C_J^2$ versus V_a . What information can one obtain from the second plot? Take $V_{bi} \approx 0.9 \text{ V}$. ($T = 300 \text{ K}$)

Solution: The junction capacitance is given by

$$C_J = \frac{A\epsilon_s}{W} = A\epsilon_s \sqrt{\frac{qN_a}{2\epsilon_s(V_{bi} - V_a)}}.$$

Example

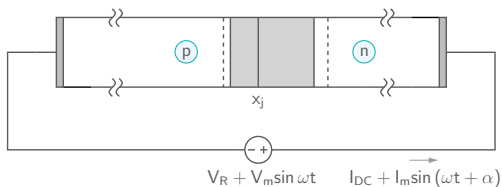


For a silicon n^+p junction, $N_a = 10^{16} \text{ cm}^{-3}$, and area = 0.01 cm^2 . Plot C_J versus V_a for $-5 \text{ V} < V_a < -0.1 \text{ V}$. Also, plot $1/C_J^2$ versus V_a . What information can one obtain from the second plot? Take $V_{bi} \approx 0.9 \text{ V}$. ($T = 300 \text{ K}$)

Solution: The junction capacitance is given by


$$C_J = \frac{A\epsilon_s}{W} = A\epsilon_s \sqrt{\frac{qN_a}{2\epsilon_s(V_{bi} - V_a)}}.$$

$$\frac{1}{C_J^2} = \frac{1}{(A\epsilon_s)^2} \frac{2\epsilon_s(V_{bi} - V_a)}{qN_a} = \frac{2}{qN_a\epsilon_s A^2} (V_{bi} - V_a).$$

Example

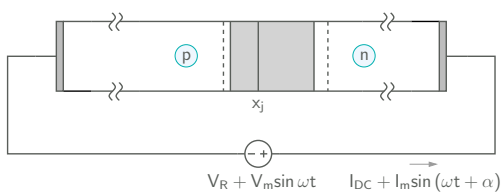

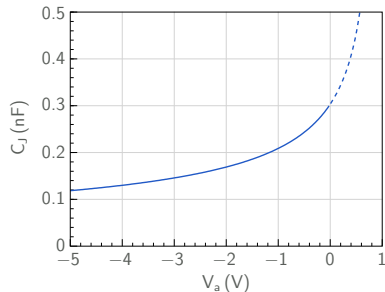For a silicon n^+p junction, $N_a = 10^{16} \text{ cm}^{-3}$, and area = 0.01 cm^2 . Plot C_J versus V_a for $-5 \text{ V} < V_a < -0.1 \text{ V}$. Also, plot $1/C_J^2$ versus V_a . What information can one obtain from the second plot? Take $V_{bi} \approx 0.9 \text{ V}$. ($T = 300 \text{ K}$)




Solution: The junction capacitance is given by

$$C_J = \frac{A\epsilon_s}{W} = A\epsilon_s \sqrt{\frac{qN_a}{2\epsilon_s(V_{bi} - V_a)}}.$$

$$\frac{1}{C_J^2} = \frac{1}{(A\epsilon_s)^2} \frac{2\epsilon_s(V_{bi} - V_a)}{qN_a} = \frac{2}{qN_a\epsilon_s A^2} (V_{bi} - V_a).$$

Example


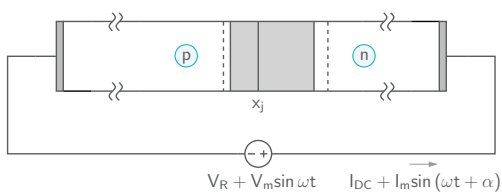


For a silicon n^+p junction, $N_a = 10^{16} \text{ cm}^{-3}$, and area = 0.01 cm^2 . Plot C_J versus V_a for $-5 \text{ V} < V_a < -0.1 \text{ V}$. Also, plot $1/C_J^2$ versus V_a . What information can one obtain from the second plot? Take $V_{bi} \approx 0.9 \text{ V}$. ($T = 300 \text{ K}$)


Solution: The junction capacitance is given by

$$C_J = \frac{A\epsilon_s}{W} = A\epsilon_s \sqrt{\frac{qN_a}{2\epsilon_s(V_{bi} - V_a)}}.$$
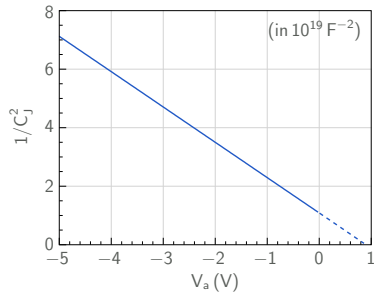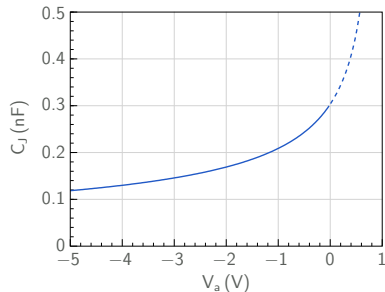
$$\frac{1}{C_J^2} = \frac{1}{(A\epsilon_s)^2} \frac{2\epsilon_s(V_{bi} - V_a)}{qN_a} = \frac{2}{qN_a\epsilon_s A^2} (V_{bi} - V_a).$$



Example

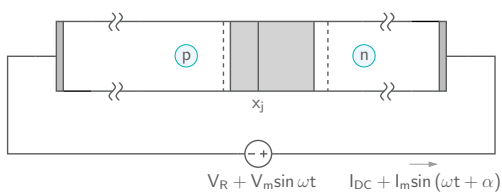



For a silicon n^+p junction, $N_a = 10^{16} \text{ cm}^{-3}$, and area = 0.01 cm^2 . Plot C_J versus V_a for $-5 \text{ V} < V_a < -0.1 \text{ V}$. Also, plot $1/C_J^2$ versus V_a . What information can one obtain from the second plot? Take $V_{bi} \approx 0.9 \text{ V}$. ($T = 300 \text{ K}$)

Solution: The junction capacitance is given by


$$C_J = \frac{A\epsilon_s}{W} = A\epsilon_s \sqrt{\frac{qN_a}{2\epsilon_s(V_{bi} - V_a)}}.$$

$$\frac{1}{C_J^2} = \frac{1}{(A\epsilon_s)^2} \frac{2\epsilon_s(V_{bi} - V_a)}{qN_a} = \frac{2}{qN_a\epsilon_s A^2} (V_{bi} - V_a).$$

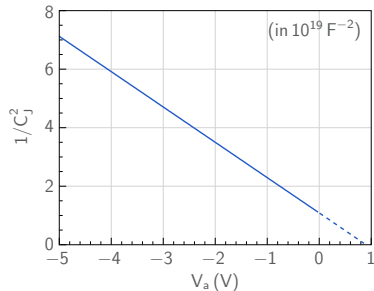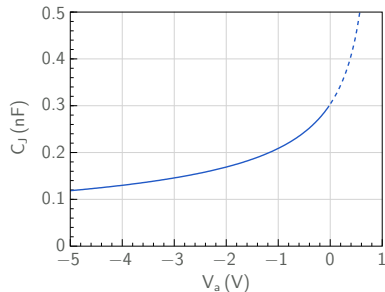→ $1/C_J^2$ versus V_a : Slope gives N_a ; x-intercept gives V_{bi} .




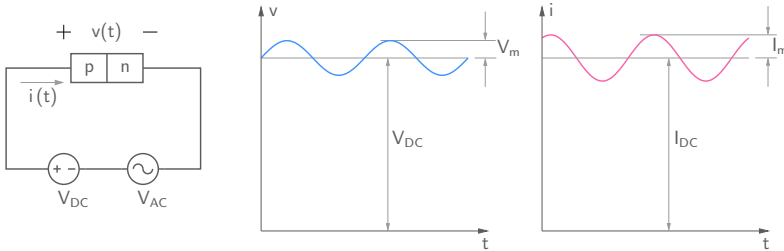What is meant by “small-signal” condition?



Small signal → With a sinusoidal input, the output (voltage or current) should also be sinusoidal, i.e., it should not be distorted.

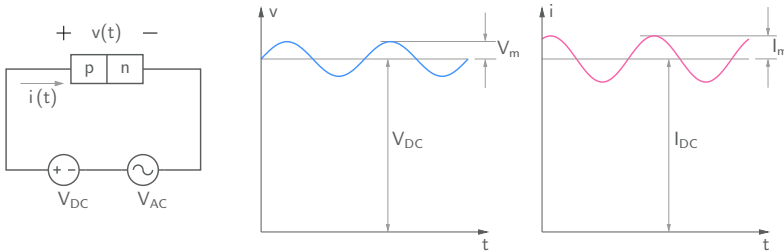
What is meant by “small-signal” condition?



Small signal \rightarrow With a sinusoidal input, the output (voltage or current) should also be sinusoidal, i.e., it should not be distorted.

For a reverse-biased pn junction, $C_J = \frac{dQ}{dV_a} = \frac{A\epsilon_s}{W(V_a)} = \frac{K}{\sqrt{V_{bi} - V_a}}$, with $K = A\epsilon_s \sqrt{\frac{qN_aN_d}{2\epsilon_s(N_a + N_d)}}$.

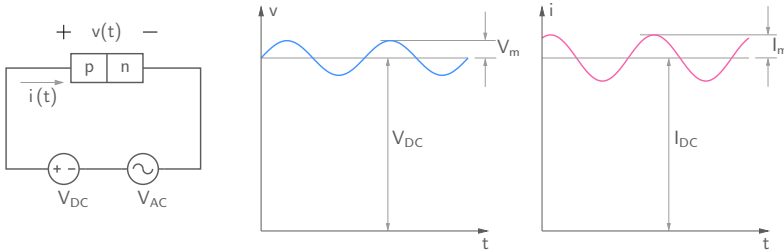What is meant by “small-signal” condition?




Small signal \rightarrow With a sinusoidal input, the output (voltage or current) should also be sinusoidal, i.e., it should not be distorted.

For a reverse-biased pn junction, $C_J = \frac{dQ}{dV_a} = \frac{A\epsilon_s}{W(V_a)} = \frac{K}{\sqrt{V_{bi} - V_a}}$, with $K = A\epsilon_s \sqrt{\frac{qN_aN_d}{2\epsilon_s(N_a + N_d)}}$.

With $V_a(t) = -(V_R + V_m \sin \omega t)$, $i(t) = \frac{dQ}{dt} = \frac{dQ}{dV_a} \frac{dV_a}{dt} = C_J(V_a) \times (-\omega V_m \cos \omega t)$.

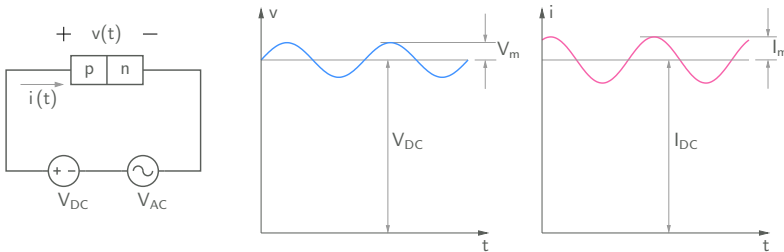What is meant by “small-signal” condition?




Small signal \rightarrow With a sinusoidal input, the output (voltage or current) should also be sinusoidal, i.e., it should not be distorted.

For a reverse-biased pn junction, $C_J = \frac{dQ}{dV_a} = \frac{A\epsilon_s}{W(V_a)} = \frac{K}{\sqrt{V_{bi} - V_a}}$, with $K = A\epsilon_s \sqrt{\frac{qN_aN_d}{2\epsilon_s(N_a + N_d)}}$.

With $V_a(t) = -(V_R + V_m \sin \omega t)$, $i(t) = \frac{dQ}{dt} = \frac{dQ}{dV_a} \frac{dV_a}{dt} = C_J(V_a) \times (-\omega V_m \cos \omega t)$.

$\rightarrow i(t)$ is sinusoidal if C_J can be treated as a constant.

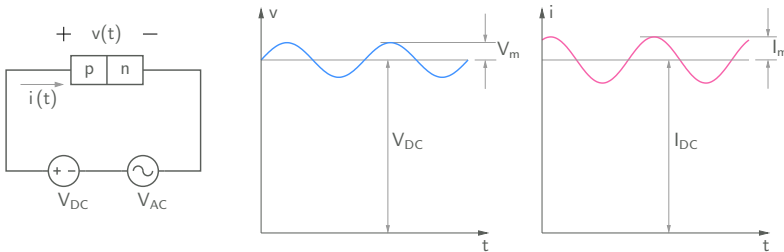
What is meant by “small-signal” condition?



$$v_a(t) = -(V_R + V_m \sin \omega t) \rightarrow -(V_R + V_m) < v_a < -(V_R - V_m).$$

$$C_J^{\min} = \frac{K}{\sqrt{V_{bi} + V_R + V_m}}, \quad C_J^{\max} = \frac{K}{\sqrt{V_{bi} + V_R - V_m}}.$$

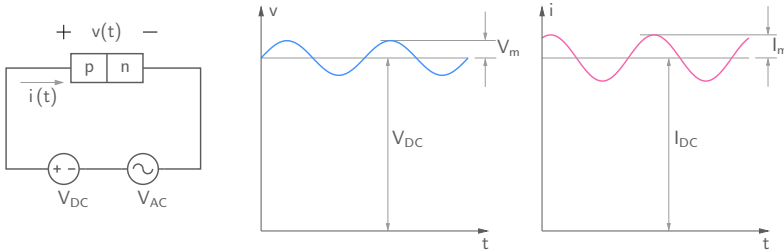What is meant by “small-signal” condition?




$$v_a(t) = -(V_R + V_m \sin \omega t) \rightarrow -(V_R + V_m) < v_a < -(V_R - V_m).$$

$$C_J^{\min} = \frac{K}{\sqrt{V_{bi} + V_R + V_m}}, \quad C_J^{\max} = \frac{K}{\sqrt{V_{bi} + V_R - V_m}}.$$

Consider one of these two extreme values,

$$C_J^{\max} = \frac{K}{\sqrt{V_{bi} + V_R - V_m}} = \frac{K}{\sqrt{V_{bi} + V_R}} \times \frac{1}{\sqrt{1 - \frac{V_m}{V_{bi} + V_R}}} \approx \frac{K}{\sqrt{V_{bi} + V_R}} \left(1 + \frac{1}{2} \frac{V_m}{V_{bi} + V_R} \right).$$

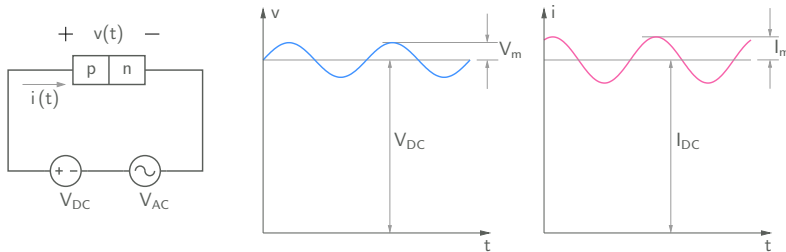What is meant by “small-signal” condition?



$$v_a(t) = -(V_R + V_m \sin \omega t) \rightarrow -(V_R + V_m) < v_a < -(V_R - V_m).$$


$$C_J^{\min} = \frac{K}{\sqrt{V_{bi} + V_R + V_m}}, \quad C_J^{\max} = \frac{K}{\sqrt{V_{bi} + V_R - V_m}}.$$

Consider one of these two extreme values,

$$C_J^{\max} = \frac{K}{\sqrt{V_{bi} + V_R - V_m}} = \frac{K}{\sqrt{V_{bi} + V_R}} \times \frac{1}{\sqrt{1 - \frac{V_m}{V_{bi} + V_R}}} \approx \frac{K}{\sqrt{V_{bi} + V_R}} \left(1 + \frac{1}{2} \frac{V_m}{V_{bi} + V_R} \right).$$



If $\frac{V_m}{2(V_{bi} + V_R)} \ll 1$, C_J can be treated as a constant.

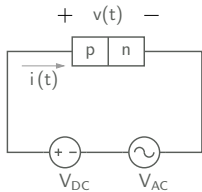What is meant by “small-signal” condition?






* Small-signal condition: $\frac{V_m}{2(V_{bi} + V_R)} \ll 1$.

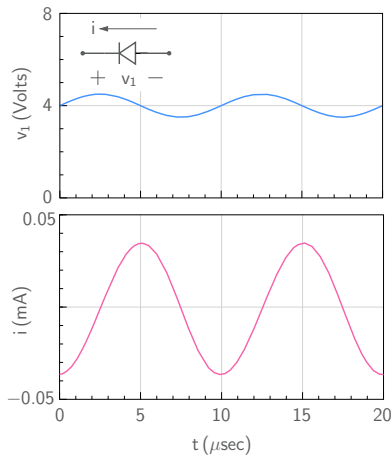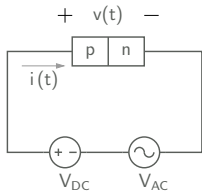What is meant by “small-signal” condition?






* Small-signal condition: $\frac{V_m}{2(V_{bi} + V_R)} \ll 1$.

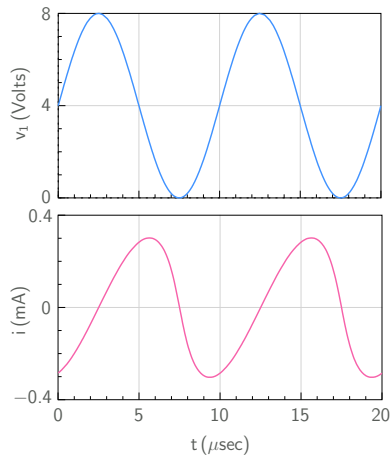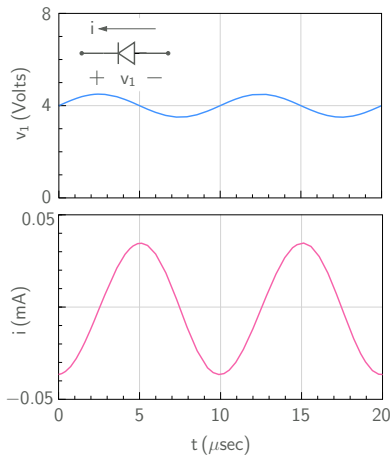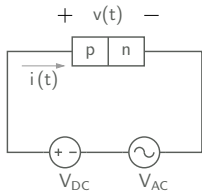What is meant by “small-signal” condition?



* Small-signal condition: $\frac{V_m}{2(V_{bi} + V_R)} \ll 1$.

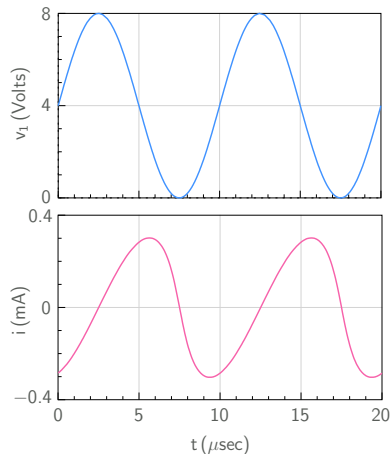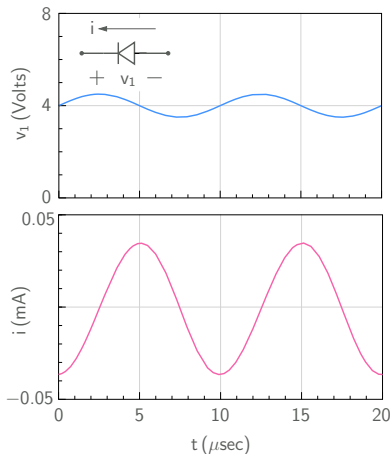
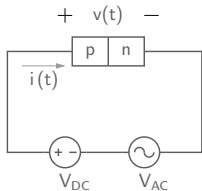
What is meant by “small-signal” condition?





* Small-signal condition: $\frac{V_m}{2(V_{bi} + V_R)} \ll 1$.

* If the small-signal condition is not satisfied, $i(t)$ shows distortion.

Small-signal behaviour: reverse bias

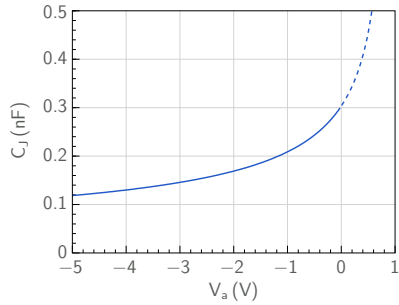
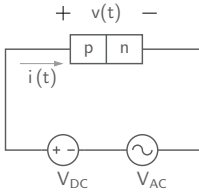


Small-signal behaviour: reverse bias

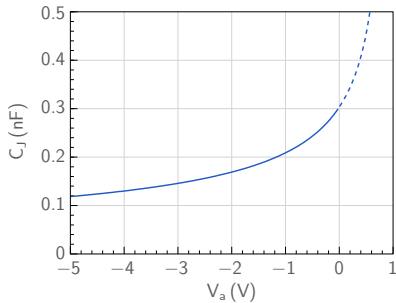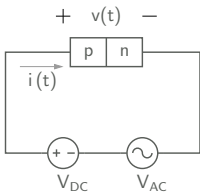



- * The voltage-dependent capacitance provided by a reverse-biased pn junction is useful in practice.

Small-signal behaviour: reverse bias

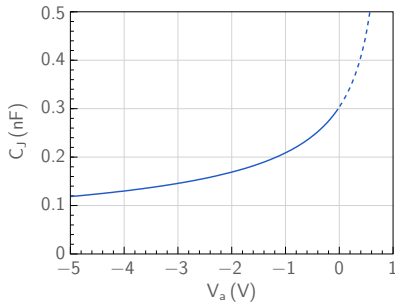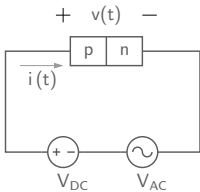

- * The voltage-dependent capacitance provided by a reverse-biased *pn* junction is useful in practice.
- * Specially designed diodes called “varactors” (variable reactors) are used in applications such as voltage-variable tuning, mixing, detection, etc.

Small-signal behaviour: reverse bias

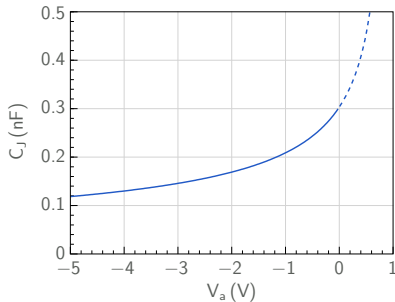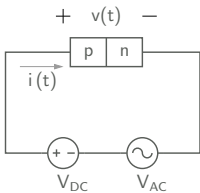

- * The voltage-dependent capacitance provided by a reverse-biased *pn* junction is useful in practice.
- * Specially designed diodes called “varactors” (variable reactors) are used in applications such as voltage-variable tuning, mixing, detection, etc.
- * In these devices, the doping density profiles are designed so as to get a large capacitance change for a small change in reverse bias.