

SEMICONDUCTOR DEVICES

Junction Field-Effect Transistors: Part 2





M. B. Patil

mbpatil@ee.iitb.ac.in

www.ee.iitb.ac.in/~sequel

Department of Electrical Engineering
Indian Institute of Technology Bombay



JFET I - V relationship

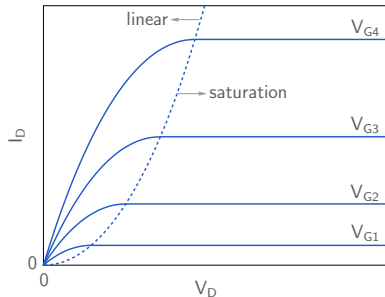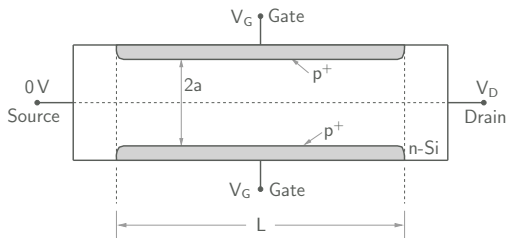

In the linear region, i.e., $V_D < V_D^{\text{sat}}$,

$$I_D = G_0 \left\{ V_D - \frac{2}{3} (V_{bi} - V_P) \left[\left(\frac{V_D + V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, \quad G_0 = \frac{(2aZ)}{L} \times (q\mu_n N_d).$$

JFET I - V relationship

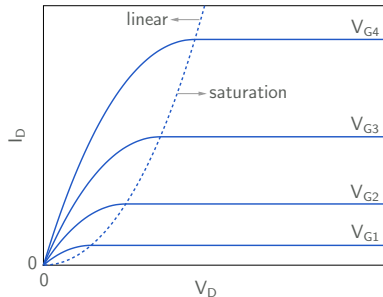
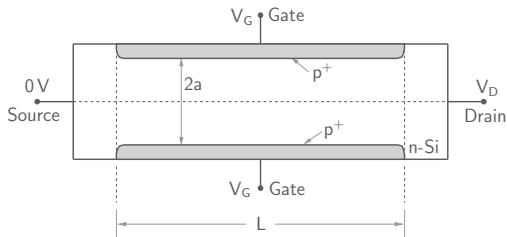


In the linear region, i.e., $V_D < V_D^{\text{sat}}$,

$$I_D = G_0 \left\{ V_D - \frac{2}{3} (V_{bi} - V_P) \left[\left(\frac{V_D + V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, \quad G_0 = \frac{(2aZ)}{L} \times (q\mu_n N_d).$$

Pinch-off (saturation): $V_G - V_D = V_P \rightarrow V_D^{\text{sat}} = V_G - V_P$.

JFET I - V relationship

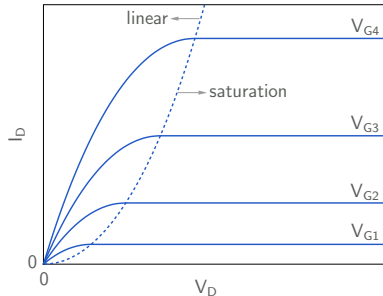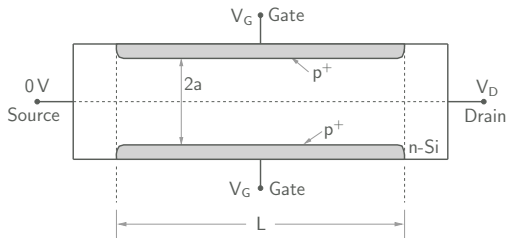

In the linear region, i.e., $V_D < V_D^{\text{sat}}$,



$$I_D = G_0 \left\{ V_D - \frac{2}{3} (V_{\text{bi}} - V_P) \left[\left(\frac{V_D + V_{\text{bi}} - V_G}{V_{\text{bi}} - V_P} \right)^{3/2} - \left(\frac{V_{\text{bi}} - V_G}{V_{\text{bi}} - V_P} \right)^{3/2} \right] \right\}, \quad G_0 = \frac{(2aZ)}{L} \times (q\mu_n N_d).$$

Pinch-off (saturation): $V_G - V_D = V_P \rightarrow V_D^{\text{sat}} = V_G - V_P$.

Substituting in the I_D equation, we get

$$I_D^{\text{sat}}(V_G) = G_0 \left\{ (V_G - V_P) - \frac{2}{3} (V_{\text{bi}} - V_P) \left[1 - \left(\frac{V_{\text{bi}} - V_G}{V_{\text{bi}} - V_P} \right)^{3/2} \right] \right\}.$$

JFET I - V relationship

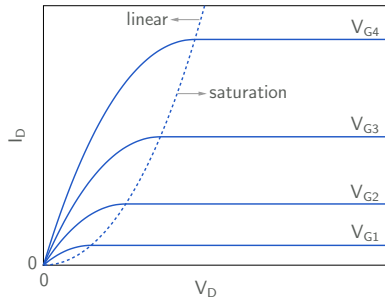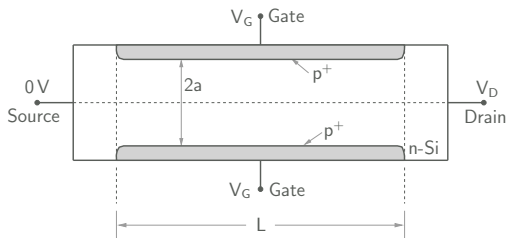

In the linear region, i.e., $V_D < V_D^{\text{sat}}$,

$$I_D = G_0 \left\{ V_D - \frac{2}{3} (V_{bi} - V_P) \left[\left(\frac{V_D + V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, \quad G_0 = \frac{(2aZ)}{L} \times (q\mu_n N_d).$$



Pinch-off (saturation): $V_G - V_D = V_P \rightarrow V_D^{\text{sat}} = V_G - V_P$.

Substituting in the I_D equation, we get



$$I_D^{\text{sat}}(V_G) = G_0 \left\{ (V_G - V_P) - \frac{2}{3} (V_{bi} - V_P) \left[1 - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}.$$

Note that I_D^{sat} depends on V_G . For an n -channel JFET, $I_D^{\text{sat}} \downarrow$ as $V_G \downarrow$

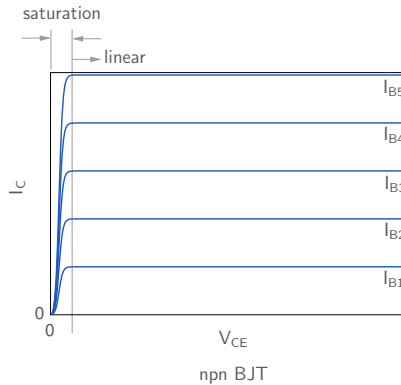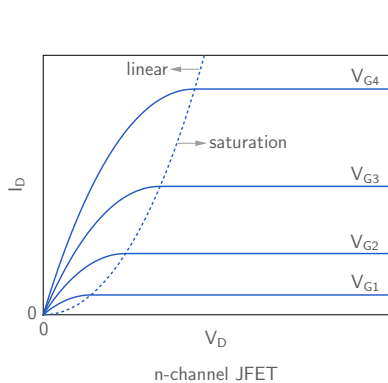Comparison of JFET and BJT I - V relationships





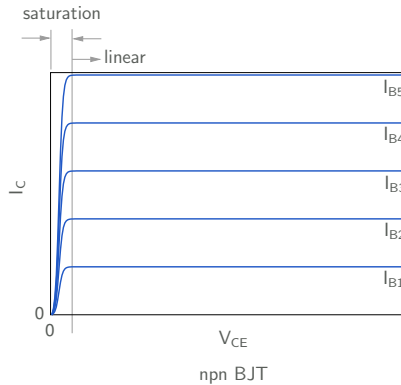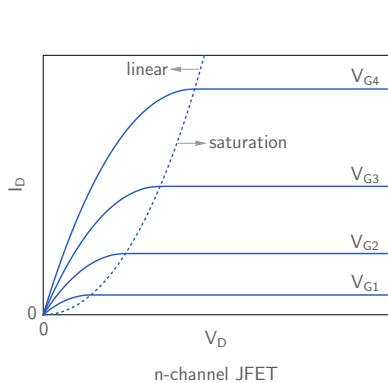Comparison of JFET and BJT I - V relationships




* Note the different nomenclature for linear and saturation regions.

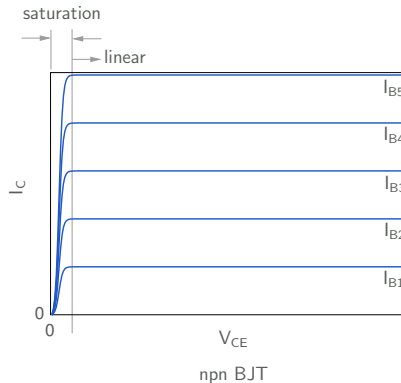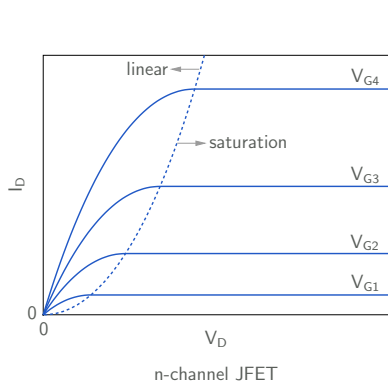Comparison of JFET and BJT I - V relationships




- * Note the different nomenclature for linear and saturation regions.
- * In a BJT, $V_{CE}^{\text{sat}} \approx 0.2 \text{ V}$ irrespective of I_B .
In a JFET, $V_D^{\text{sat}} (= V_G - V_P)$ depends on V_G .

Example

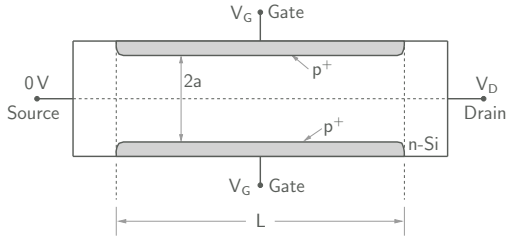

For an n -channel Si JFET with $N_d = 1 \times 10^{17} \text{ cm}^{-3}$, $\mu_n = 300 \text{ cm}^2/\text{V-s}$, $a = 0.2 \text{ } \mu\text{m}$, $L = 5 \text{ } \mu\text{m}$, $Z = 10 \text{ } \mu\text{m}$, $V_{bi} = 0.9 \text{ V}$ for the p^+n gate-to-channel junction,


Example

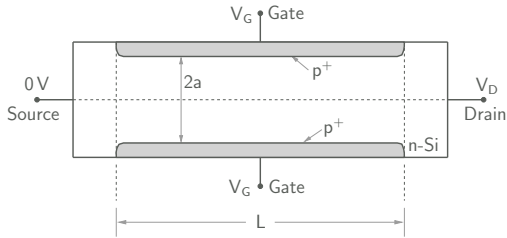

For an n -channel Si JFET with $N_d = 1 \times 10^{17} \text{ cm}^{-3}$, $\mu_n = 300 \text{ cm}^2/\text{V-s}$, $a = 0.2 \mu\text{m}$, $L = 5 \mu\text{m}$, $Z = 10 \mu\text{m}$, $V_{bi} = 0.9 \text{ V}$ for the p^+n gate-to-channel junction,

(a) What is the pinch-off voltage V_P ?


Example

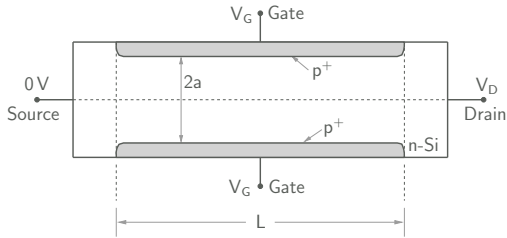

For an n -channel Si JFET with $N_d = 1 \times 10^{17} \text{ cm}^{-3}$, $\mu_n = 300 \text{ cm}^2/\text{V-s}$, $a = 0.2 \mu\text{m}$, $L = 5 \mu\text{m}$, $Z = 10 \mu\text{m}$, $V_{bi} = 0.9 \text{ V}$ for the p^+n gate-to-channel junction,

- (a) What is the pinch-off voltage V_P ?
- (b) Plot I_D versus V_G for $-2.5 \text{ V} < V_G < 0 \text{ V}$ and with (i) $V_D = 0.1 \text{ V}$ and (ii) $V_D = 5 \text{ V}$.


Example

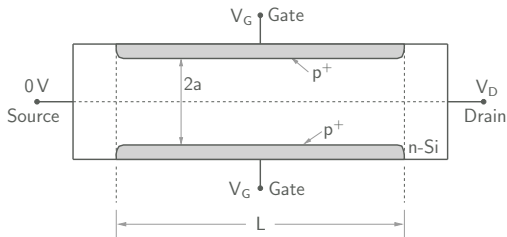

For an n -channel Si JFET with $N_d = 1 \times 10^{17} \text{ cm}^{-3}$, $\mu_n = 300 \text{ cm}^2/\text{V-s}$, $a = 0.2 \text{ } \mu\text{m}$, $L = 5 \text{ } \mu\text{m}$, $Z = 10 \text{ } \mu\text{m}$, $V_{bi} = 0.9 \text{ V}$ for the p^+n gate-to-channel junction,


- What is the pinch-off voltage V_P ?
- Plot I_D versus V_G for $-2.5 \text{ V} < V_G < 0 \text{ V}$ and with (i) $V_D = 0.1 \text{ V}$ and (ii) $V_D = 5 \text{ V}$.
- Plot I_D versus V_D for $0 \text{ V} < V_D < 5 \text{ V}$ and $V_G = -1.5, -1, -0.5, 0 \text{ V}$. Mark the boundary between the linear and saturation regions.

Example

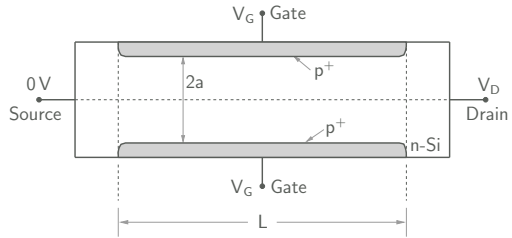

(a) $V_P = V_{bi} - \frac{qN_d}{2\epsilon} a^2 = -2.2 \text{ V}.$


Example

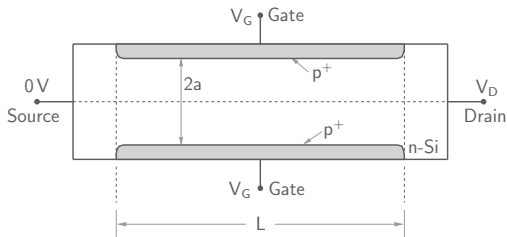

$$(a) \quad V_P = V_{bi} - \frac{qN_d}{2\epsilon} a^2 = -2.2 \text{ V}.$$

$$(b) \quad I_D = G_0 \left\{ V_D - \frac{2}{3} (V_{bi} - V_P) \left[\left(\frac{V_D + V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, \quad V_D < V_D^{\text{sat}}$$

Example

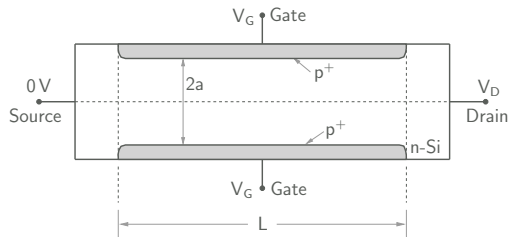


$$(a) \quad V_P = V_{bi} - \frac{qN_d}{2\epsilon} a^2 = -2.2 V.$$

$$(b) \quad I_D = G_0 \left\{ V_D - \frac{2}{3} (V_{bi} - V_P) \left[\left(\frac{V_D + V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, \quad V_D < V_D^{\text{sat}}$$

$$= G_0 \left\{ (V_G - V_P) - \frac{2}{3} (V_{bi} - V_P) \left[1 - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, \quad V_D > V_D^{\text{sat}}$$

Example

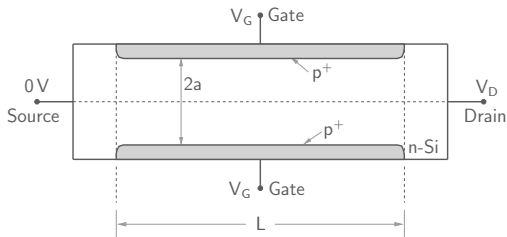


$$(a) \quad V_P = V_{bi} - \frac{qN_d}{2\epsilon} a^2 = -2.2 \text{ V}.$$

$$(b) \quad I_D = G_0 \left\{ V_D - \frac{2}{3} (V_{bi} - V_P) \left[\left(\frac{V_D + V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, \quad V_D < V_D^{\text{sat}}$$

$$= G_0 \left\{ (V_G - V_P) - \frac{2}{3} (V_{bi} - V_P) \left[1 - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, \quad V_D > V_D^{\text{sat}}$$

$$G_0 = \frac{2aZ}{L} q\mu_n N_d = \frac{2 \times 0.2 \times 10^{-4} \times 10 \times 10^{-4}}{5 \times 10^{-4}} \times 1.6 \times 10^{-19} \times 300 \times 10^{17} = 3.84 \times 10^{-4} \text{ V} = 0.384 \text{ mV}.$$

Example

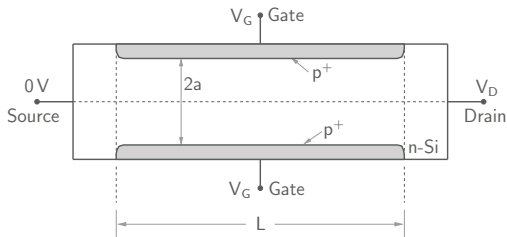

$$(a) \quad V_P = V_{bi} - \frac{qN_d}{2\epsilon} a^2 = -2.2 \text{ V}.$$



$$(b) \quad I_D = G_0 \left\{ V_D - \frac{2}{3} (V_{bi} - V_P) \left[\left(\frac{V_D + V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, \quad V_D < V_D^{\text{sat}}$$

$$= G_0 \left\{ (V_G - V_P) - \frac{2}{3} (V_{bi} - V_P) \left[1 - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, \quad V_D > V_D^{\text{sat}}$$



$$G_0 = \frac{2aZ}{L} q\mu_n N_d = \frac{2 \times 0.2 \times 10^{-4} \times 10 \times 10^{-4}}{5 \times 10^{-4}} \times 1.6 \times 10^{-19} \times 300 \times 10^{17} = 3.84 \times 10^{-4} \text{ } \mathcal{U} = 0.384 \text{ m}\mathcal{U}.$$

$$\text{Units: } \frac{\text{cm} \times \text{cm}}{\text{cm}} \times \text{Coul} \times \frac{\text{cm}^2}{\text{V-sec}} \times \frac{1}{\text{cm}^3} = \frac{\text{A}}{\text{V}} = \mathcal{U}.$$

Example

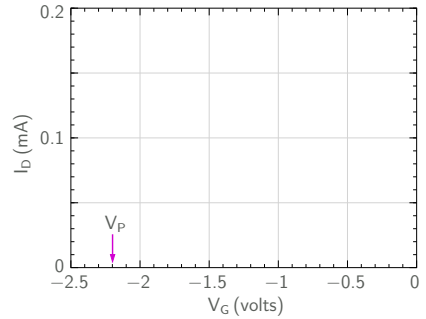
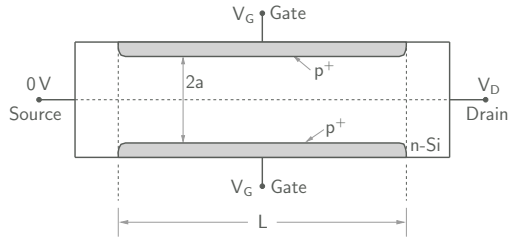


Example

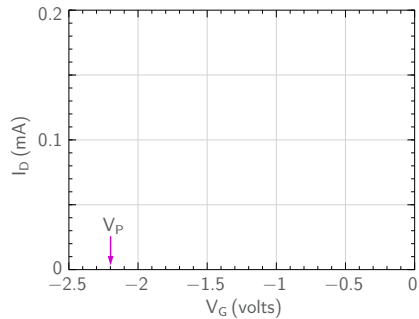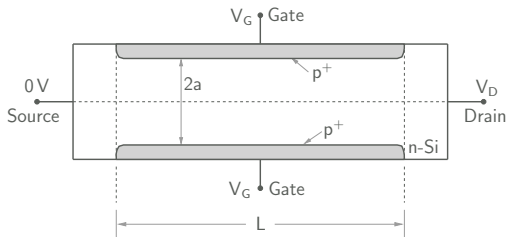

(b) For the transistor to be in the linear region, we need $V_G - V_D > V_P$, i.e., $V_G > V_P + V_D$.



Example

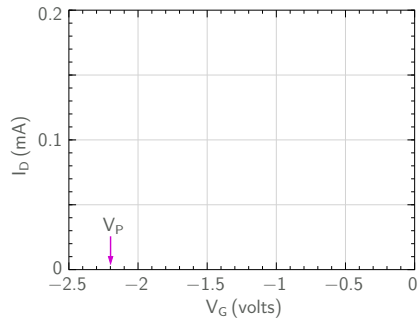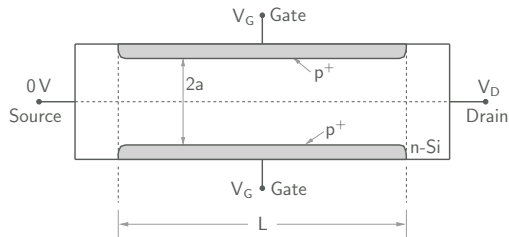

(b) For the transistor to be in the linear region, we need $V_G - V_D > V_P$, i.e., $V_G > V_P + V_D$.

(i) $V_D = 0.1$ V, $\rightarrow V_G > -2.2 + 0.1 = -2.1$ V for linear region.

Example

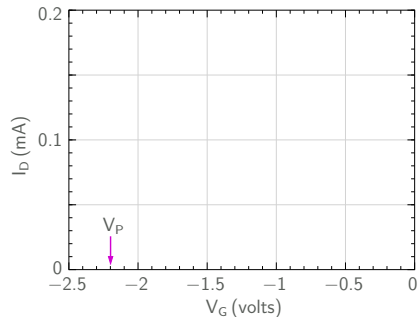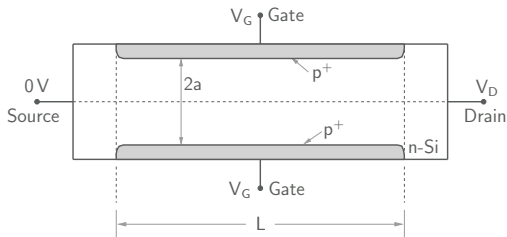



(b) For the transistor to be in the linear region, we need $V_G - V_D > V_P$, i.e., $V_G > V_P + V_D$.

(i) $V_D = 0.1 \text{ V}$, $\rightarrow V_G > -2.2 + 0.1 = -2.1 \text{ V}$ for linear region.

(ii) $V_D = 5 \text{ V}$, $\rightarrow V_G > -2.2 + 5 = 2.8 \text{ V}$ for linear region.

(Note: such a large V_G is not realistic.)

Example

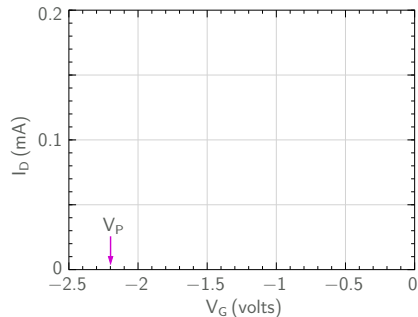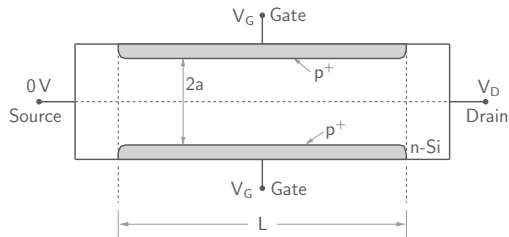

(b) For the transistor to be in the linear region, we need $V_G - V_D > V_P$, i.e., $V_G > V_P + V_D$.



(i) $V_D = 0.1$ V, $\rightarrow V_G > -2.2 + 0.1 = -2.1$ V for linear region.

(ii) $V_D = 5$ V, $\rightarrow V_G > -2.2 + 5 = 2.8$ V for linear region.

(Note: such a large V_G is not realistic.)

The I_D - V_G plot can now be obtained using the appropriate I_D expression.

Example

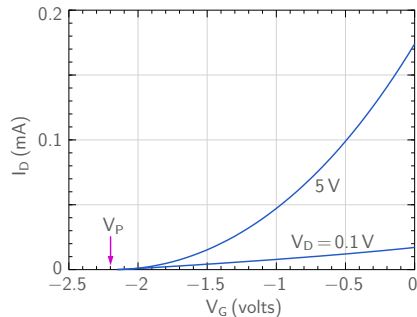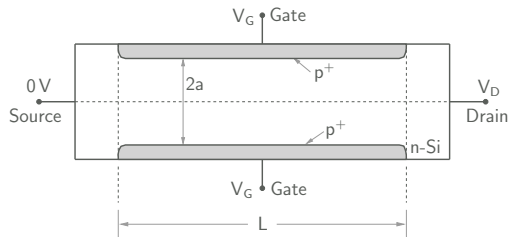

(b) For the transistor to be in the linear region, we need $V_G - V_D > V_P$, i.e., $V_G > V_P + V_D$.


(i) $V_D = 0.1V$, $\rightarrow V_G > -2.2 + 0.1 = -2.1V$ for linear region.

(ii) $V_D = 5V$, $\rightarrow V_G > -2.2 + 5 = 2.8V$ for linear region.


(Note: such a large V_G is not realistic.)

The I_D - V_G plot can now be obtained using the appropriate I_D expression.

Example

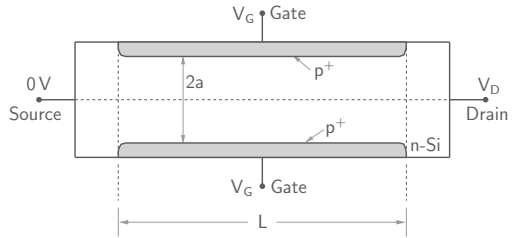


Example

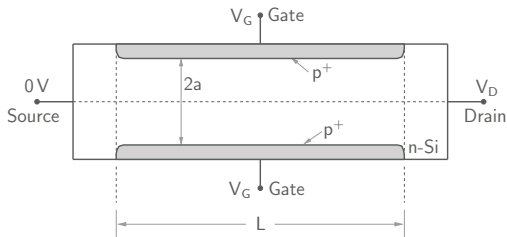

$$\begin{aligned}
 \text{(c) } I_D &= G_0 \left\{ V_D - \frac{2}{3} (V_{bi} - V_P) \left[\left(\frac{V_D + V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, & V_D < V_D^{\text{sat}} \\
 &= G_0 \left\{ (V_G - V_P) - \frac{2}{3} (V_{bi} - V_P) \left[1 - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, & V_D > V_D^{\text{sat}}
 \end{aligned}$$


Example

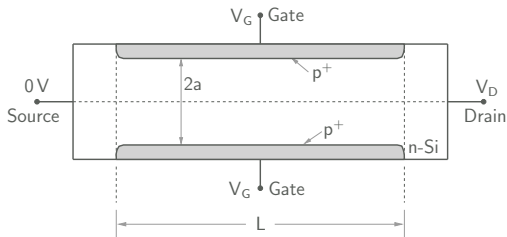

$$\begin{aligned}
 \text{(c) } I_D &= G_0 \left\{ V_D - \frac{2}{3} (V_{bi} - V_P) \left[\left(\frac{V_D + V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, \quad V_D < V_D^{\text{sat}} \\
 &= G_0 \left\{ (V_G - V_P) - \frac{2}{3} (V_{bi} - V_P) \left[1 - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, \quad V_D > V_D^{\text{sat}}
 \end{aligned}$$

For each V_G , we first find V_D^{sat} . For example, with $V_G = -1.5\text{V}$, $V_D^{\text{sat}} = V_G - V_P = -1.5 - (-2.2) = 0.7\text{V}$.

Example


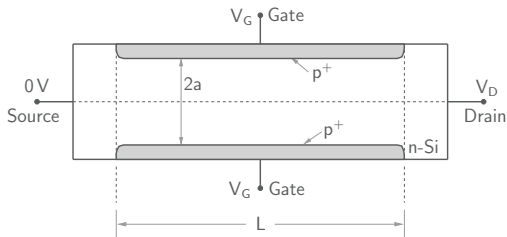


$$\begin{aligned}
 \text{(c) } I_D &= G_0 \left\{ V_D - \frac{2}{3} (V_{bi} - V_P) \left[\left(\frac{V_D + V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, & V_D < V_D^{\text{sat}} \\
 &= G_0 \left\{ (V_G - V_P) - \frac{2}{3} (V_{bi} - V_P) \left[1 - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, & V_D > V_D^{\text{sat}}
 \end{aligned}$$

For each V_G , we first find V_D^{sat} . For example, with $V_G = -1.5\text{V}$, $V_D^{\text{sat}} = V_G - V_P = -1.5 - (-2.2) = 0.7\text{V}$.

We then use the appropriate I_D expression to obtain the I_D - V_D plot for that particular V_G .

Example

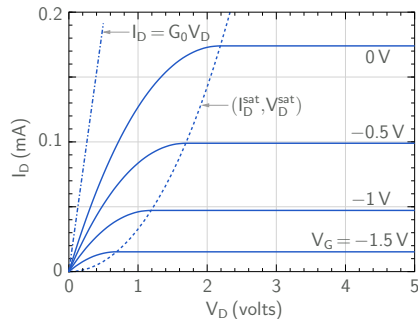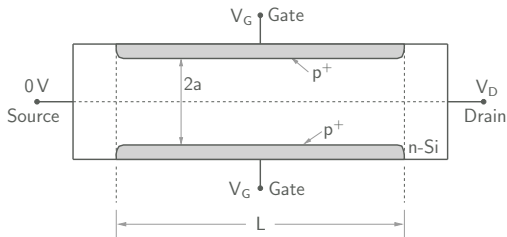


$$\begin{aligned}
 \text{(c) } I_D &= G_0 \left\{ V_D - \frac{2}{3} (V_{bi} - V_P) \left[\left(\frac{V_D + V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, & V_D < V_D^{\text{sat}} \\
 &= G_0 \left\{ (V_G - V_P) - \frac{2}{3} (V_{bi} - V_P) \left[1 - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}, & V_D > V_D^{\text{sat}}
 \end{aligned}$$


For each V_G , we first find V_D^{sat} . For example, with $V_G = -1.5V$, $V_D^{\text{sat}} = V_G - V_P = -1.5 - (-2.2) = 0.7V$.

We then use the appropriate I_D expression to obtain the I_D - V_D plot for that particular V_G .

JFET source/drain resistances

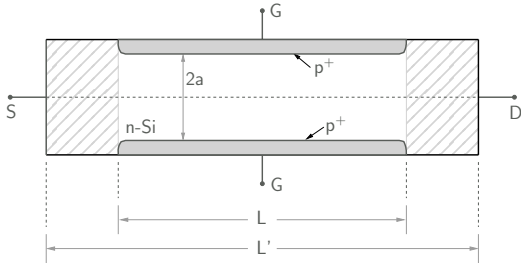


JFET source/drain resistances

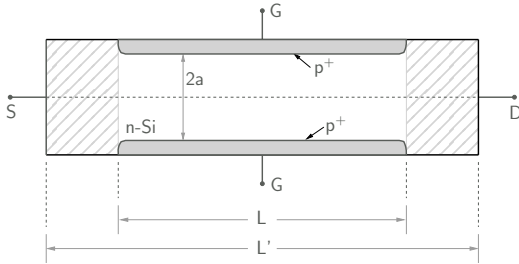


- * In a real JFET structure, the source and drain contacts are some distance away from the active part of the device, adding resistances R_S and R_D in the current path.

JFET source/drain resistances

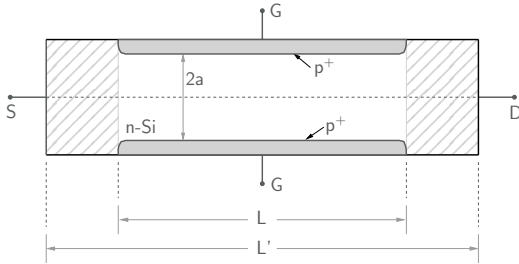


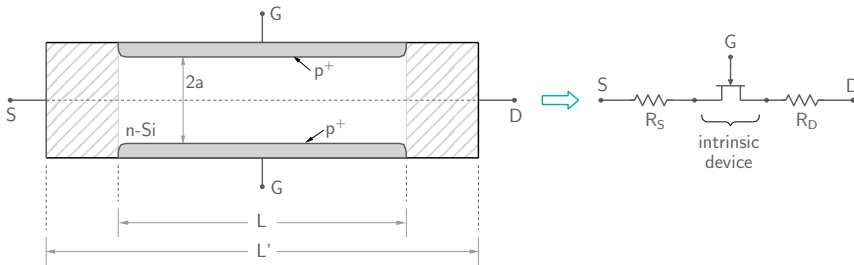- * In a real JFET structure, the source and drain contacts are some distance away from the active part of the device, adding resistances R_S and R_D in the current path.
- * The intrinsic device model needs to be augmented to include these resistances.




- * In a real JFET structure, the source and drain contacts are some distance away from the active part of the device, adding resistances R_S and R_D in the current path.
- * The intrinsic device model needs to be augmented to include these resistances.

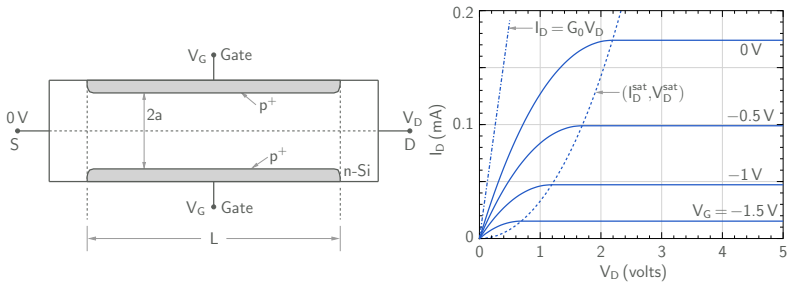Simplified JFET model for circuit analysis




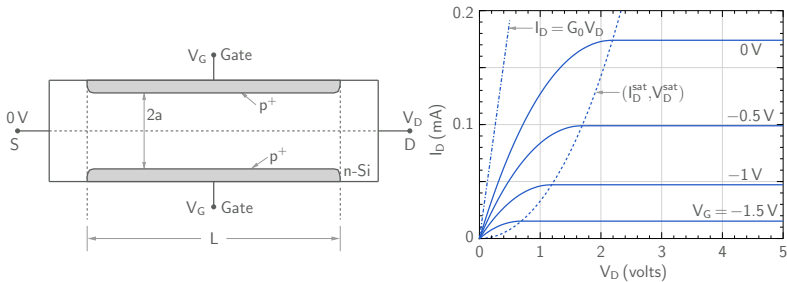Simplified JFET model for circuit analysis



- * When a JFET is used for amplification, it is biased in the saturation region, and the saturation current I_D^{sat} at a given V_G is of interest.

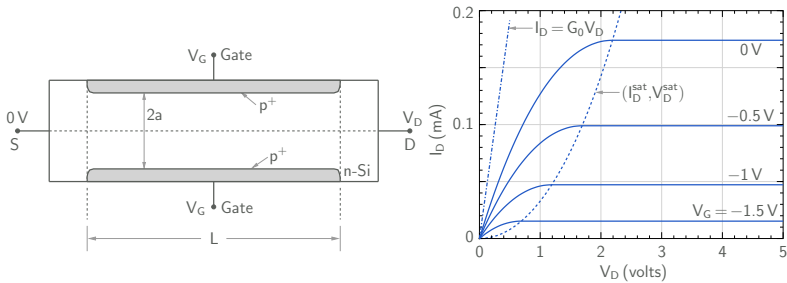
Simplified JFET model for circuit analysis



* When a JFET is used for amplification, it is biased in the saturation region, and the saturation current I_D^{sat} at a given V_G is of interest.

$$* I_D^{sat}(V_G) = G_0 \left\{ (V_G - V_P) - \frac{2}{3} (V_{bi} - V_P) \left[1 - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}.$$



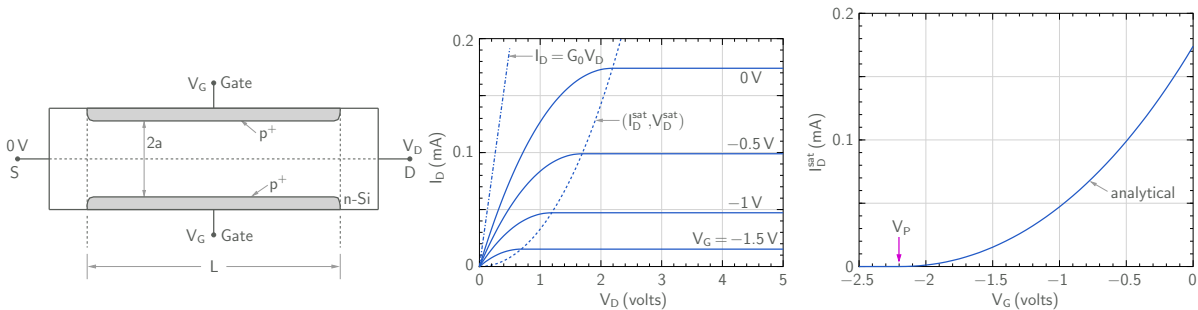
Simplified JFET model for circuit analysis



* When a JFET is used for amplification, it is biased in the saturation region, and the saturation current I_D^{sat} at a given V_G is of interest.

$$* I_D^{\text{sat}}(V_G) = G_0 \left\{ (V_G - V_P) - \frac{2}{3} (V_{bi} - V_P) \left[1 - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}.$$

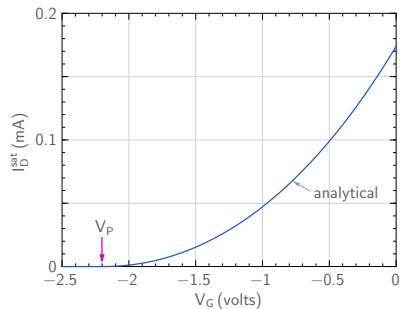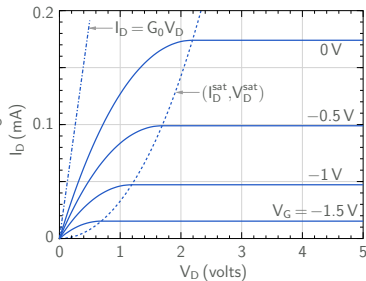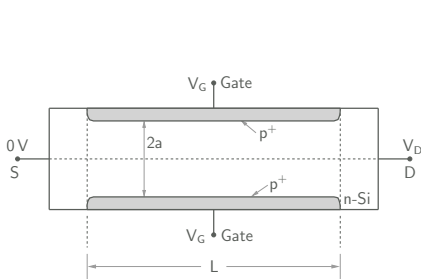Simplified JFET model for circuit analysis






* When a JFET is used for amplification, it is biased in the saturation region, and the saturation current I_D^{sat} at a given V_G is of interest.

$$* I_D^{sat}(V_G) = G_0 \left\{ (V_G - V_P) - \frac{2}{3} (V_{bi} - V_P) \left[1 - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}.$$

* For circuit design, we can use a simplified empirical expression for I_D^{sat} :

$$I_D^{sat}(V_G) = I_{DSS} [1 - (V_G/V_P)]^2, \quad \text{where } I_{DSS} = I_D^{sat}|_{V_G=0V}.$$

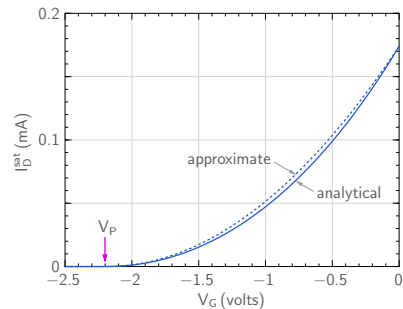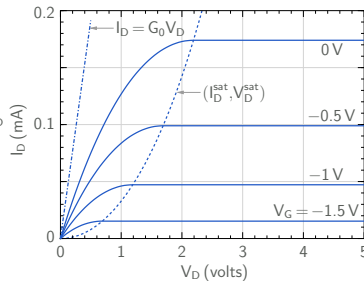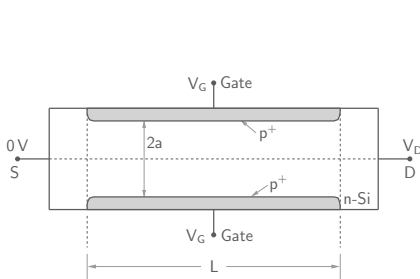Simplified JFET model for circuit analysis




- * When a JFET is used for amplification, it is biased in the saturation region, and the saturation current I_D^{sat} at a given V_G is of interest.

$$* I_D^{\text{sat}}(V_G) = G_0 \left\{ (V_G - V_P) - \frac{2}{3} (V_{bi} - V_P) \left[1 - \left(\frac{V_{bi} - V_G}{V_{bi} - V_P} \right)^{3/2} \right] \right\}.$$


- * For circuit design, we can use a simplified empirical expression for I_D^{sat} :

$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_G/V_P)]^2, \quad \text{where } I_{DSS} = I_D^{\text{sat}}|_{V_G=0V}.$$

JFET small-signal model

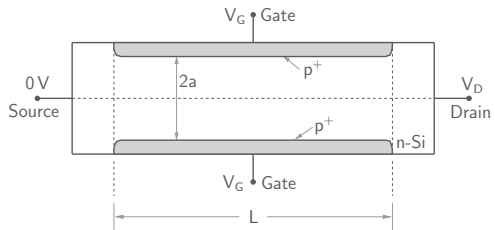


JFET small-signal model

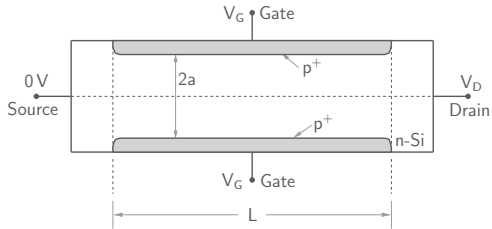

In an amplifier, a JFET is biased in saturation, and we have

$$I_D^{\text{sat}} = I_{DSS} [1 - (V_G/V_P)]^2.$$


JFET small-signal model

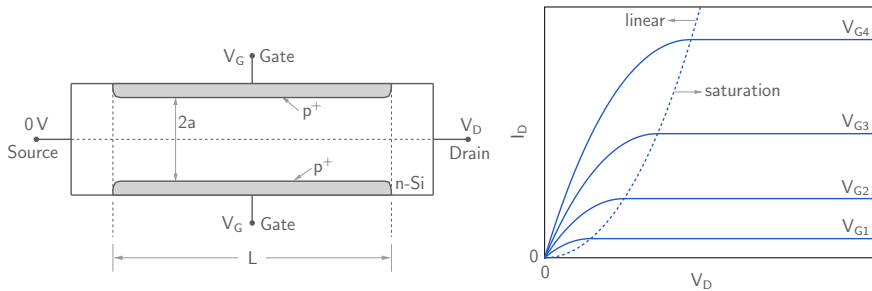

In an amplifier, a JFET is biased in saturation, and we have

$$I_D^{\text{sat}} = I_{DSS} [1 - (V_G/V_P)]^2.$$

JFET small-signal model

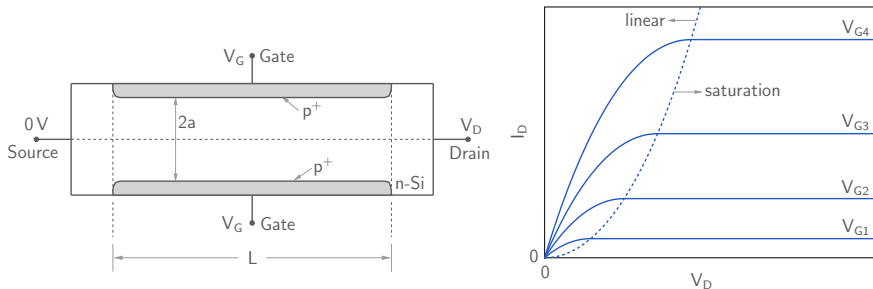


In an amplifier, a JFET is biased in saturation, and we have

$$I_D^{\text{sat}} = I_{DSS} [1 - (V_G/V_P)]^2.$$

The small-signal model at low frequencies can be derived as follows (with source at 0 V).

$$\Delta I_D = \frac{\partial I_D}{\partial V_G} \Delta V_G + \frac{\partial I_D}{\partial V_D} \Delta V_D.$$

JFET small-signal model

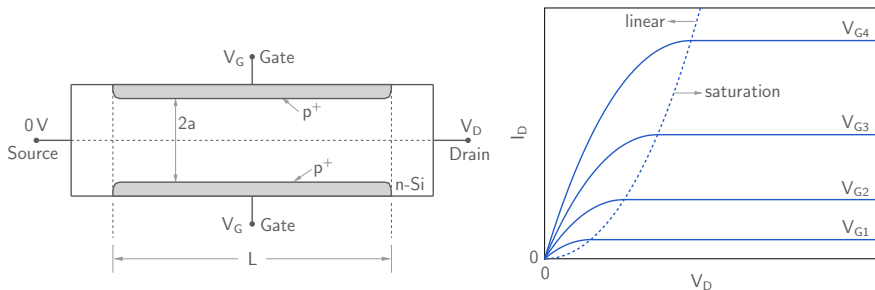

In an amplifier, a JFET is biased in saturation, and we have




$$I_D^{\text{sat}} = I_{DSS} \left[1 - (V_G/V_P) \right]^2.$$

The small-signal model at low frequencies can be derived as follows (with source at $0V$).

$$\Delta I_D = \frac{\partial I_D}{\partial V_G} \Delta V_G + \frac{\partial I_D}{\partial V_D} \Delta V_D.$$

$$\rightarrow i_d = g_m v_g, \text{ with } g_m = \frac{\partial I_D}{\partial V_G} = -\frac{2I_{DSS}}{V_P} \left(1 - \frac{V_G}{V_P} \right).$$

JFET small-signal model

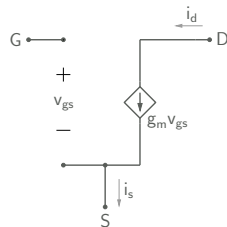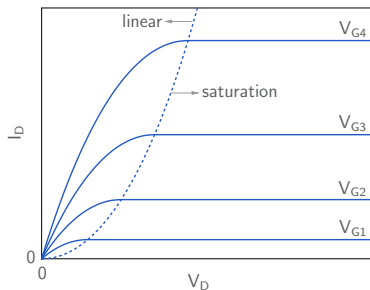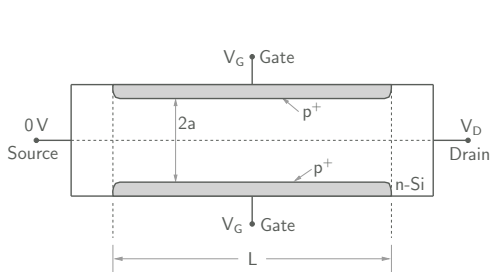

Small-signal model

In an amplifier, a JFET is biased in saturation, and we have


$$I_D^{\text{sat}} = I_{DSS} [1 - (V_G/V_P)]^2.$$

The small-signal model at low frequencies can be derived as follows (with source at 0V).

$$\Delta I_D = \frac{\partial I_D}{\partial V_G} \Delta V_G + \frac{\partial I_D}{\partial V_D} \Delta V_D.$$

$$\rightarrow i_d = g_m v_g, \text{ with } g_m = \frac{\partial I_D}{\partial V_G} = -\frac{2I_{DSS}}{V_P} \left(1 - \frac{V_G}{V_P}\right).$$

JFET small-signal model

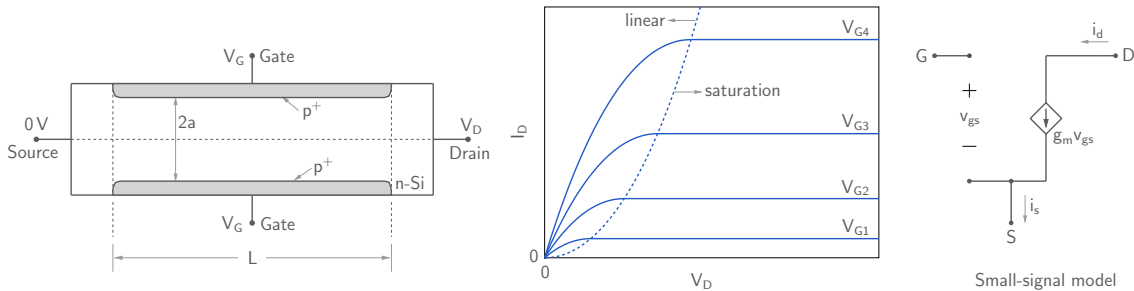

In an amplifier, a JFET is biased in saturation, and we have


$$I_D^{\text{sat}} = I_{DSS} [1 - (V_G/V_P)]^2.$$

The small-signal model at low frequencies can be derived as follows (with source at 0V).

$$\Delta I_D = \frac{\partial I_D}{\partial V_G} \Delta V_G + \frac{\partial I_D}{\partial V_D} \Delta V_D.$$


$$\rightarrow i_d = g_m v_g, \text{ with } g_m = \frac{\partial I_D}{\partial V_G} = -\frac{2I_{DSS}}{V_P} \left(1 - \frac{V_G}{V_P}\right).$$

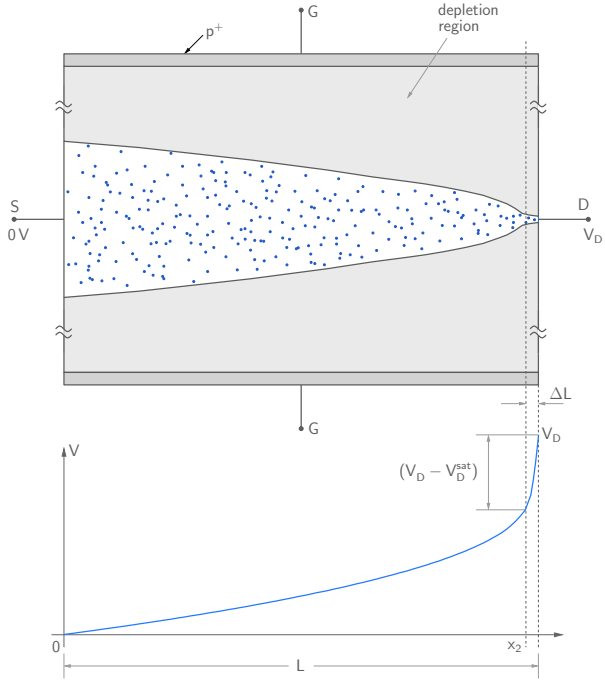(Note that there is a reverse biased *pn* junction between G and S and between G and D. $\rightarrow i_g = 0$.)



Channel length modulation:

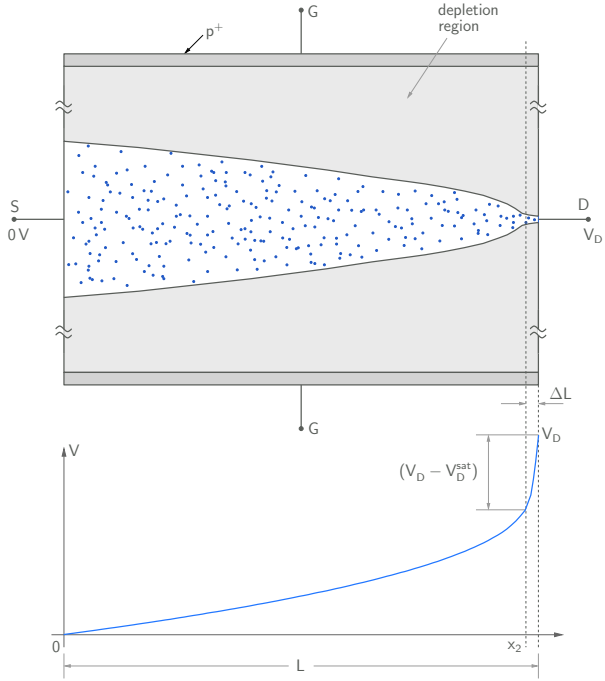- * In saturation, the actual channel length is $L_{\text{eff}} = L - \Delta L$.





Channel length modulation:

* In saturation, the actual channel length is

$$L_{\text{eff}} = L - \Delta L.$$

$$V_D \uparrow \rightarrow \Delta L \uparrow \rightarrow L_{\text{eff}} \downarrow$$
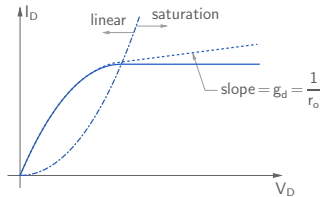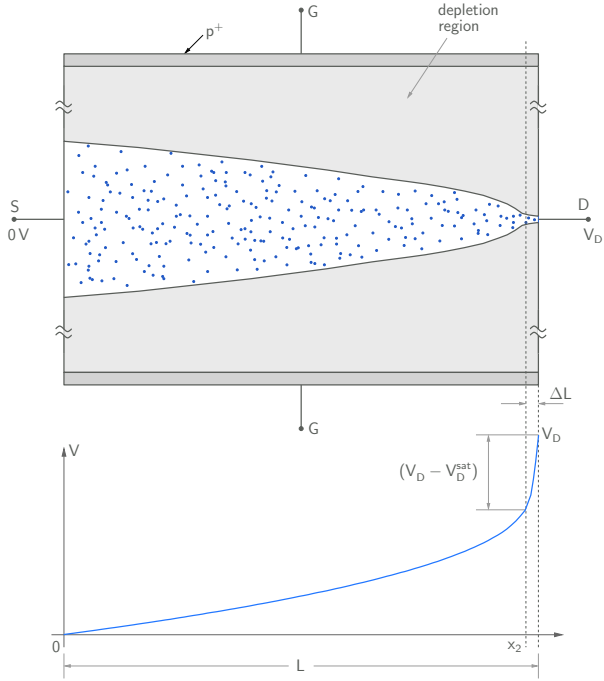
$$\rightarrow G_0 \left(= \frac{(2aZ)}{L_{\text{eff}}} \times (q\mu_n N_d) \right) \uparrow \rightarrow I_D \uparrow$$






Channel length modulation:

* In saturation, the actual channel length is

$$L_{\text{eff}} = L - \Delta L.$$

$$V_D \uparrow \rightarrow \Delta L \uparrow \rightarrow L_{\text{eff}} \downarrow$$
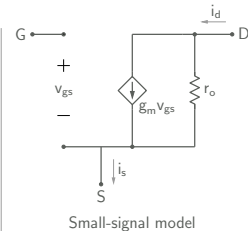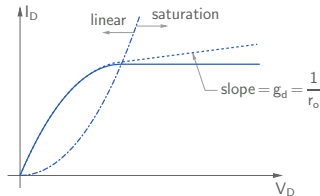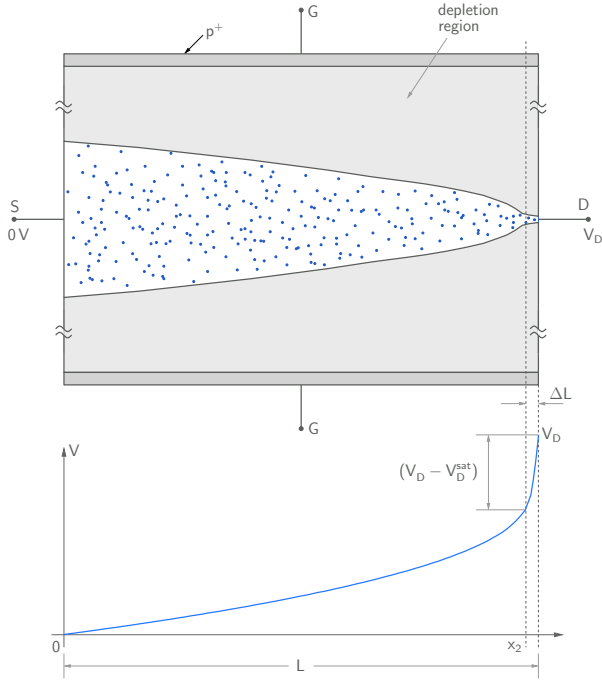
$$\rightarrow G_0 \left(= \frac{(2aZ)}{L_{\text{eff}}} \times (q\mu_n N_d) \right) \uparrow \rightarrow I_D \uparrow$$



Channel length modulation:

- * In saturation, the actual channel length is


$$L_{\text{eff}} = L - \Delta L.$$

$$V_D \uparrow \rightarrow \Delta L \uparrow \rightarrow L_{\text{eff}} \downarrow$$



$$\rightarrow G_0 \left(= \frac{2aZ}{L_{\text{eff}}} \times (q\mu_n N_d) \right) \uparrow \rightarrow I_D \uparrow$$

- * This "channel length modulation" is significant in short-channel devices ($L \sim 1 \mu\text{m}$).


JFET: small-signal model

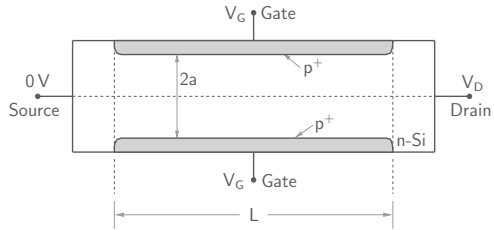

JFET: small-signal model

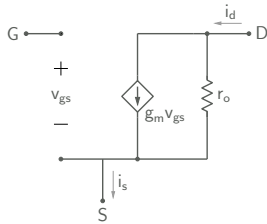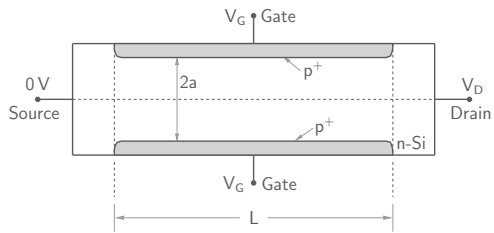


JFET: small-signal model

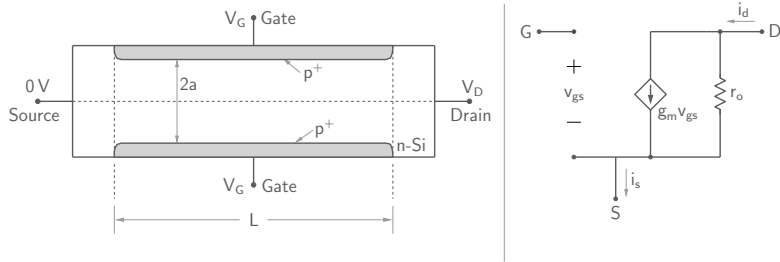


* At high frequencies, the device capacitances must be included in the small-signal model.

JFET: small-signal model

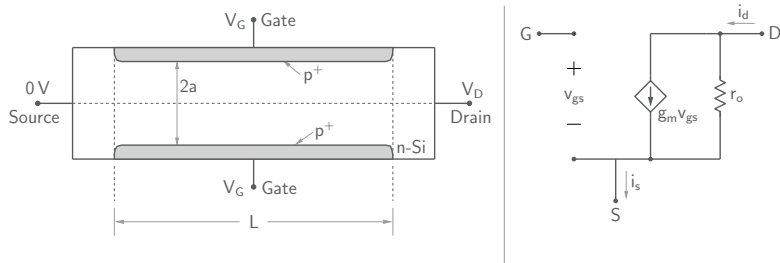





- * At high frequencies, the device capacitances must be included in the small-signal model.
- * The gate capacitance is essentially that of the gate-to-channel reverse-biased p^+n junction, which gets divided between C_{gs} and C_{gd} .

JFET: small-signal model


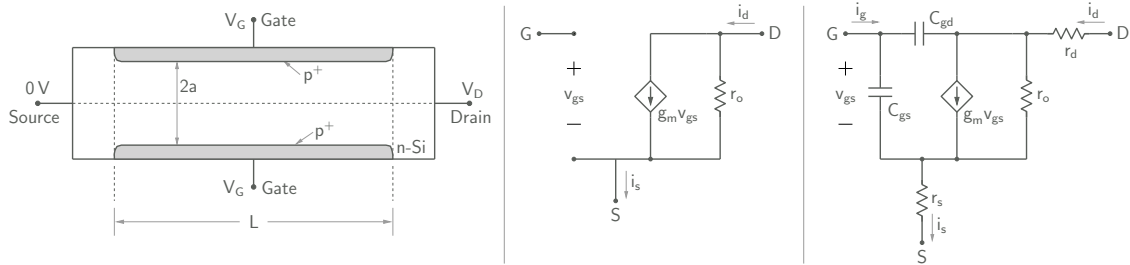


- * At high frequencies, the device capacitances must be included in the small-signal model.
- * The gate capacitance is essentially that of the gate-to-channel reverse-biased p^+n junction, which gets divided between C_{gs} and C_{gd} .



JFET amplifiers

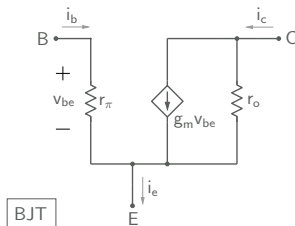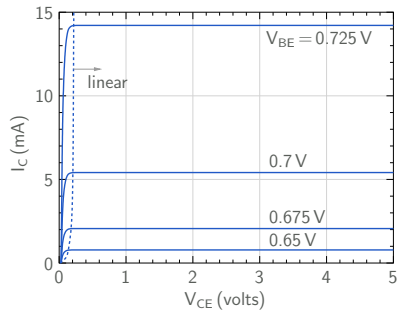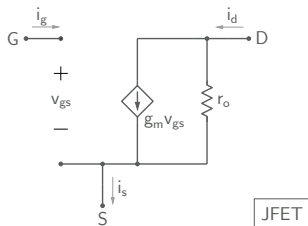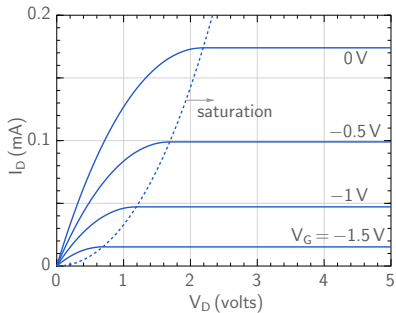

JFET amplifiers

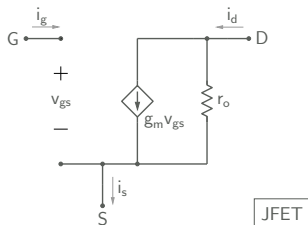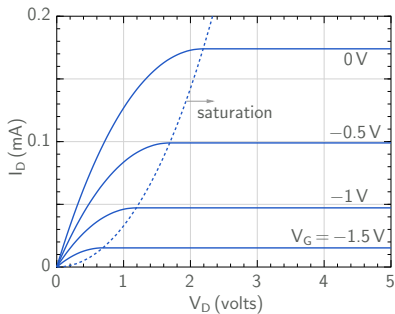



JFET

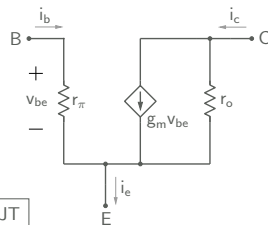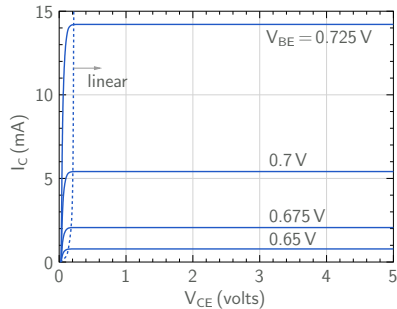



BJT

* Qualitatively, the I_D - V_{DS} relationship of a JFET is similar to the I_C - V_{CE} relationship of a BJT.

JFET amplifiers

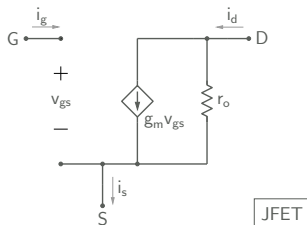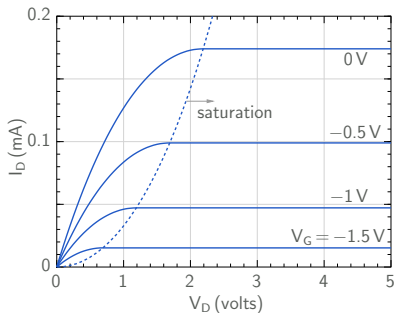

JFET

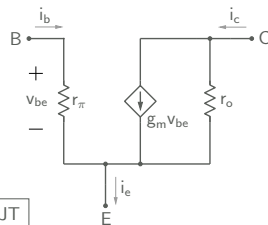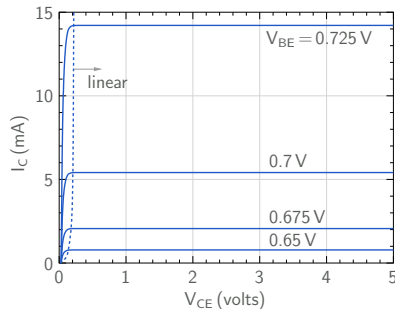

BJT


- * Qualitatively, the I_D - V_{DS} relationship of a JFET is similar to the I_C - V_{CE} relationship of a BJT.
- * A JFET can be used for amplification, e.g., we can have a "common-source" amplifier which is similar to the "common-emitter" amplifier.

JFET amplifiers

- * For amplification, a JFET needs to be biased in the saturation region, and the design goal is to bias it at a certain Q -point, (I_D, V_{DS}) .



JFET amplifiers

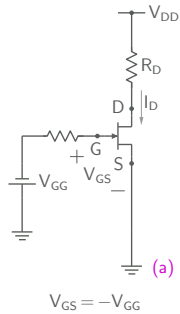- * For amplification, a JFET needs to be biased in the saturation region, and the design goal is to bias it at a certain Q -point, (I_D, V_{DS}) .






JFET amplifiers

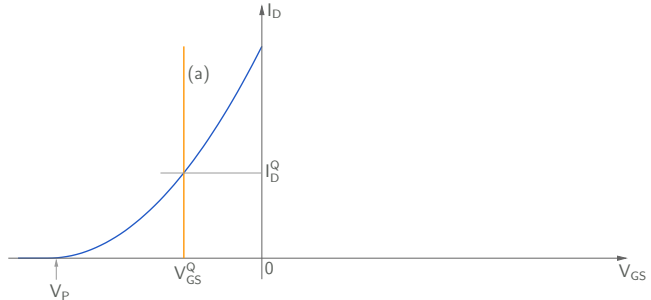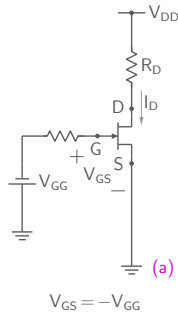- * For amplification, a JFET needs to be biased in the saturation region, and the design goal is to bias it at a certain Q -point, (I_D, V_{DS}) .






JFET amplifiers

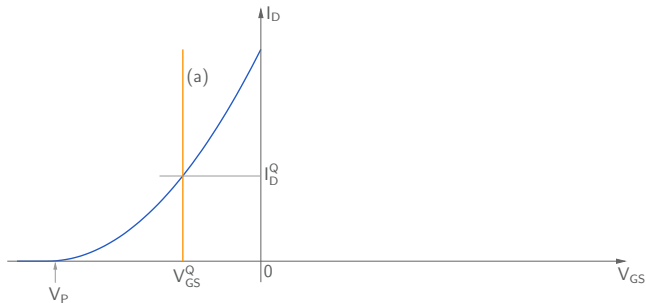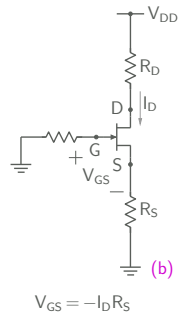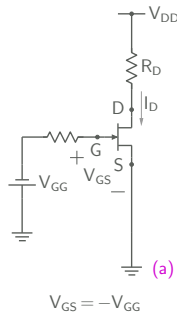- * For amplification, a JFET needs to be biased in the saturation region, and the design goal is to bias it at a certain Q -point, (I_D, V_{DS}) .







JFET amplifiers

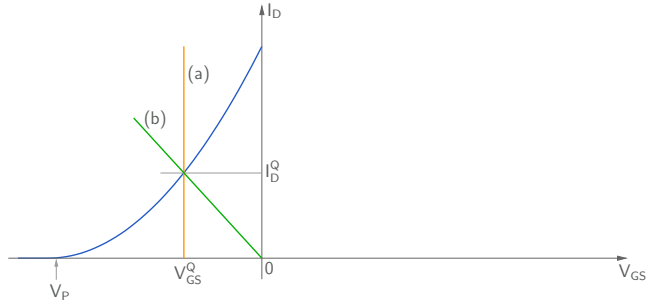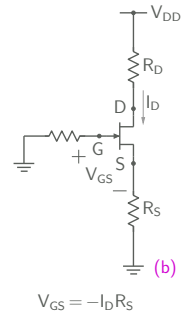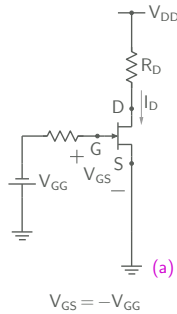- * For amplification, a JFET needs to be biased in the saturation region, and the design goal is to bias it at a certain Q -point, (I_D, V_{DS}) .





JFET amplifiers

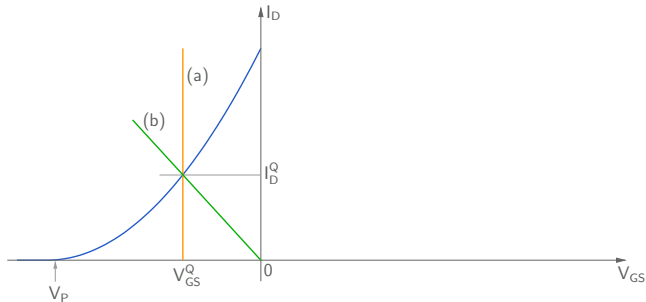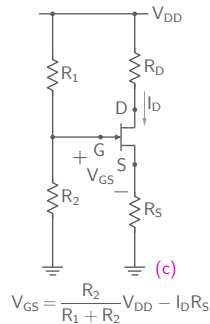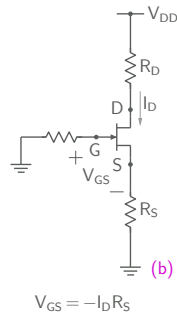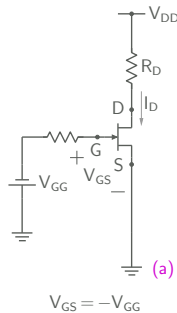- * For amplification, a JFET needs to be biased in the saturation region, and the design goal is to bias it at a certain Q -point, (I_D, V_{DS}) .



JFET amplifiers

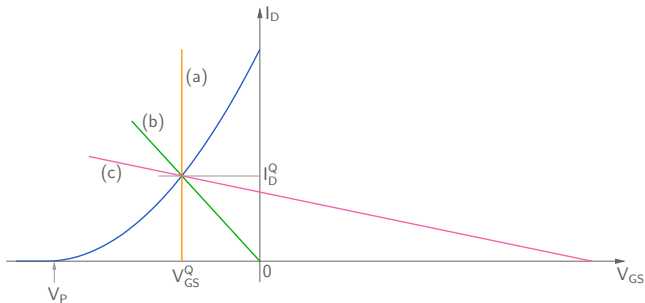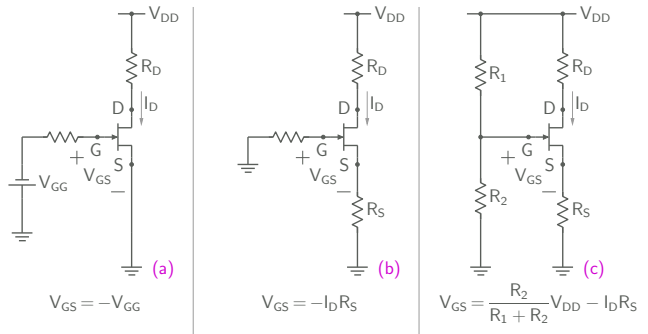- * For amplification, a JFET needs to be biased in the saturation region, and the design goal is to bias it at a certain Q -point, (I_D, V_{DS}) .



JFET amplifiers



- * For amplification, a JFET needs to be biased in the saturation region, and the design goal is to bias it at a certain Q -point, (I_D, V_{DS}) .

- * The drain current equation,

$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_G/V_P)]^2,$$

implies that there is a unique I_D for a given V_{GS} .

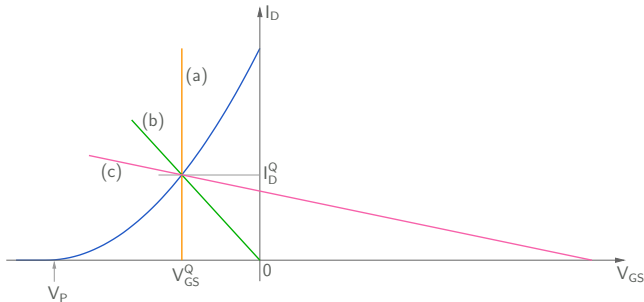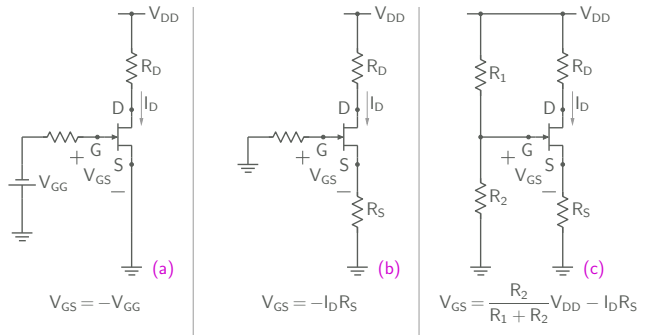However, there is a device-to-device variation in the I_D - V_{GS} curve, giving rise to some deviation from the intended bias point.



JFET amplifiers



- * For amplification, a JFET needs to be biased in the saturation region, and the design goal is to bias it at a certain Q -point, (I_D, V_{DS}) .

- * The drain current equation,

$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_G/V_P)]^2,$$

implies that there is a unique I_D for a given V_{GS} .

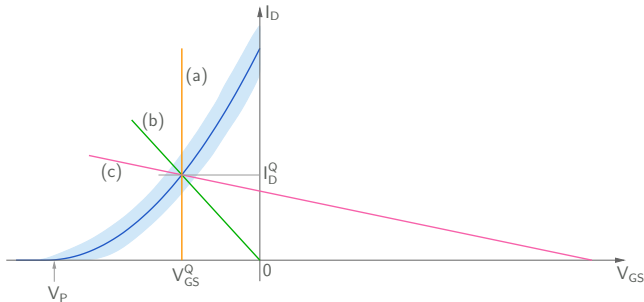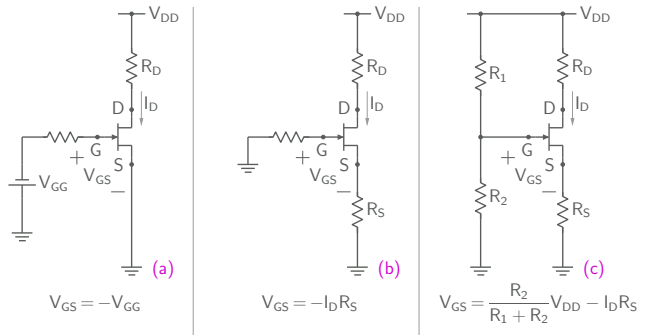However, there is a device-to-device variation in the I_D - V_{GS} curve, giving rise to some deviation from the intended bias point.



JFET amplifiers

- * For amplification, a JFET needs to be biased in the saturation region, and the design goal is to bias it at a certain Q -point, (I_D, V_{DS}) .



- * The drain current equation,

$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_G/V_P)]^2,$$

implies that there is a unique I_D for a given V_{GS} .


However, there is a device-to-device variation in the I_D - V_{GS} curve, giving rise to some deviation from the intended bias point.

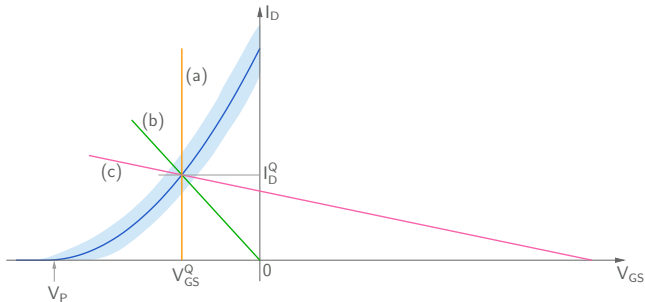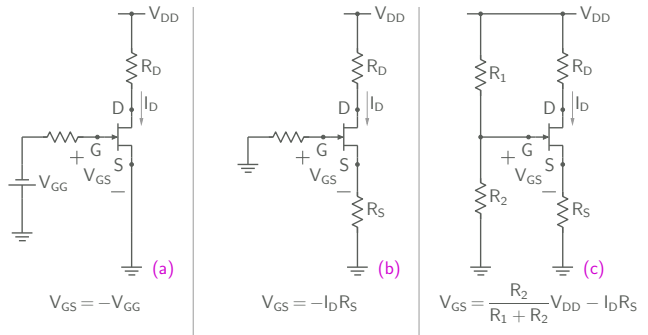- * The voltage divider scheme (c) is superior since it is least sensitive, i.e., the deviation in I_D is small compared to the other schemes.



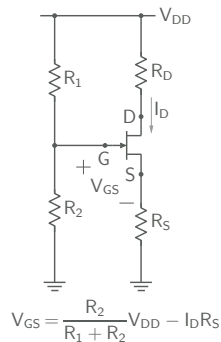Example

The JFET parameters are $I_{DSS} = 1 \text{ mA}$, $V_P = -2 \text{ V}$. For $V_{DD} = 12 \text{ V}$ and $R_D = 15 \text{ k}\Omega$, find suitable values of R_1 , R_2 , R_S to get a bias point of $I_D^Q = 0.4 \text{ mA}$ and $V_{DS}^Q = 4 \text{ V}$.




Example

The JFET parameters are $I_{DSS} = 1 \text{ mA}$, $V_P = -2 \text{ V}$. For $V_{DD} = 12 \text{ V}$ and $R_D = 15 \text{ k}\Omega$, find suitable values of R_1 , R_2 , R_S to get a bias point of $I_D^Q = 0.4 \text{ mA}$ and $V_{DS}^Q = 4 \text{ V}$.

Solution: The drain current in the saturation region is given by
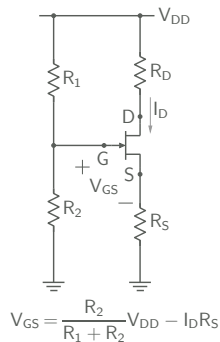
$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_{GS}/V_P)]^2.$$




Example

The JFET parameters are $I_{DSS} = 1 \text{ mA}$, $V_P = -2 \text{ V}$. For $V_{DD} = 12 \text{ V}$ and $R_D = 15 \text{ k}\Omega$, find suitable values of R_1 , R_2 , R_S to get a bias point of $I_D^Q = 0.4 \text{ mA}$ and $V_{DS}^Q = 4 \text{ V}$.

Solution: The drain current in the saturation region is given by

$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_{GS}/V_P)]^2.$$

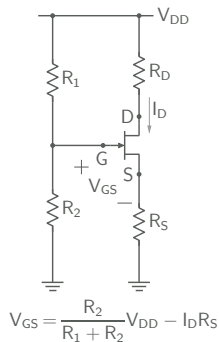Solving for $I_D^{\text{sat}} = I_D^Q = 0.4 \text{ mA}$, we get $V_{GS}^Q = -0.735 \text{ V}$.



Example


The JFET parameters are $I_{DSS} = 1 \text{ mA}$, $V_P = -2 \text{ V}$. For $V_{DD} = 12 \text{ V}$ and $R_D = 15 \text{ k}\Omega$, find suitable values of R_1 , R_2 , R_S to get a bias point of $I_D^Q = 0.4 \text{ mA}$ and $V_{DS}^Q = 4 \text{ V}$.

Solution: The drain current in the saturation region is given by

$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_{GS}/V_P)]^2.$$

Solving for $I_D^{\text{sat}} = I_D^Q = 0.4 \text{ mA}$, we get $V_{GS}^Q = -0.735 \text{ V}$.
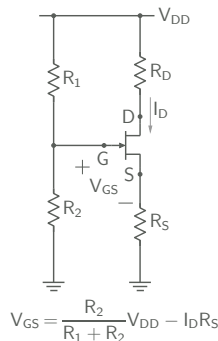
$$V_D = V_{DD} - I_D R_D = 12 \text{ V} - 0.4 \text{ mA} \times 15 \text{ k} = 6 \text{ V}.$$



Example

The JFET parameters are $I_{DSS} = 1 \text{ mA}$, $V_P = -2 \text{ V}$. For $V_{DD} = 12 \text{ V}$ and $R_D = 15 \text{ k}\Omega$, find suitable values of R_1 , R_2 , R_S to get a bias point of $I_D^Q = 0.4 \text{ mA}$ and $V_{DS}^Q = 4 \text{ V}$.


Solution: The drain current in the saturation region is given by

$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_{GS}/V_P)]^2.$$

Solving for $I_D^{\text{sat}} = I_D^Q = 0.4 \text{ mA}$, we get $V_{GS}^Q = -0.735 \text{ V}$.

$$V_D = V_{DD} - I_D R_D = 12 \text{ V} - 0.4 \text{ mA} \times 15 \text{ k} = 6 \text{ V}.$$
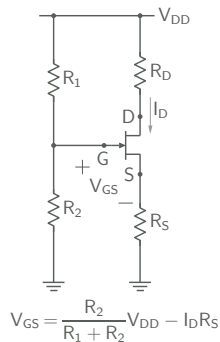
$$\rightarrow V_S = V_D - V_{DS}^Q = 6 \text{ V} - 4 \text{ V} = 2 \text{ V}$$



Example

The JFET parameters are $I_{DSS} = 1 \text{ mA}$, $V_P = -2 \text{ V}$. For $V_{DD} = 12 \text{ V}$ and $R_D = 15 \text{ k}\Omega$, find suitable values of R_1 , R_2 , R_S to get a bias point of $I_D^Q = 0.4 \text{ mA}$ and $V_{DS}^Q = 4 \text{ V}$.


Solution: The drain current in the saturation region is given by

$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_{GS}/V_P)]^2.$$

Solving for $I_D^{\text{sat}} = I_D^Q = 0.4 \text{ mA}$, we get $V_{GS}^Q = -0.735 \text{ V}$.

$$V_D = V_{DD} - I_D R_D = 12 \text{ V} - 0.4 \text{ mA} \times 15 \text{ k} = 6 \text{ V}.$$
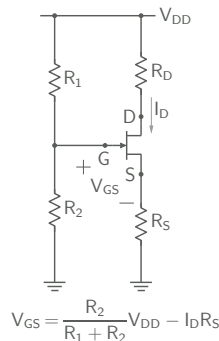
$$\rightarrow V_S = V_D - V_{DS}^Q = 6 \text{ V} - 4 \text{ V} = 2 \text{ V} \rightarrow R_S = V_S / I_D^Q = 2 \text{ V} / 0.4 \text{ mA} = 5 \text{ k}\Omega.$$



Example

The JFET parameters are $I_{DSS} = 1 \text{ mA}$, $V_P = -2 \text{ V}$. For $V_{DD} = 12 \text{ V}$ and $R_D = 15 \text{ k}\Omega$, find suitable values of R_1 , R_2 , R_S to get a bias point of $I_D^Q = 0.4 \text{ mA}$ and $V_{DS}^Q = 4 \text{ V}$.

Solution: The drain current in the saturation region is given by


$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_{GS}/V_P)]^2.$$

Solving for $I_D^{\text{sat}} = I_D^Q = 0.4 \text{ mA}$, we get $V_{GS}^Q = -0.735 \text{ V}$.

$$V_D = V_{DD} - I_D R_D = 12 \text{ V} - 0.4 \text{ mA} \times 15 \text{ k} = 6 \text{ V}.$$

$$\rightarrow V_S = V_D - V_{DS}^Q = 6 \text{ V} - 4 \text{ V} = 2 \text{ V} \rightarrow R_S = V_S / I_D^Q = 2 \text{ V} / 0.4 \text{ mA} = 5 \text{ k}\Omega.$$

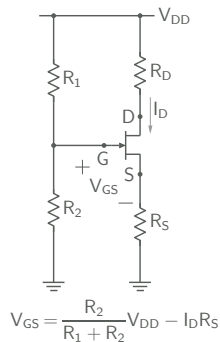For V_{GS} to be -0.735 V , we need $V_G = V_S + V_{GS} = 2 \text{ V} + (-0.735 \text{ V}) = 1.265 \text{ V}$.



Example

The JFET parameters are $I_{DSS} = 1 \text{ mA}$, $V_P = -2 \text{ V}$. For $V_{DD} = 12 \text{ V}$ and $R_D = 15 \text{ k}\Omega$, find suitable values of R_1 , R_2 , R_S to get a bias point of $I_D^Q = 0.4 \text{ mA}$ and $V_{DS}^Q = 4 \text{ V}$.

Solution: The drain current in the saturation region is given by

$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_{GS}/V_P)]^2.$$

Solving for $I_D^{\text{sat}} = I_D^Q = 0.4 \text{ mA}$, we get $V_{GS}^Q = -0.735 \text{ V}$.


$$V_D = V_{DD} - I_D R_D = 12 \text{ V} - 0.4 \text{ mA} \times 15 \text{ k} = 6 \text{ V}.$$

$$\rightarrow V_S = V_D - V_{DS}^Q = 6 \text{ V} - 4 \text{ V} = 2 \text{ V} \rightarrow R_S = V_S / I_D^Q = 2 \text{ V} / 0.4 \text{ mA} = 5 \text{ k}\Omega.$$

For V_{GS} to be -0.735 V , we need $V_G = V_S + V_{GS} = 2 \text{ V} + (-0.735 \text{ V}) = 1.265 \text{ V}$.

Since $V_G = \frac{R_2}{R_1 + R_2} V_{DD}$, we now need to choose suitable values of R_1 and R_2 to get

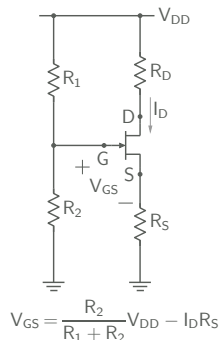the above V_G . $R_1 = 200 \text{ k}\Omega$ and $R_2 = 23.5 \text{ k}\Omega$ is one such choice.



Example

The JFET parameters are $I_{DSS} = 1 \text{ mA}$, $V_P = -2 \text{ V}$. For $V_{DD} = 12 \text{ V}$ and $R_D = 15 \text{ k}\Omega$, find suitable values of R_1 , R_2 , R_S to get a bias point of $I_D^Q = 0.4 \text{ mA}$ and $V_{DS}^Q = 4 \text{ V}$.

Solution: The drain current in the saturation region is given by

$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_{GS}/V_P)]^2.$$

Solving for $I_D^{\text{sat}} = I_D^Q = 0.4 \text{ mA}$, we get $V_{GS}^Q = -0.735 \text{ V}$.

$$V_D = V_{DD} - I_D R_D = 12 \text{ V} - 0.4 \text{ mA} \times 15 \text{ k} = 6 \text{ V}.$$


$$\rightarrow V_S = V_D - V_{DS}^Q = 6 \text{ V} - 4 \text{ V} = 2 \text{ V} \rightarrow R_S = V_S / I_D^Q = 2 \text{ V} / 0.4 \text{ mA} = 5 \text{ k}\Omega.$$

For V_{GS} to be -0.735 V , we need $V_G = V_S + V_{GS} = 2 \text{ V} + (-0.735 \text{ V}) = 1.265 \text{ V}$.

Since $V_G = \frac{R_2}{R_1 + R_2} V_{DD}$, we now need to choose suitable values of R_1 and R_2 to get

the above V_G . $R_1 = 200 \text{ k}\Omega$ and $R_2 = 23.5 \text{ k}\Omega$ is one such choice.

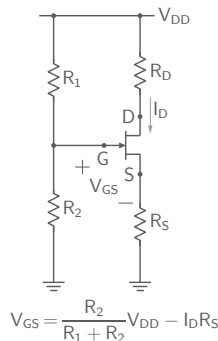Finally, we check whether the transistor is indeed biased in saturation.



Example

The JFET parameters are $I_{DSS} = 1 \text{ mA}$, $V_P = -2 \text{ V}$. For $V_{DD} = 12 \text{ V}$ and $R_D = 15 \text{ k}\Omega$, find suitable values of R_1 , R_2 , R_S to get a bias point of $I_D^Q = 0.4 \text{ mA}$ and $V_{DS}^Q = 4 \text{ V}$.

Solution: The drain current in the saturation region is given by

$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_{GS}/V_P)]^2.$$

Solving for $I_D^{\text{sat}} = I_D^Q = 0.4 \text{ mA}$, we get $V_{GS}^Q = -0.735 \text{ V}$.

$$V_D = V_{DD} - I_D R_D = 12 \text{ V} - 0.4 \text{ mA} \times 15 \text{ k} = 6 \text{ V}.$$

$$\rightarrow V_S = V_D - V_{DS}^Q = 6 \text{ V} - 4 \text{ V} = 2 \text{ V} \rightarrow R_S = V_S / I_D^Q = 2 \text{ V} / 0.4 \text{ mA} = 5 \text{ k}\Omega.$$


For V_{GS} to be -0.735 V , we need $V_G = V_S + V_{GS} = 2 \text{ V} + (-0.735 \text{ V}) = 1.265 \text{ V}$.

Since $V_G = \frac{R_2}{R_1 + R_2} V_{DD}$, we now need to choose suitable values of R_1 and R_2 to get

the above V_G . $R_1 = 200 \text{ k}\Omega$ and $R_2 = 23.5 \text{ k}\Omega$ is one such choice.

Finally, we check whether the transistor is indeed biased in saturation.

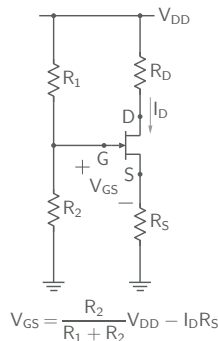For saturation, we need $V_{GS} - V_{DS} < V_P$,



Example

The JFET parameters are $I_{DSS} = 1 \text{ mA}$, $V_P = -2 \text{ V}$. For $V_{DD} = 12 \text{ V}$ and $R_D = 15 \text{ k}\Omega$, find suitable values of R_1 , R_2 , R_S to get a bias point of $I_D^Q = 0.4 \text{ mA}$ and $V_{DS}^Q = 4 \text{ V}$.

Solution: The drain current in the saturation region is given by

$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_{GS}/V_P)]^2.$$

Solving for $I_D^{\text{sat}} = I_D^Q = 0.4 \text{ mA}$, we get $V_{GS}^Q = -0.735 \text{ V}$.

$$V_D = V_{DD} - I_D R_D = 12 \text{ V} - 0.4 \text{ mA} \times 15 \text{ k} = 6 \text{ V}.$$

$$\rightarrow V_S = V_D - V_{DS}^Q = 6 \text{ V} - 4 \text{ V} = 2 \text{ V} \rightarrow R_S = V_S / I_D^Q = 2 \text{ V} / 0.4 \text{ mA} = 5 \text{ k}\Omega.$$


For V_{GS} to be -0.735 V , we need $V_G = V_S + V_{GS} = 2 \text{ V} + (-0.735 \text{ V}) = 1.265 \text{ V}$.

Since $V_G = \frac{R_2}{R_1 + R_2} V_{DD}$, we now need to choose suitable values of R_1 and R_2 to get

the above V_G . $R_1 = 200 \text{ k}\Omega$ and $R_2 = 23.5 \text{ k}\Omega$ is one such choice.

Finally, we check whether the transistor is indeed biased in saturation.

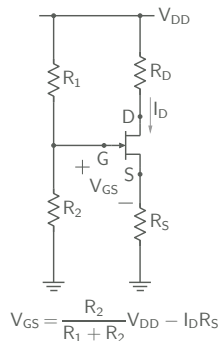For saturation, we need $V_{GS} - V_{DS} < V_P$, i.e., $-0.735 - 4 < -2 \text{ V}$.



Example

The JFET parameters are $I_{DSS} = 1 \text{ mA}$, $V_P = -2 \text{ V}$. For $V_{DD} = 12 \text{ V}$ and $R_D = 15 \text{ k}\Omega$, find suitable values of R_1 , R_2 , R_S to get a bias point of $I_D^Q = 0.4 \text{ mA}$ and $V_{DS}^Q = 4 \text{ V}$.

Solution: The drain current in the saturation region is given by

$$I_D^{\text{sat}}(V_G) = I_{DSS} [1 - (V_{GS}/V_P)]^2.$$

Solving for $I_D^{\text{sat}} = I_D^Q = 0.4 \text{ mA}$, we get $V_{GS}^Q = -0.735 \text{ V}$.

$$V_D = V_{DD} - I_D R_D = 12 \text{ V} - 0.4 \text{ mA} \times 15 \text{ k} = 6 \text{ V}.$$

$$\rightarrow V_S = V_D - V_{DS}^Q = 6 \text{ V} - 4 \text{ V} = 2 \text{ V} \rightarrow R_S = V_S / I_D^Q = 2 \text{ V} / 0.4 \text{ mA} = 5 \text{ k}\Omega.$$


For V_{GS} to be -0.735 V , we need $V_G = V_S + V_{GS} = 2 \text{ V} + (-0.735 \text{ V}) = 1.265 \text{ V}$.

Since $V_G = \frac{R_2}{R_1 + R_2} V_{DD}$, we now need to choose suitable values of R_1 and R_2 to get


the above V_G . $R_1 = 200 \text{ k}\Omega$ and $R_2 = 23.5 \text{ k}\Omega$ is one such choice.

Finally, we check whether the transistor is indeed biased in saturation.

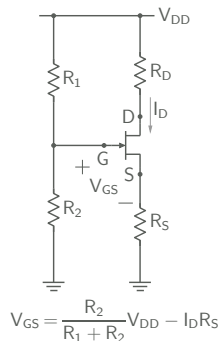
For saturation, we need $V_{GS} - V_{DS} < V_P$, i.e., $-0.735 - 4 < -2 \text{ V}$. ✓



Common-source amplifier

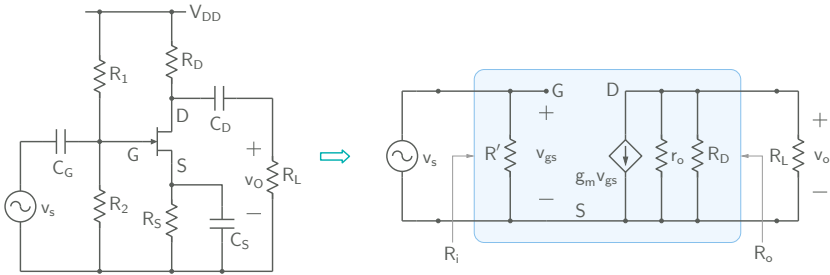


Common-source amplifier

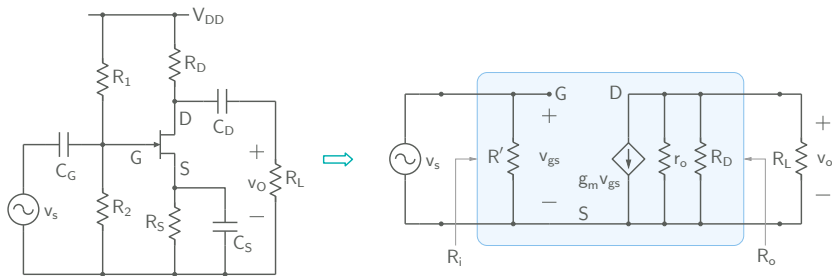

* $A_V \equiv \frac{v_o}{v_s} = -g_m(R'_D \parallel R_L)$, where $R'_D = R_D \parallel r_o \approx R_D$ if r_o is large.


Common-source amplifier

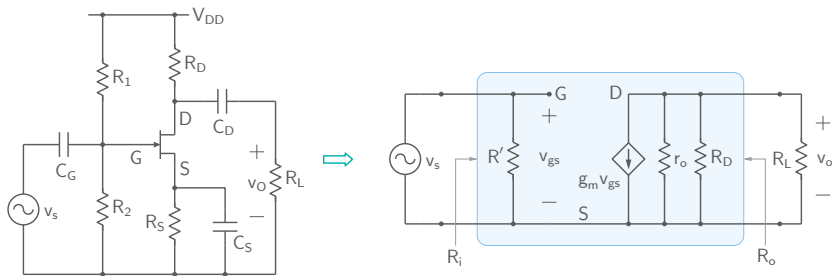

* $A_V \equiv \frac{v_o}{v_s} = -g_m(R'_D \parallel R_L)$, where $R'_D = R_D \parallel r_o \approx R_D$ if r_o is large.

$$A_{VO} = A_V \Big|_{R_L \rightarrow \infty} = -g_m R'_D.$$

Common-source amplifier

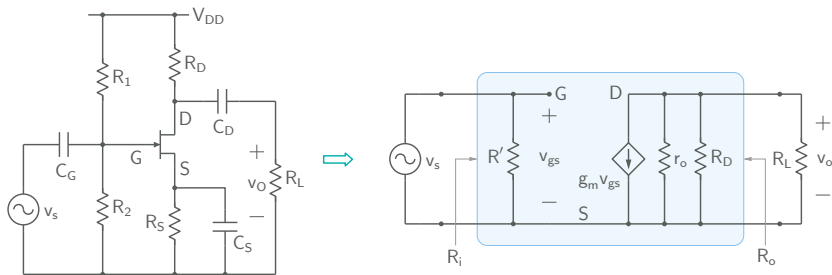


$$* A_V \equiv \frac{v_o}{v_s} = -g_m(R'_D \parallel R_L), \text{ where } R'_D = R_D \parallel r_o \approx R_D \text{ if } r_o \text{ is large.}$$

$$A_{VO} = A_V \Big|_{R_L \rightarrow \infty} = -g_m R'_D.$$


$$* R_i = R' = R_1 \parallel R_2, \quad R_o = R'_D.$$

Common-source amplifier: Example

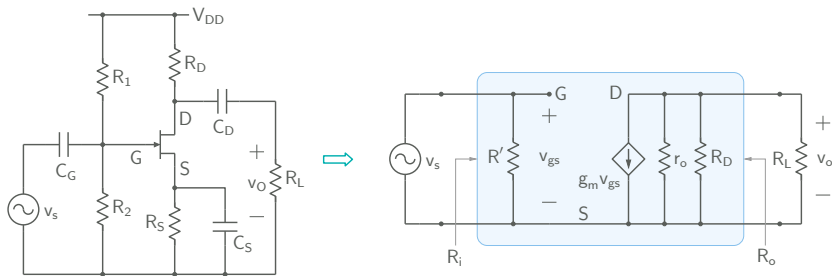

For the common-source amplifier of the last example, find (a) gain with $R_L \rightarrow \infty$ and (b) input resistance R_i .


Common-source amplifier: Example

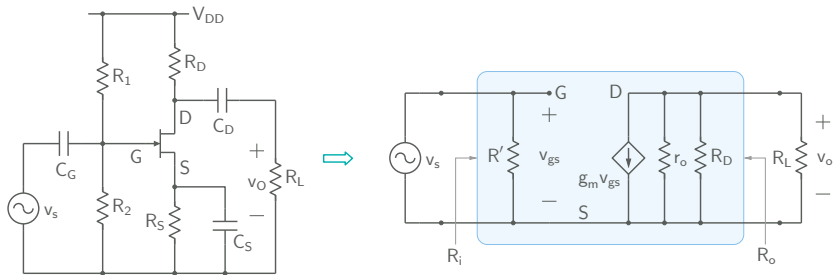

For the common-source amplifier of the last example, find (a) gain with $R_L \rightarrow \infty$ and (b) input resistance R_i .

Solution:

Common-source amplifier: Example

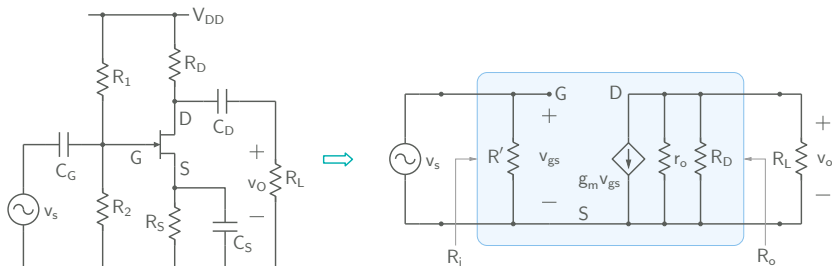


For the common-source amplifier of the last example, find (a) gain with $R_L \rightarrow \infty$ and (b) input resistance R_i .

Solution:

$$g_m = 2 I_{DSS} \left(1 - \frac{V_{GS}^Q}{V_P} \right) \times \left(-\frac{1}{V_P} \right) = 2 (1 \text{ mA}) \left(1 - \frac{-0.735 \text{ V}}{-2 \text{ V}} \right) \times \left(-\frac{1}{-2 \text{ V}} \right) = 0.63 \text{ mS}.$$

Common-source amplifier: Example

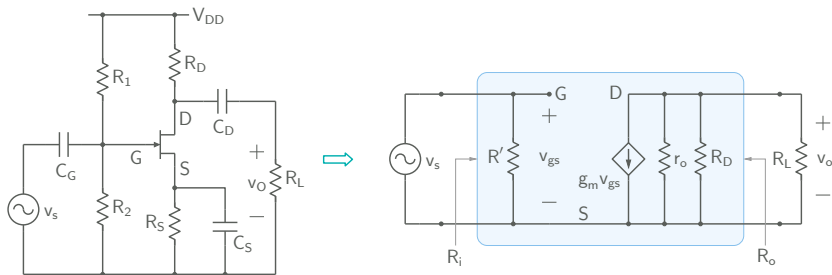


For the common-source amplifier of the last example, find (a) gain with $R_L \rightarrow \infty$ and (b) input resistance R_i .

Solution:

$$g_m = 2 I_{DSS} \left(1 - \frac{V_{GS}^Q}{V_P} \right) \times \left(-\frac{1}{V_P} \right) = 2 (1 \text{ mA}) \left(1 - \frac{-0.735 \text{ V}}{-2 \text{ V}} \right) \times \left(-\frac{1}{-2 \text{ V}} \right) = 0.63 \text{ mS}.$$

(a) $A_{VO} = -g_m R_D = -0.63 \text{ mS} \times 15 \text{ k}\Omega = -9.5$, assuming r_o to be large.

Common-source amplifier: Example

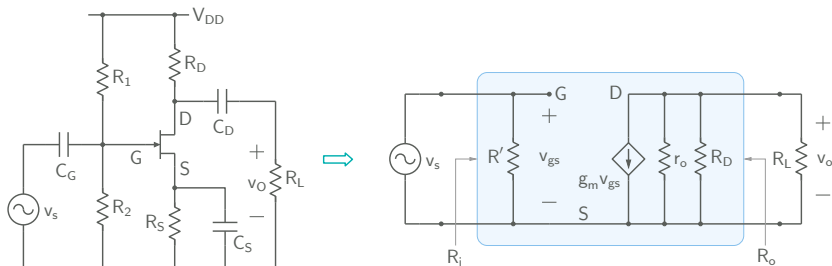

For the common-source amplifier of the last example, find (a) gain with $R_L \rightarrow \infty$ and (b) input resistance R_i .


Solution:

$$g_m = 2 I_{DSS} \left(1 - \frac{V_{GS}^Q}{V_P} \right) \times \left(-\frac{1}{V_P} \right) = 2 (1 \text{ mA}) \left(1 - \frac{-0.735 \text{ V}}{-2 \text{ V}} \right) \times \left(-\frac{1}{-2 \text{ V}} \right) = 0.63 \text{ mS}.$$


(a) $A_{VO} = -g_m R_D = -0.63 \text{ mS} \times 15 \text{ k}\Omega = -9.5$, assuming r_o to be large.

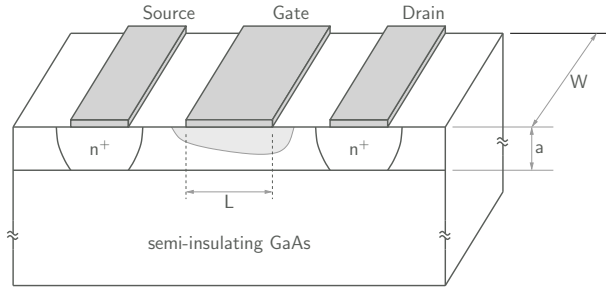(b) $R_i = R_1 \parallel R_2 = 200 \text{ k}\Omega \parallel 23.5 \text{ k}\Omega = 21 \text{ k}\Omega$.

n -channel Metal-Semiconductor Field-Effect Transistor (MESFET)




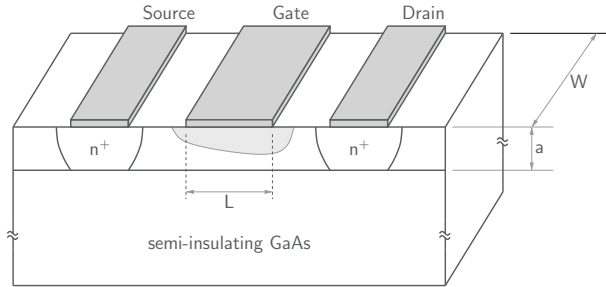n -channel Metal-Semiconductor Field-Effect Transistor (MESFET)




- * In a MESFET, the channel conductance is modulated by a rectifying metal-semiconductor junction.

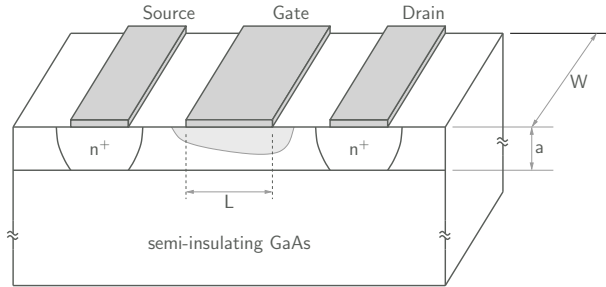n -channel Metal-Semiconductor Field-Effect Transistor (MESFET)




- * In a MESFET, the channel conductance is modulated by a rectifying metal-semiconductor junction.
- * The substrate is semi-insulating, with a resistivity of about $10^8 \Omega\text{-cm}$.

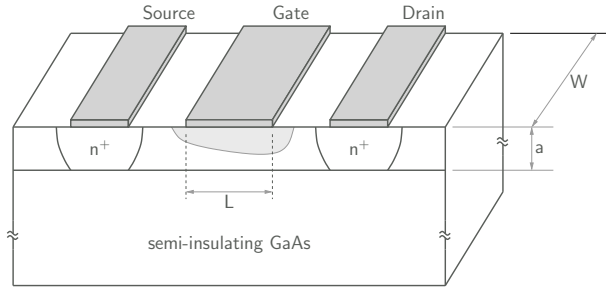n -channel Metal-Semiconductor Field-Effect Transistor (MESFET)




- * In a MESFET, the channel conductance is modulated by a rectifying metal-semiconductor junction.
- * The substrate is semi-insulating, with a resistivity of about $10^8 \Omega\text{-cm}$.
- * On the substrate, an n -type channel region is deposited, and the n^+ source/drain regions are created by ion implantation.

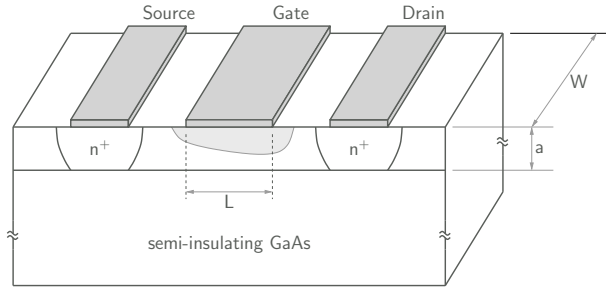n -channel Metal-Semiconductor Field-Effect Transistor (MESFET)




- * In a MESFET, the channel conductance is modulated by a rectifying metal-semiconductor junction.
- * The substrate is semi-insulating, with a resistivity of about $10^8 \Omega\text{-cm}$.
- * On the substrate, an n -type channel region is deposited, and the n^+ source/drain regions are created by ion implantation.
- * The S/D contacts are ohmic; gate contact is rectifying.

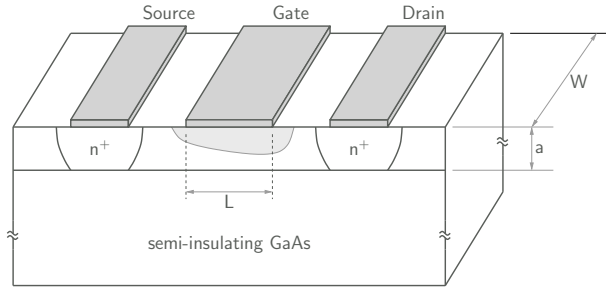n -channel Metal-Semiconductor Field-Effect Transistor (MESFET)




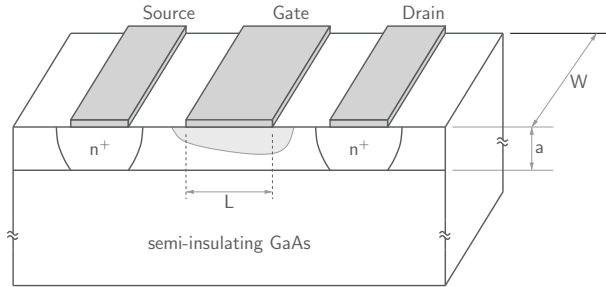n -channel Metal-Semiconductor Field-Effect Transistor (MESFET)




- * For MESFETs, GaAs is preferred over silicon because of its higher electron mobility (typically a factor of 5 larger than μ_n in silicon).

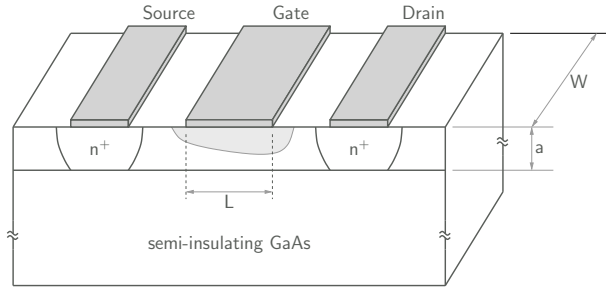n -channel Metal-Semiconductor Field-Effect Transistor (MESFET)



- * For MESFETs, GaAs is preferred over silicon because of its higher electron mobility (typically a factor of 5 larger than μ_n in silicon).
- * Small channel lengths (tenths of a micron) are often used to make the transistor faster, by reducing the transit time from source to drain and also the gate capacitance.

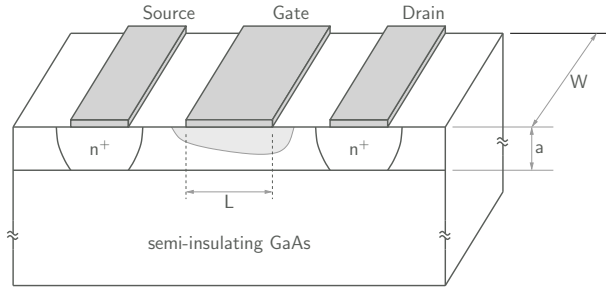n -channel Metal-Semiconductor Field-Effect Transistor (MESFET)



- * For MESFETs, GaAs is preferred over silicon because of its higher electron mobility (typically a factor of 5 larger than μ_n in silicon).
- * Small channel lengths (tenths of a micron) are often used to make the transistor faster, by reducing the transit time from source to drain and also the gate capacitance.
- * GaAs MESFETs are commonly used in high-frequency (a few GHz) applications.